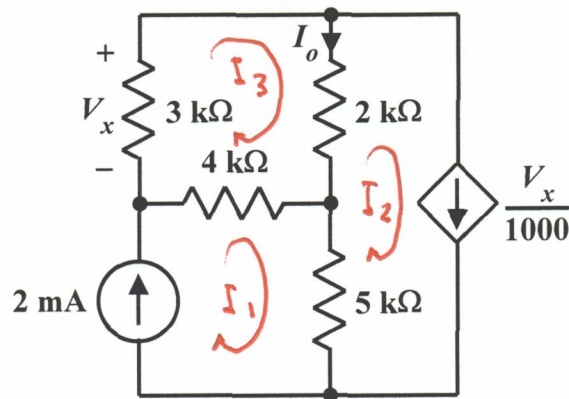


EE 2240  
**Problem #11**

Use mesh analysis to find  $I_o$ .



$$I_1 = 2 \text{ mA} \quad (\text{constraint})$$

$$I_2 = \frac{V_x}{1000} \quad (\text{constraint})$$

$$3000 I_3 + 2000(I_3 - I_2) + 4000(I_3 - I_1) = 0 \quad (\text{mesh 3})$$

$$V_x = -3000 I_3 \quad (\text{definition})$$

$I_1$  matrix form:

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & -0.001 \\ -4000 & -2000 & 9000 & 0 \\ 0 & 0 & 3000 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ V_x \end{bmatrix} = \begin{bmatrix} 0.002 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Solving yields  $I_2 = -1.6 \text{ mA}$  and  $I_3 = \frac{8}{15} \text{ mA}$

Then  $I_o = I_3 - I_2 = \frac{32}{15} \text{ mA}$