

EE 2240
Problem #07

Use the nodal analysis method to determine V_x and I_y .

