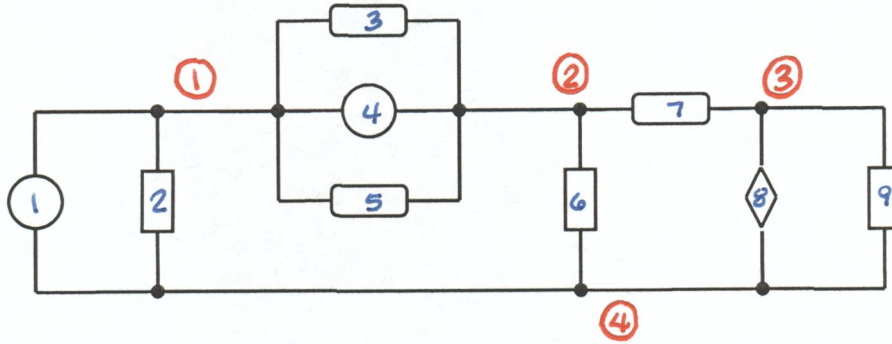


EE 2240
Problem #04



a. How many nodes does the circuit have?

4

b. How many branches does the circuit have?

9