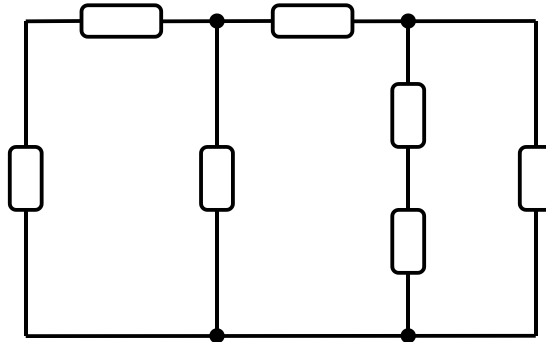


EE 2240
Problem #06



- a. How many nodes does the circuit have?

- b. How many branches does the circuit have?