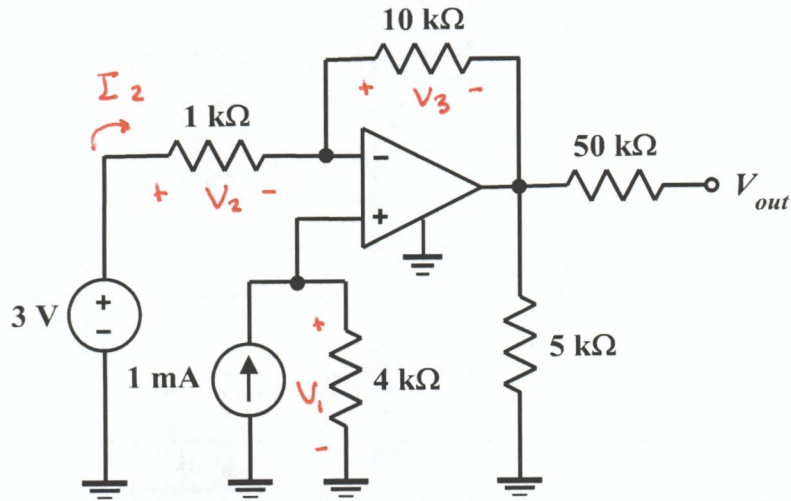


EE 2240
Problem #06

Calculate the value of V_{out} .



$$V_1 = (1\text{mA})(4\text{k}\Omega) = 4\text{V}$$

$$V_2 = 3\text{V} - V_1 = 3\text{V} - 4\text{V} = -1\text{V}$$

$$I_2 = \frac{V_2}{1\text{k}\Omega} = \frac{-1\text{V}}{1\text{k}\Omega} = -1\text{mA}$$

$$V_3 = (10\text{k}\Omega) I_2 = -(10\text{k}\Omega)(1\text{mA}) = -10\text{V}$$

$$V_{out} = -V_3 + V_1 = -(-10\text{V}) + 4\text{V} = 14\text{V}$$