

EE 2240
Problem #08

Find V_o .

