

EE 2240
Problem #05

Determine the amount of power absorbed by the 4-k Ω resistor.

