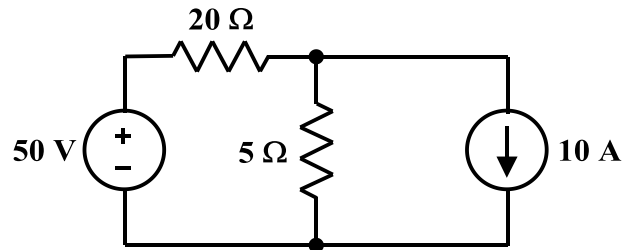


EE 2240  
**Problem #08**

Given the circuit shown below:



- How much power does the  $5\Omega$  resistor absorb?
- How much power does the  $20\Omega$  resistor absorb?
- Does the independent current source deliver power or absorb power? How much?
- Does the independent voltage source deliver power or absorb power? How much?