

EE 2240  
**Problem #09**

Determine which components are absorbing power, and which are delivering power, and how much power each is absorbing or delivering.

