

EE 2240  
**Problem #03**

The capacitor voltage,  $v_C(t)$ , in the circuit shown below is

$$v_C(t) = 5e^{-8t} \text{ V for } t \geq 0.$$

Determine the value of  $C$  and the initial value of  $v_C(t)$ .

