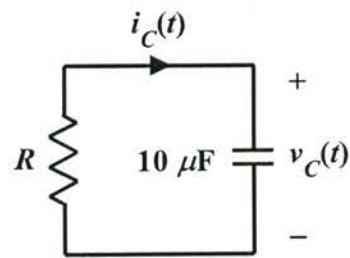


EE 2240  
Problem #04

The capacitor current,  $i_C(t)$ , in the circuit shown below is

$$i_C(t) = 50e^{-5t} \mu\text{A} \quad \text{for } t \geq 0.$$

Determine the value of  $R$  and the initial value of  $v_C(t)$ .



$$\frac{1}{R(10\mu\text{F})} = 5 \Rightarrow R \approx \frac{1}{5(10\mu\text{F})} = 20 \text{ k}\Omega$$

$$\begin{aligned} v_C(t) &= -R i_C(t) \Rightarrow v_C(0) = -(20 \text{ k}\Omega) i_C(0) \\ &= -(20 \text{ k}\Omega)(50 \mu\text{A}) \\ &= -1 \text{ V} \end{aligned}$$