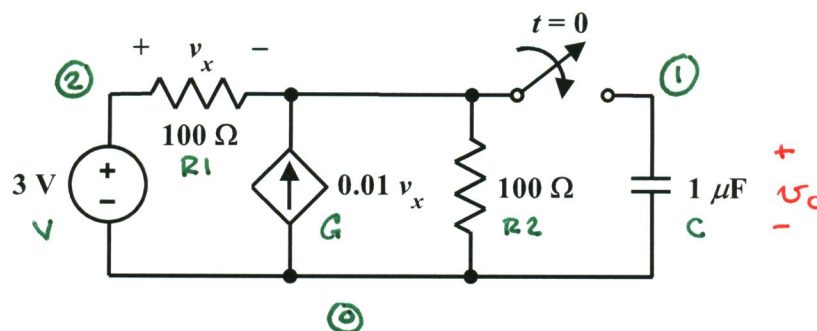


EE 2240  
**Problem #08**

The capacitor is initially uncharged when the switch is closed at  $t=0$ . Find an analytical expression for the energy stored in the capacitor for  $t \geq 0$ . Also use PSpice and Probe to plot the energy stored in the capacitor for  $0 \leq t \leq 5\tau$ , where  $\tau$  is the circuit time constant for  $t > 0$ .



$$v_c(0) = 0$$

For  $t > 0$ :

$$10^{-6} \dot{v}_c + \frac{1}{100} v_c - 0.01(3 - v_c) + \frac{1}{100}(v_c - 3) = 0$$

$$\text{or } 10^{-6} \dot{v}_c + 0.03 v_c = 0.06$$

$$\Rightarrow \dot{v}_c + 30000 v_c = 60000$$

↓

$$\tau = \frac{1}{30000} = 33\frac{1}{3} \mu\text{s}$$

$$\Rightarrow 30000 v_c(\infty) = 60000$$

$$\therefore v_c(\infty) = 2 \text{ V}$$

$$\therefore v_c(t) = (-2 e^{-30000t} + 2) \text{ V}, t \geq 0$$

$$w_c(t) = \frac{1}{2} (1 \mu\text{F}) v_c^2(t)$$

$$= \frac{1}{2} \times 10^{-6} \times (4 e^{-60000t} - 8 e^{-30000t} + 4)$$

$$= (2 e^{-60000t} - 4 e^{-30000t} + 2) \mu\text{J}, t \geq 0$$

Problem #08

V 2 0 DC 3

R1 2 1 100

G 0 1 2 1 0.01

R2 1 0 100

C 1 0 1u IC=0

.TRAN 1u 167u 0 1u USE

.PROBE

↑

ST = 167us

.END

See the next page for the output.

Problem #08

