EE 2240 **Problem #07**

Find v(t) for $t \ge 0$ if v(0) = -1V and i(0) = 1A.

