## EE 2240 **Problem #08**

Find i(t) for  $t \ge 0$  if v(0) = -1/3V and i(0) = 1A.

