

EE 2240
Problem #03

Determine the value of V_x .

