

EE 2240
Problem #05

Find V_o .

