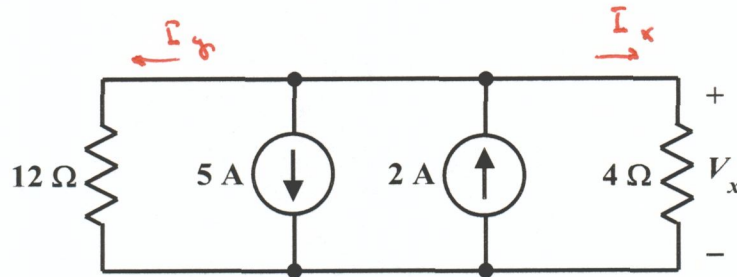


EE 2240  
Problem #06

Determine the value of  $V_x$ .



$$I_d = \frac{V_x}{12\Omega}$$

$$I_x = \frac{V_x}{4\Omega}$$

$$I_d + 5A - 2A + I_x = 0 \quad (\text{KCL})$$

$$\therefore \frac{V_x}{12} + 5 - 2 + \frac{V_x}{4} = 0$$

$$4 \frac{V_x}{12} = -3$$

$$V_x = -9V$$