

EE 2240  
**Problem #01**

Use source transformations to reduce the circuit shown below to its simplest possible equivalent with respect to terminals *A-B*.

