

EE 2240
Problem #02

Use a sequence of source transformations and equivalent resistance calculations to determine V_x in the circuit shown below.

