## EE 2240 **Problem #03**

Use a sequence of source transformations to find  $I_o$ .

