

EE 2240
Problem #01

Use the superposition method to find V_o .

