

EE 2240  
Problem #01

Find  $I_o$  using Thévenin's Theorem.

