

EE 2240
Problem #03

The $4\text{k}\Omega$ resistor is to be treated as the “load” for this problem. Use a sequence of source transformations to reduce the remainder of the circuit to its Thévenin equivalent, and then apply the voltage-divider principle to find V_o .

