

EE 2240
Problem #04

The $2\text{k}\Omega$ resistor is the load. Use the method described in class to find the Thévenin equivalent of the remainder of the circuit. (*Do not use source transformations!*) Then determine the value of I_o .

