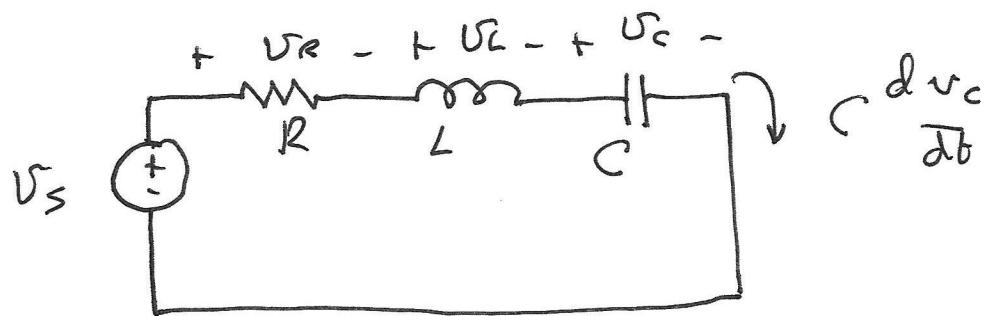


$$i_R = \frac{1}{R} L \frac{di_L}{dt}$$

$$i_C = C \frac{d}{dt} \left[L \frac{di_L}{dt} \right] = C L \frac{d^2 i_L}{dt^2}$$

$$i_C + i_R + i_L = i_s$$

$$C L \frac{d^2 i_L}{dt^2} + \frac{L}{R} \frac{di_L}{dt} + i_L = i_s$$



$$V_R = R C \frac{dV_C}{dt}$$

$$V_L = L \frac{d}{dt} \left(C \frac{dV_C}{dt} \right) = L C \frac{d^2 V_C}{dt^2}$$

$$L C \frac{d^2 V_C}{dt^2} + R C \frac{dV_C}{dt} + V_C = V_S$$

AC circuit analysis




Sources are sinusoidal

$$v_s = 177 \cos(2\pi 60t + \phi)$$

$$LC \frac{d^2 v_c}{dt^2} + RC \frac{dv_c}{dt} + v_c = v_s$$

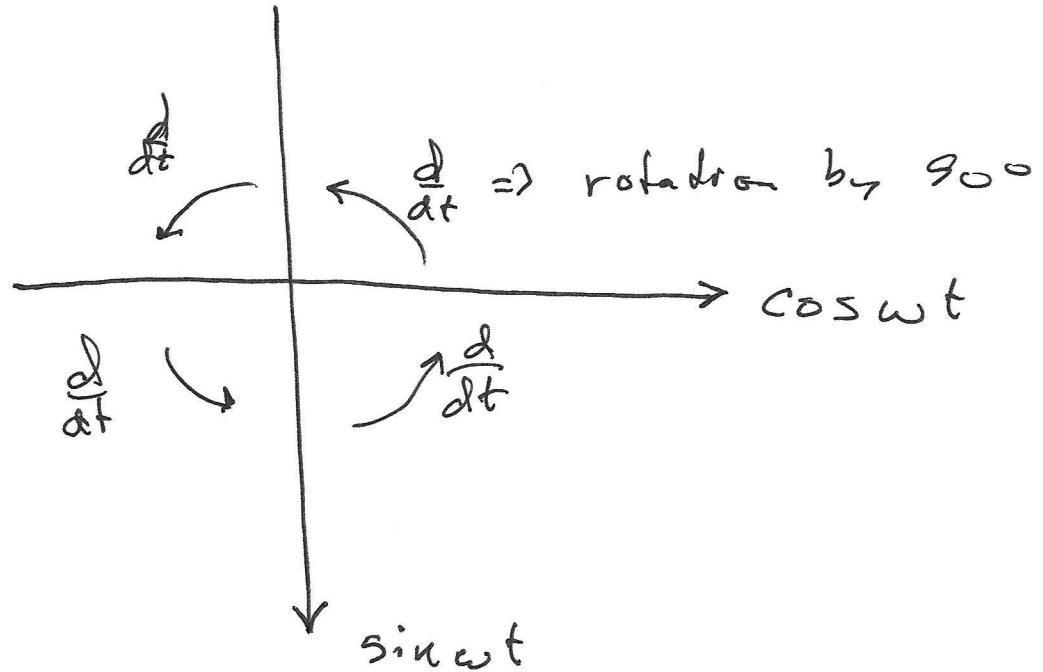C \rightarrow $a \sin \omega t$ B $\cos \omega t$ A $\sin \omega t$ \uparrow
 sin ωt



Complex Numbers

$$x^2 + 4x + 13 = 0$$


$$(x+2)^2 + 3^2 = 0$$

$$x = -2 \pm j3$$

$$\begin{aligned}
 x &= \frac{-4 \pm \sqrt{4^2 - 4 \cdot 1 \cdot 13}}{2 \cdot 1} \\
 &= \frac{-4 \pm \sqrt{16 - 52}}{2} \\
 &= \frac{-4 \pm \sqrt{-36}}{2} = \frac{\sqrt{-1} \sqrt{36}}{2} = 6j \\
 &= \frac{-4 \pm 6j}{2} \\
 &= -2 \pm 3j
 \end{aligned}$$

Complex Plane

Imaginary

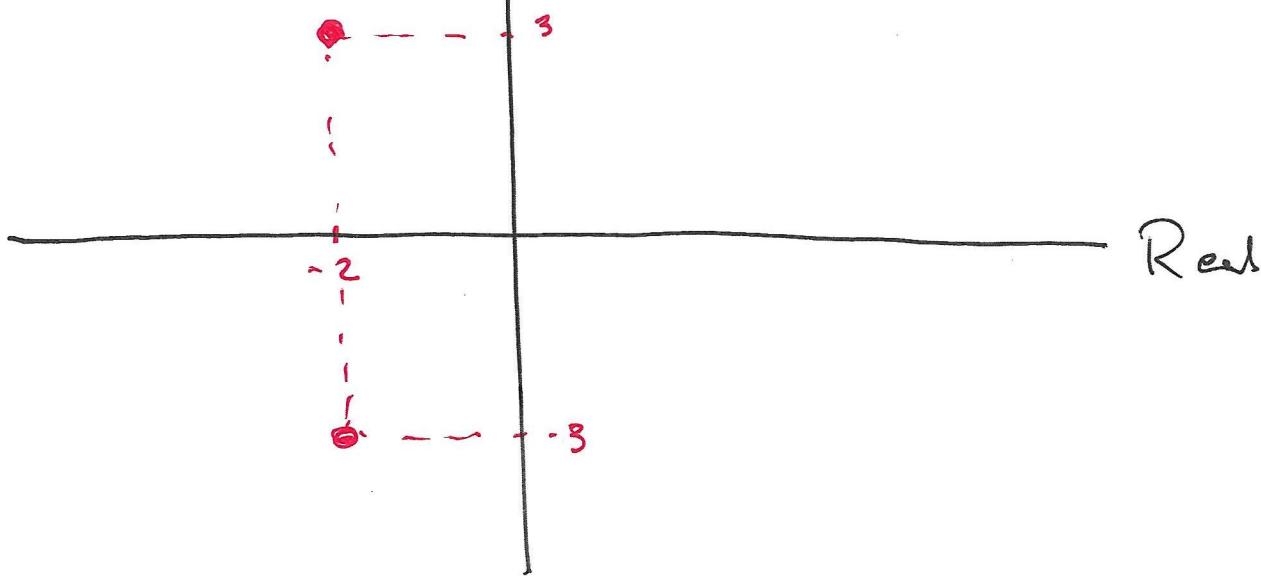


Let

$$z = (a + jb)$$

↑ ↑
Real Imaginary
Part Part

Cartesian Form
or Rectangular Form

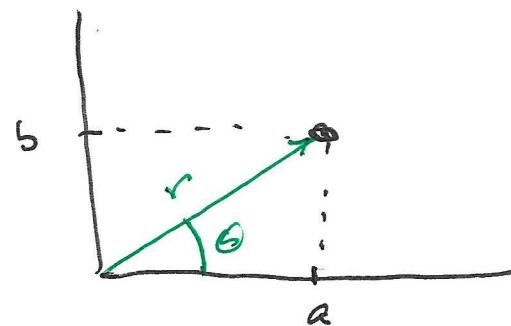

$$a = r \cos \theta$$

$$b = r \sin \theta$$

$$z = r \cos \theta + j r \sin \theta$$

Euler's Identity


$$r e^{\pm j\theta} = r \cos \theta \pm r j \sin \theta$$

Exponential Form

$$r \angle \theta$$

Polar Form
Phasor
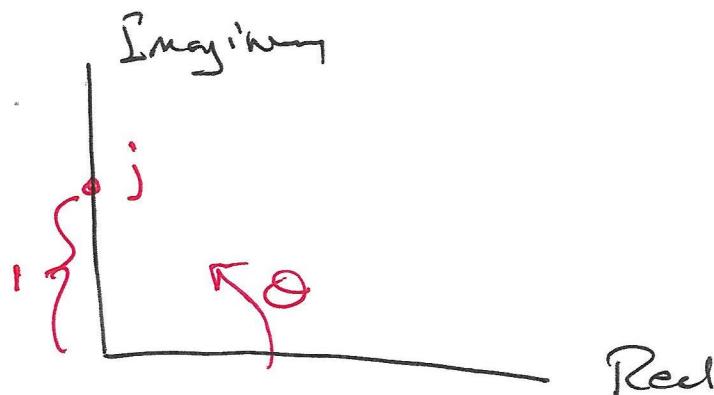
$$r \angle \theta = r e^{j\theta} = r (\cos \theta + j \sin \theta)$$



$$j = 1 \angle 90^\circ$$


Multiply a complex number by j .

$$A[\theta \cdot j] = A[\theta \cdot 1[90^\circ]$$


$$= A e^{j\theta} \cdot 1 e^{j90^\circ}$$

$$= A e^{j(\theta + 90^\circ)}$$


$$= A \underline{[\theta + 90^\circ]}$$

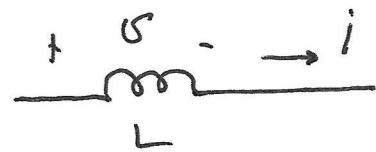
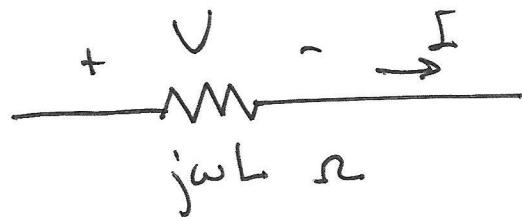
$$v = L \frac{di}{dt} \Rightarrow V = L(j\omega L)$$




Impedance

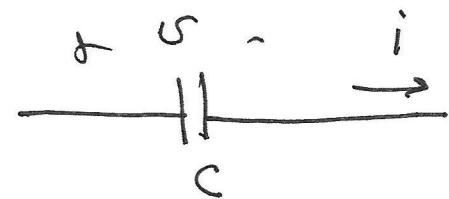


$$i = C \frac{dV}{dt} \Rightarrow I = C j\omega V$$


$$V = \frac{1}{j\omega C} I$$

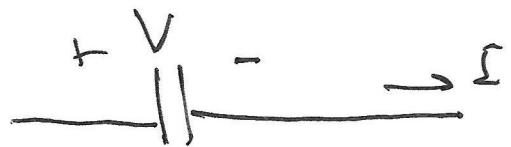

$$\frac{1}{j\omega C} \text{~N}$$

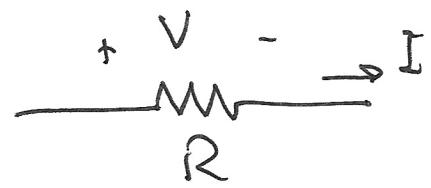

$$V = RI$$

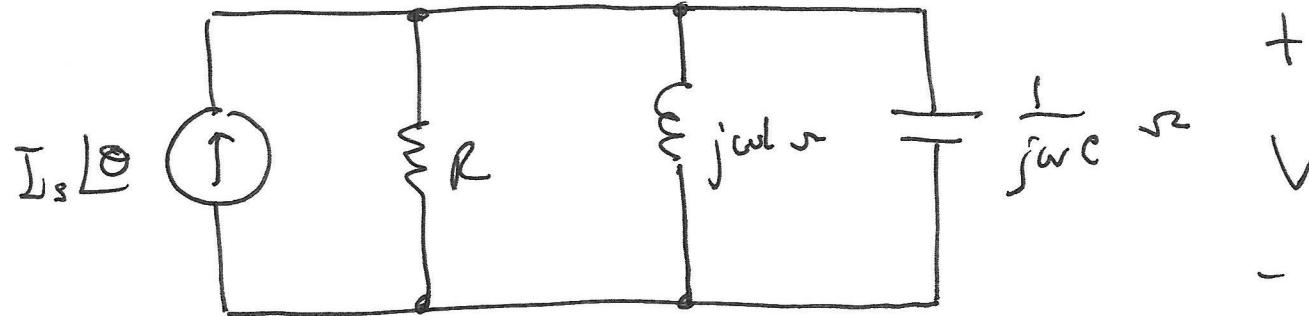

$$\frac{V}{R} + \frac{V}{j\omega L} + \frac{V}{(\frac{1}{j\omega C})} = I_s \leftarrow$$

$$\left(\frac{V}{R} + \frac{V}{j\omega L} + j\omega C V \right) = I_s \leftarrow$$

$$\frac{j\omega L + R + \cancel{(j\omega L)(j\omega C)}}{j\omega L \cdot R} V = I_s \mathbb{L}$$

$- \omega^2 L C$

$$\frac{(R - \omega^2 LC) + j\omega L}{j\omega L R} V = I_s \mathbb{L}$$

$$V = \frac{j\omega L R}{(R - \omega^2 LC) + j\omega L} I_s \mathbb{L}$$

$$\text{Let } z_1 = a + jb$$

$$z_2 = c + jd$$

$$z_1 + z_2 = a + jb + c + jd = (a+c) + j(b+d)$$

$$z_1 = 1 + j2$$

$$z_2 = 3 - js$$

$$z_1 + z_2 = 1 + j2 + 3 - js = 4 - j3$$

$$Z_1 = a + jb = A_1 \angle \Theta_1$$

$$Z_2 = c + jd = A_2 \angle \Theta_2$$

$$\begin{aligned} Z_1 \cdot Z_2 &= (a+jb)(c+jd) \\ &= ac + jad + jbc - bd \\ &= (ac - bd) + j(ad + bc) \end{aligned}$$

$$\begin{aligned} Z_1 \cdot Z_2 &= A_1 \angle \Theta_1 \cdot A_2 \angle \Theta_2 \\ &= A_1 A_2 \angle \Theta_1 + \Theta_2 \end{aligned}$$

$$z_1 = a + jb = A_1 \angle \theta_1$$

$$z_2 = c + jd = A_2 \angle \theta_2$$


$$\begin{aligned} \frac{z_1}{z_2} &= \frac{a+jb}{c+jd} \cdot \frac{c-jd}{c-jd} \\ &= \frac{(a+jb)(c-jd)}{c^2 - jcd + jdc + d^2} \\ &= \frac{(a+jb)(c-jd)}{(c^2 + d^2)} \\ &= \frac{ac - jad + jb c + bd}{c^2 + d^2} \\ &= \frac{(ac + bd) + j(bc - ad)}{c^2 + d^2} \end{aligned}$$

$$\frac{z_1}{z_2} = \frac{A_1 e^{j\theta_1}}{A_2 e^{j\theta_2}} = \frac{A_1}{A_2} e^{j(\theta_1 - \theta_2)}$$

$$A_1 e^{j\theta_1} \cdot A_2 e^{j\theta_2} = A_1 A_2 e^{j(\theta_1 + \theta_2)}$$

$$\frac{A_1 e^{j\theta_1}}{A_2 e^{j\theta_2}} = \frac{A_1}{A_2} e^{j(\theta_1 - \theta_2)}$$
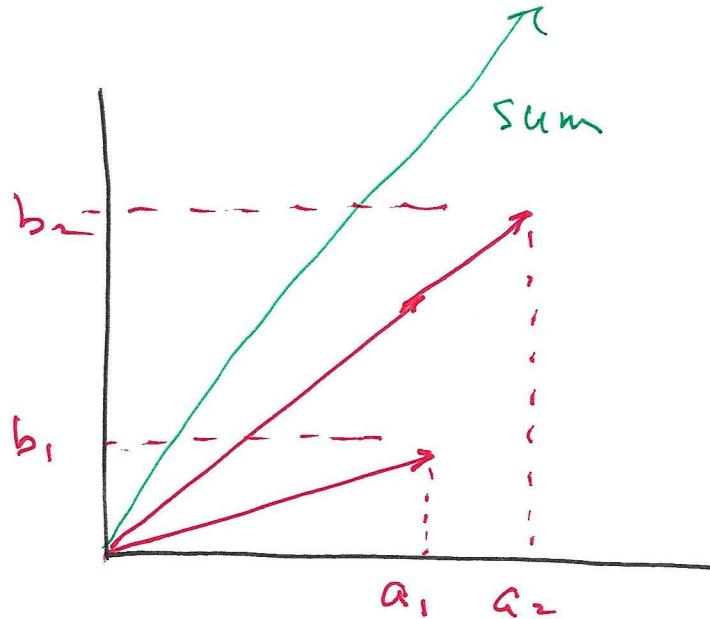
$$\begin{aligned} \text{Imag. part} \\ = b_1 + b_2 \end{aligned}$$




$$\text{Real part of sum} = a_1 + a_2$$

$$\text{Sum} = (a_1 + a_2) + j(b_1 + b_2)$$

$$\text{Magnitude} = \sqrt{(a_1 + a_2)^2 + (b_1 + b_2)^2}$$

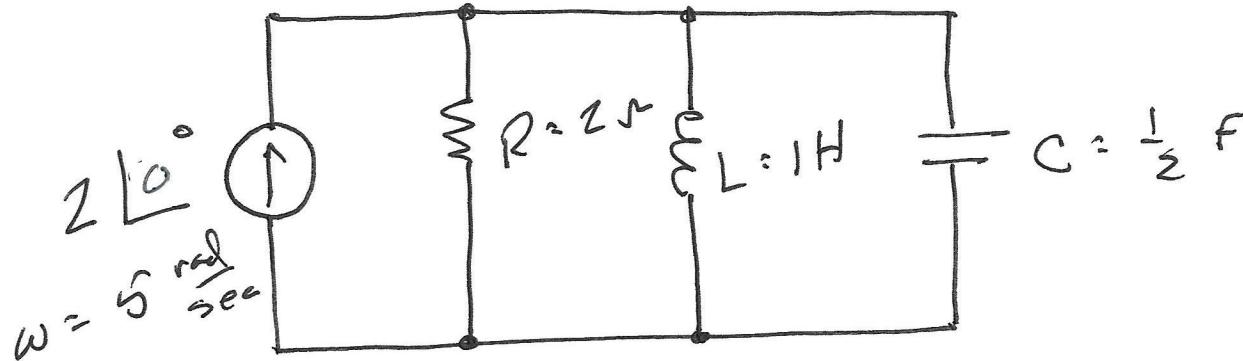
$$\text{Angle} = \tan^{-1} \frac{b_1 + b_2}{a_1 + a_2}$$



$$\omega = 5 \frac{\text{rad}}{\text{sec}}$$

$$Z_L = j\omega L = j5 \Omega$$
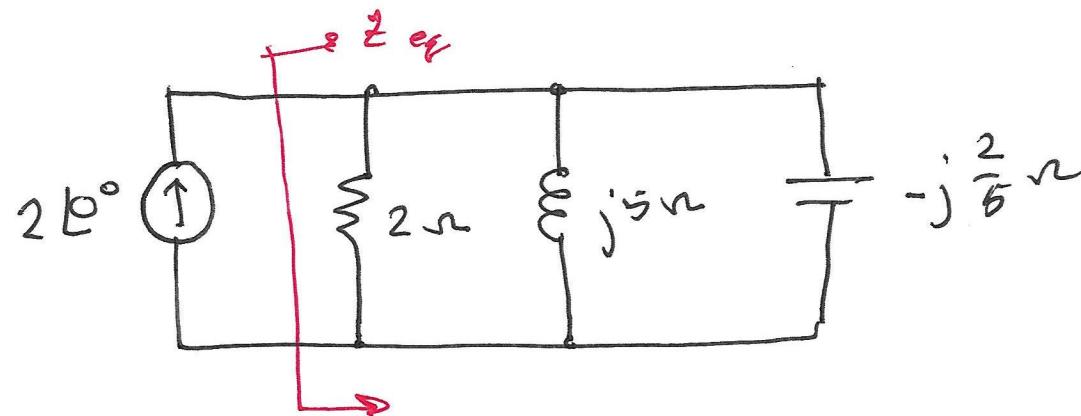
$$Z_C = \frac{1}{j\omega C} = -j\frac{2}{5} \Omega$$



$$Y_{eq} = \frac{1}{2} + \frac{1}{j5} + \frac{1}{(-j\frac{2}{5})}$$

$$= \frac{1}{2} - j\frac{1}{5} + j\frac{5}{2} \quad S$$

$$= \frac{1}{2} + j\frac{23}{10} \quad S$$

$$Z_{eq} = \frac{1}{Y_{eq}} = \frac{1}{\frac{1}{2} + j\frac{23}{10}}$$

$$= \frac{10}{5 + j23}$$

$$= \frac{10}{(25 + 23^2)^{1/2}} \angle \tan^{-1} \frac{23}{5}$$