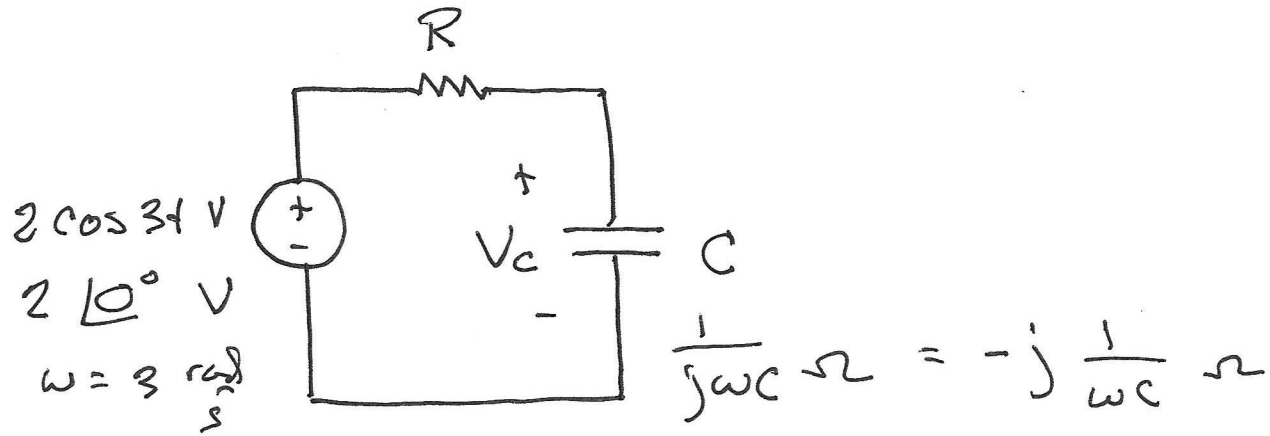


$$z = 3 + j5$$

$$|z| = \sqrt{3^2 + 5^2}$$

$$\theta = \angle z = \tan^{-1} \frac{5}{3}$$



What is the steady-state AC voltage across the capacitor. (V_c)

$$\begin{aligned}
 V_c &= \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \cdot 2 \angle 0^\circ \\
 &= \frac{\frac{2}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{2}{1 + j\omega RC} = \frac{2}{1 + j3RC}
 \end{aligned}$$

Choose $R = 1 \Omega$, $C = \frac{1}{3} \text{ F}$

$$V_C = \frac{2}{1 + j(3)(1)(\frac{1}{3})} = \frac{2}{1 + j}$$

$$z = 1 + j = \sqrt{2} \angle 45^\circ$$

$$|z| = \sqrt{1^2 + 1^2} = \sqrt{2}$$

$$\angle z = \tan^{-1} \frac{1}{1} = 45^\circ$$


$$V_C = \frac{2}{\sqrt{2} \angle 45^\circ} = \sqrt{2} \angle -45^\circ \text{ V}$$

$$v_{C_{ss}}(t) = \sqrt{2} \cos(3t - 45^\circ) \text{ V}$$

$$\frac{A \angle \theta_1}{B \angle \theta_2} = \frac{A}{B} \angle (\theta_1 - \theta_2)$$

$$\frac{A e^{j\theta_1}}{B e^{j\theta_2}} = \frac{A}{B} e^{j(\theta_1 - \theta_2)}$$
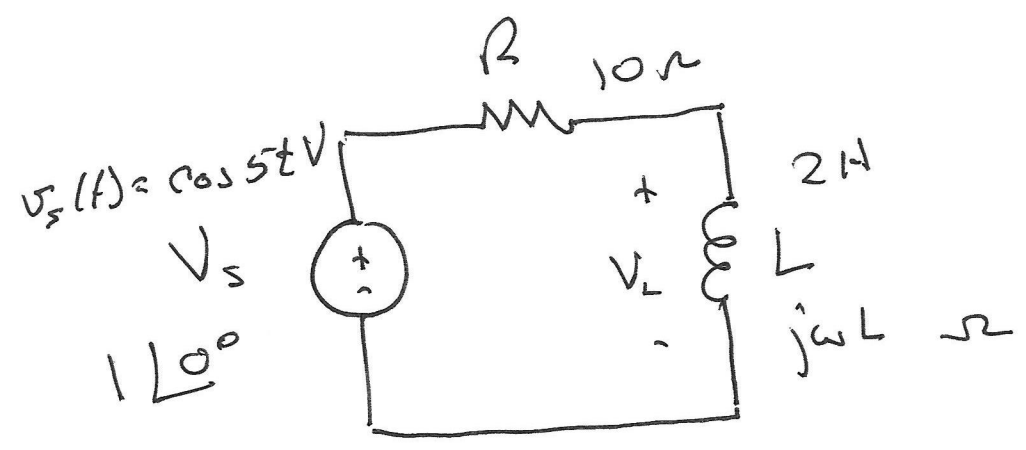
$$= \frac{A}{B} \angle (\theta_1 - \theta_2)$$



$\omega = 5$
 $R = 10$
 $j = 2$
 $j\omega L = j10$

$$V_L = \frac{j\omega L}{R + j\omega L} \cdot V_s$$


$$V_L = \frac{j10}{10 + j10} \cdot V_s = \frac{j10}{10 + j10} \cdot 1 \angle 0^\circ$$

$$= \frac{10 \angle 90^\circ}{\sqrt{200} \angle 45^\circ} \cdot 1 \angle 0^\circ = \frac{1}{\sqrt{2}} \angle^{90+0-45} 45^\circ \text{ V}$$

or

$$V_L = \frac{j}{1+j} = \frac{1 \angle 90^\circ}{\sqrt{2} \angle 45^\circ} = \frac{1}{\sqrt{2}} \angle 45^\circ \text{ V}$$
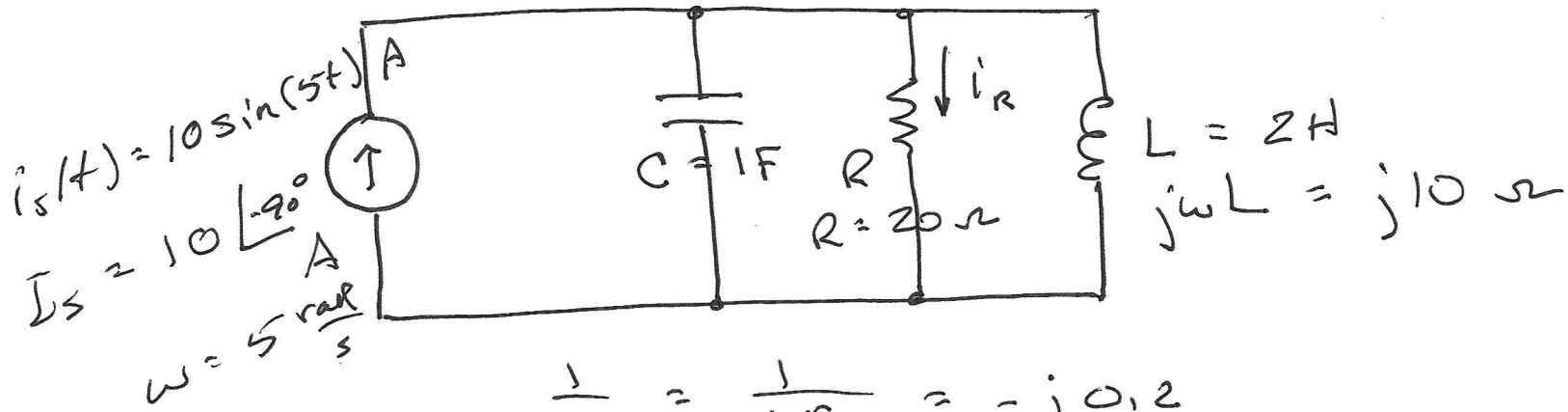
$$V_{L_{ss}}(t) = \frac{1}{\sqrt{2}} \cos(5t + 45^\circ) \text{ V}$$



$$\frac{1}{j\omega C} = \frac{1}{j5} = -j0.2$$

Find $i_R(t)$

$$\begin{aligned} \tilde{I}_R &= \frac{\frac{1}{R}}{j\omega C + \frac{1}{R} + j\omega L} \cdot \tilde{I}_s \\ &= \frac{\frac{1}{20}}{j5 + \frac{1}{20} - j\frac{1}{10}} \cdot 10 \angle -90^\circ \\ &= \frac{1}{j100 + 1 - j'2} \cdot 10 \angle -90^\circ \end{aligned}$$


$$I_R = \frac{1}{1 + j98} \cdot 10 \angle -90^\circ$$

$$\approx \frac{1}{j100} \cdot 10 \angle -90^\circ$$

$$= .01 \angle -90^\circ \cdot 10 \angle -90^\circ$$

$$= .1 \angle -180^\circ$$
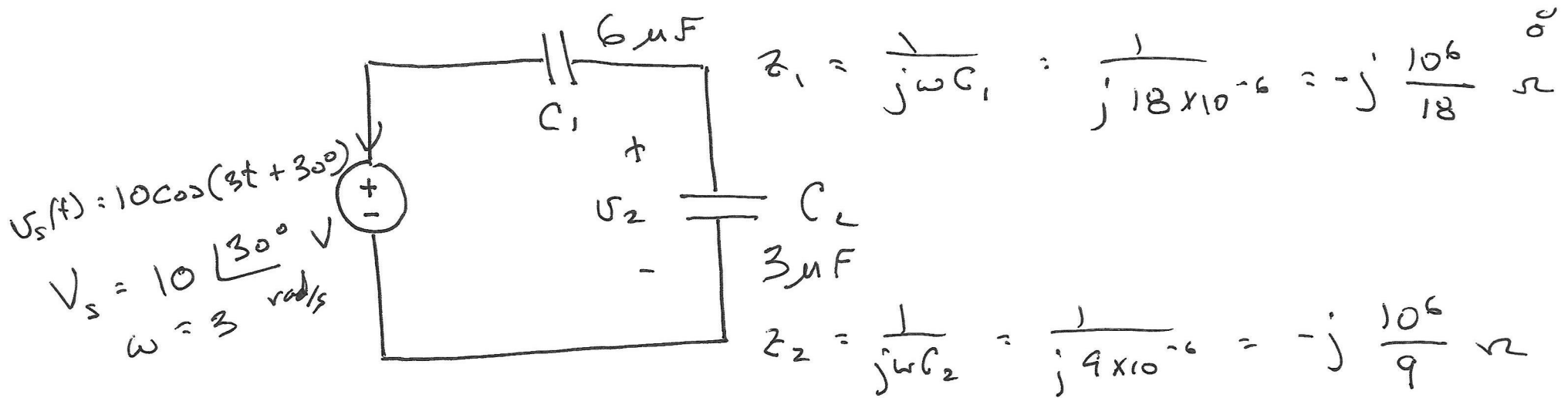
$$i_R(t) \approx .1 \cos(5t - 180^\circ) \text{ A}$$



What if $v_s(t) = 10 \sin(3t + 30^\circ)$?
 What is the proper phase notation?
 $10 \angle -60^\circ$ w.r.t. \cos
 $\omega = 3 \text{ rad/s}$

$$\begin{aligned}
 V_2 &= \frac{z_2}{z_1 + z_2} \cdot V_s = \frac{-j \frac{10^6}{9}}{-j \frac{10^6}{18} - j \frac{10^6}{9}} \cdot 10 \angle 30^\circ \cdot \left(\frac{18}{10^6} \right) \\
 &= \frac{-j 2}{-j - j 2} \cdot 10 \angle 30^\circ = \frac{2}{1 + 2} \cdot 10 \angle 30^\circ \\
 &= \frac{20}{3} \angle 30^\circ
 \end{aligned}$$

$$v_2(t) = \frac{20}{3} \cos(3t + 30^\circ) \text{ V}$$