
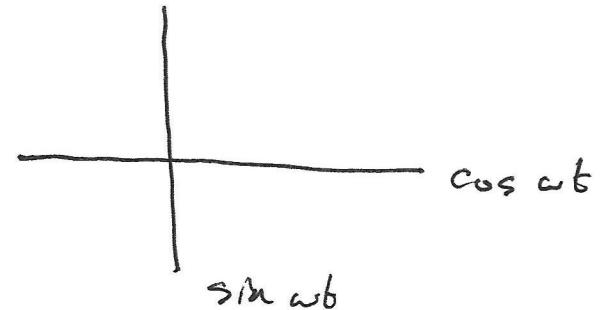


Step 1

Express the circuit in the time domain.

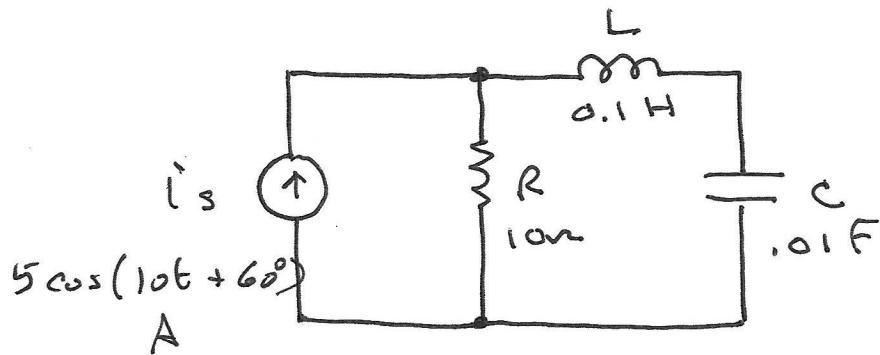


$$\omega = 2\pi f$$

\uparrow
rad/s \uparrow Hz

Step 2

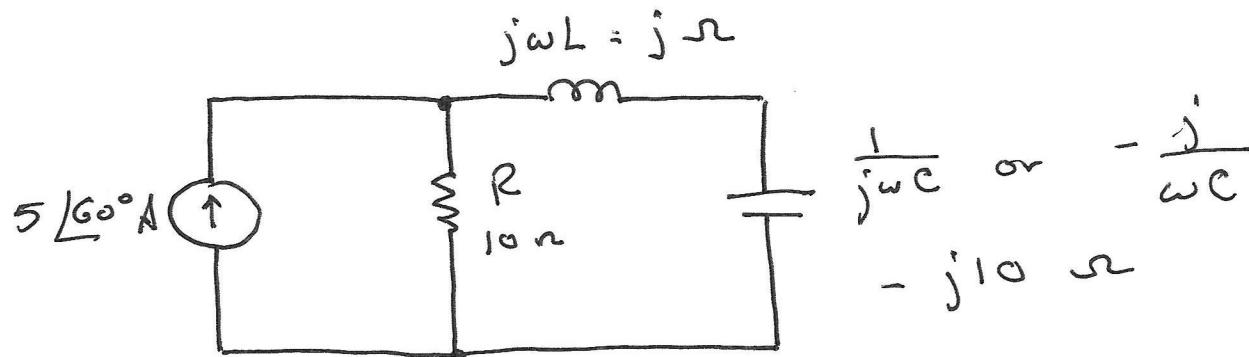Represent the circuit in the phasor domain:





Step 3

Solve as if a resistor problem,
but impedances are complex numbers.


Determine the magnitude and phase angle
of the variable of interest.

Step 4

Convert back to the time domain.

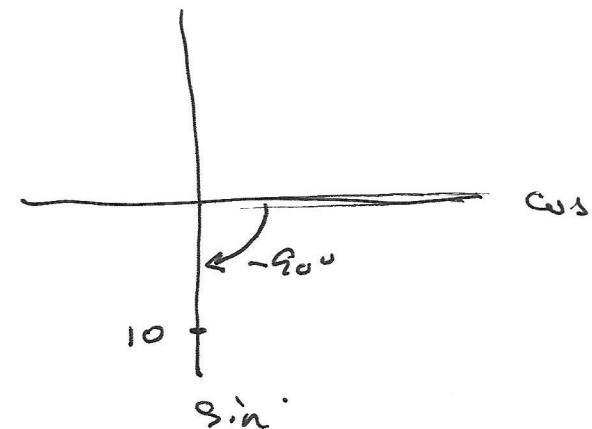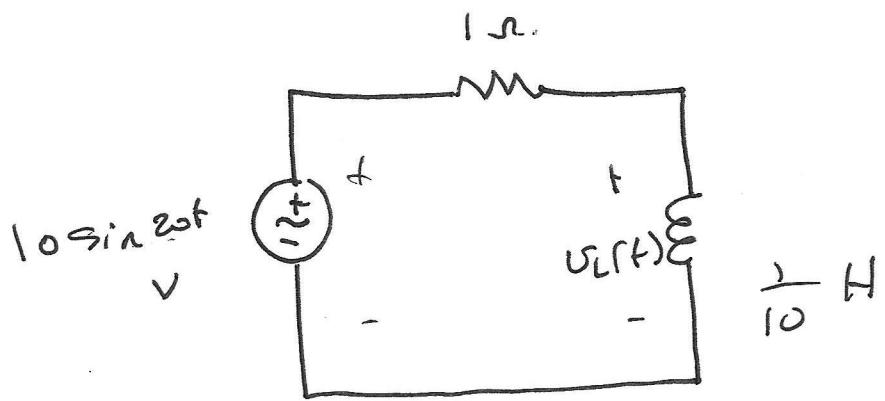

↓ convert to phasor domain

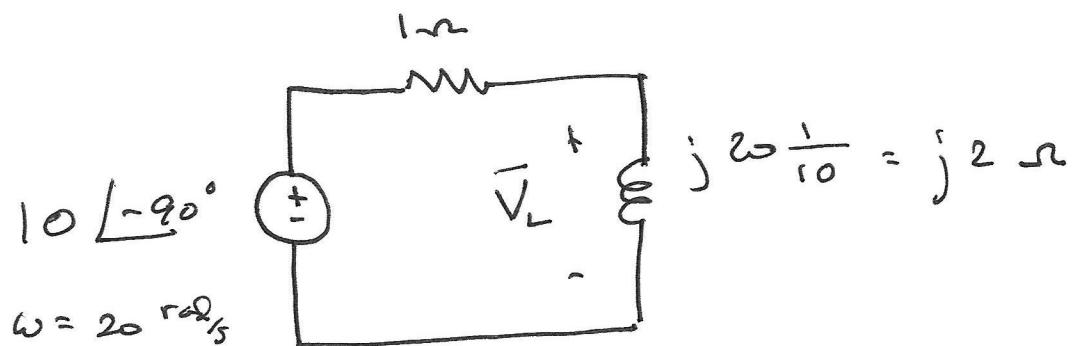

↓ solve for V_L


$$V_L = \frac{j^2}{1+j^2} \cdot 10 \angle -90^\circ = \frac{2 \angle 90^\circ}{\sqrt{5} \tan^{-1} \frac{2}{1}} \cdot 10 \angle -90^\circ$$

$$\sqrt{5} \angle 63.4^\circ$$


$$V_L = \frac{20}{\sqrt{5}} \angle -63.4^\circ$$

↓ Convert to time domain
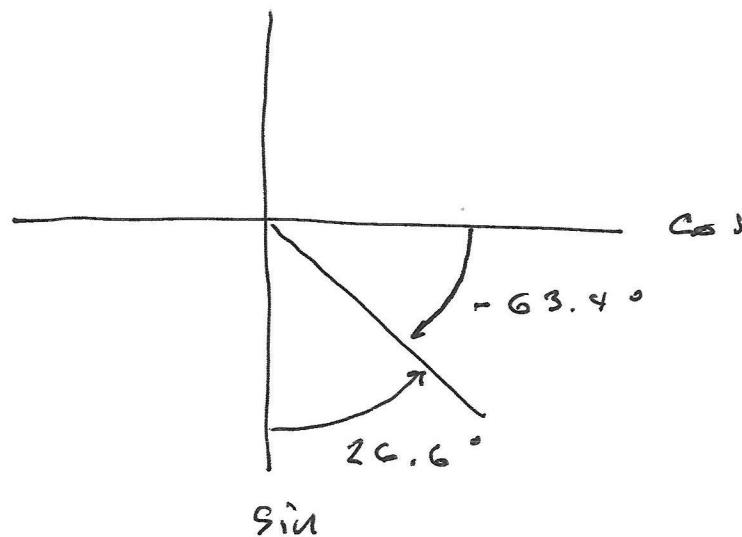
$$v_L(t) = \frac{20}{\sqrt{5}} \cos(20t - 63.4^\circ) \text{ V}$$



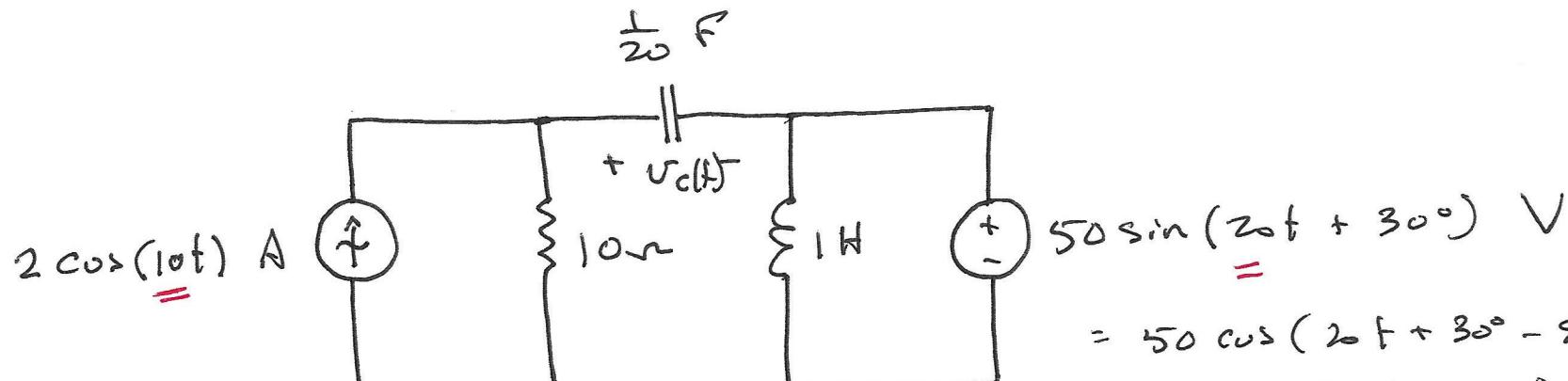
$$v_L(t) = \frac{20}{\sqrt{5}} \sin(20t + 26.6^\circ) \text{ V}$$



$$\frac{1}{j\omega C} = \frac{1}{j10 \cdot \frac{1}{20}} = -j^2$$


$$j\omega L = j10 \cdot 1 = j10$$

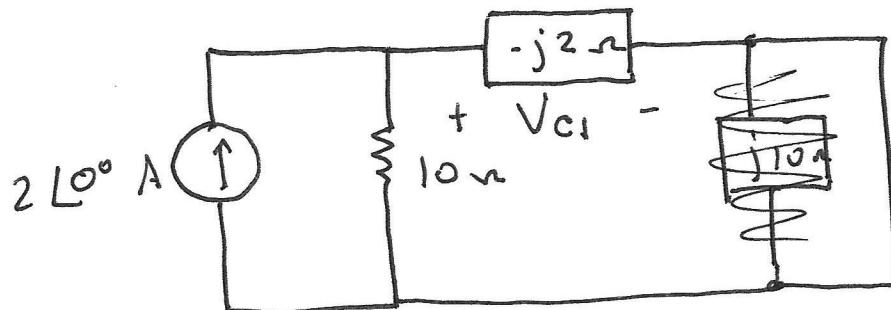

Solve for V_{C1}

$$\begin{aligned} 50 \sin(20t + 30^\circ) &= \\ &= 50 \cos(20t + 30^\circ - 90^\circ) \\ &= 50 \cos(20t - 60^\circ) \end{aligned}$$
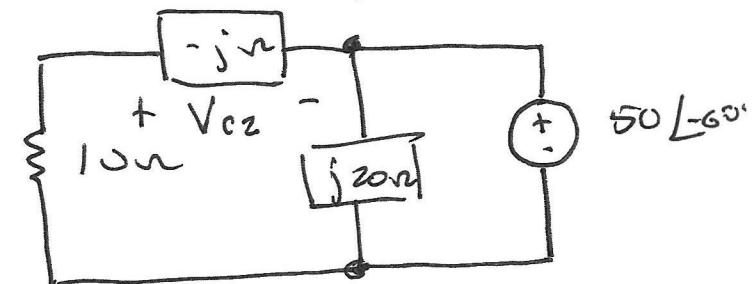
$$\begin{aligned} j\omega L &= j20 \Omega \\ \frac{1}{j\omega C} &= -j10 \Omega \end{aligned}$$





Solve for V_{C2}

$$\text{Then } V_C = V_{C1} + V_{C2}$$

$$= |V_{C1}| \cos(\omega t + \angle V_{C1})$$

$$+ |V_{C2}| \cos(2\omega t + \angle V_{C2})$$

To solve for V_{C_1} :

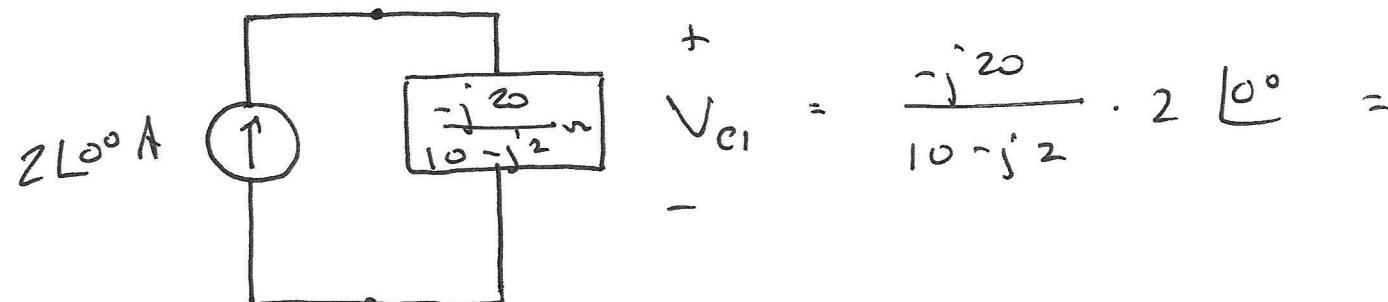
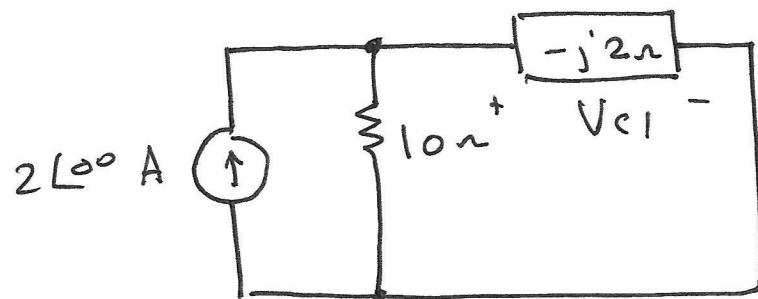


$$V_{C_1} = \frac{-j20}{10-j2} \cdot \frac{10+j2}{10+j2} 2\angle 0^\circ$$

$$= \frac{80-j400}{104} = \frac{10}{13} - j \frac{50}{13} \text{ V}$$


$$|V_{C_1}(t)| = \sqrt{\left(\frac{10}{13}\right)^2 + \left(\frac{50}{13}\right)^2} \quad \boxed{\tan^{-1}(-5)} \quad \checkmark$$

To solve for V_{C2} :

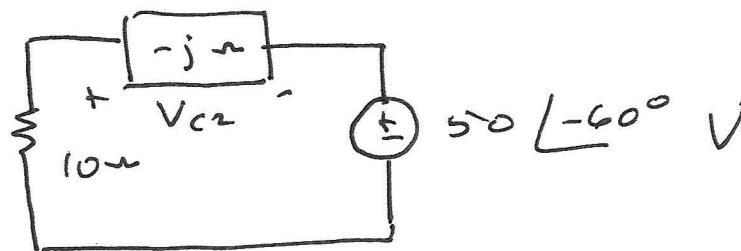
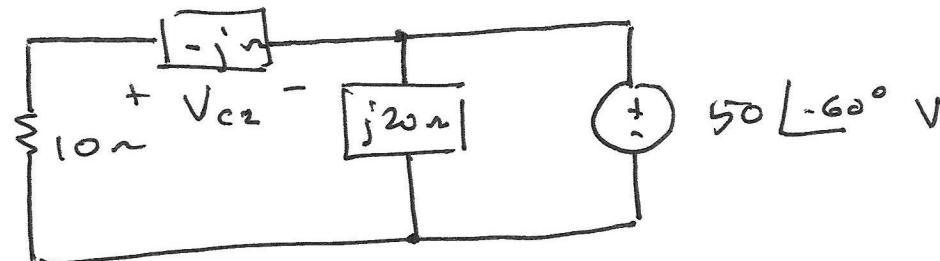


$$\begin{aligned}
 V_{C2} &= -\frac{-j1}{10-j} \cdot 50 \angle -60^\circ \\
 &= \frac{j \cdot 50 \angle -60^\circ}{10-j} \cdot \frac{10+j}{10+j} \\
 &= \frac{50 \angle -60^\circ (-1+j10)}{101}
 \end{aligned}$$

Complex Plane

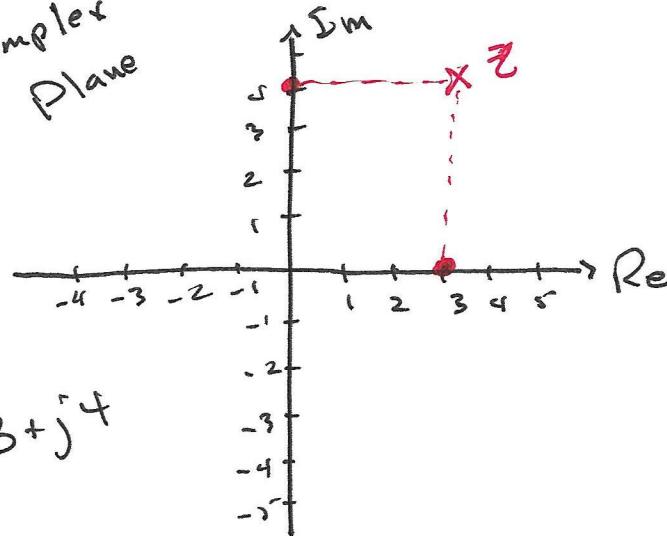

$$z = 3 + j4$$

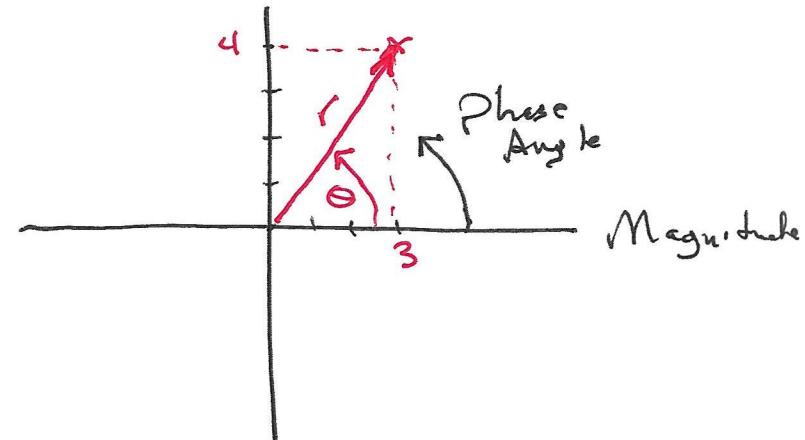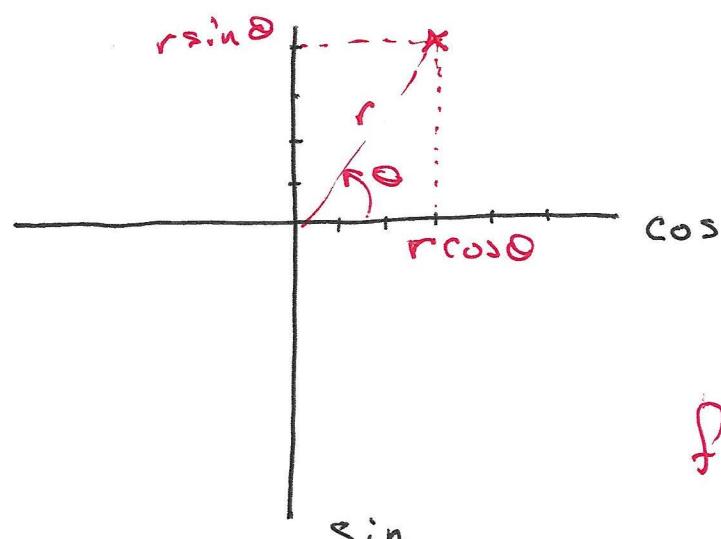

$$r = \sqrt{3^2 + 4^2}$$

$$= 5$$

$$\theta = \tan^{-1} \frac{4}{3}$$

$$= 53.13^\circ$$

$$z = 5 \angle 53.13^\circ$$

$$\begin{aligned}
 f(t) &= 5 \cos(10t + 53.13^\circ) \\
 &= 5 \cos(53.13^\circ) \cos 10t \\
 &\quad - 5 \sin(53.13^\circ) \sin 10t
 \end{aligned}$$