


For DC steady-state analysis


.OP

For AC steady-state analysis

.AC

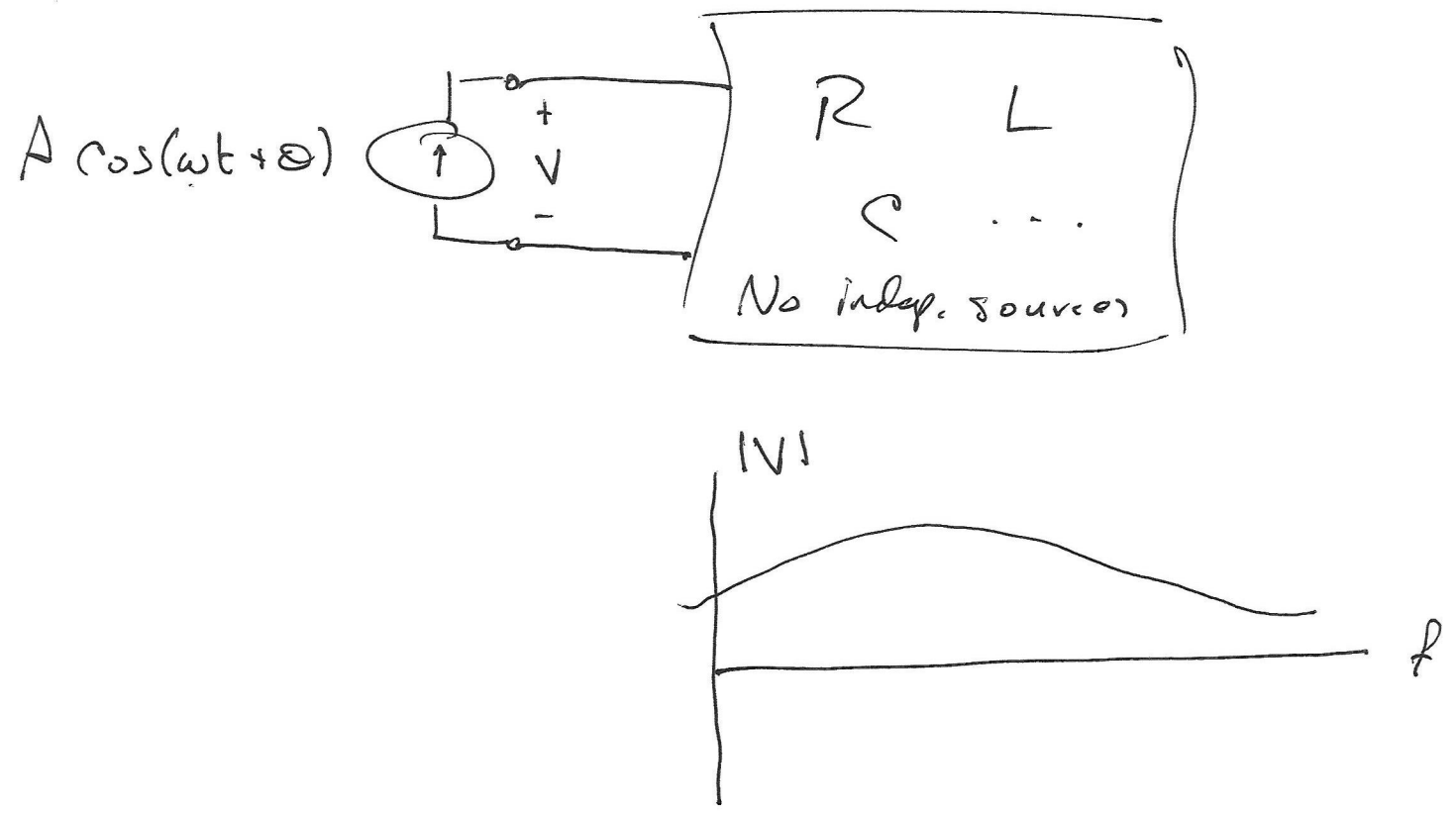
Make a plot of magnitude and phase angle of a transfer function or impedance vs. frequency.




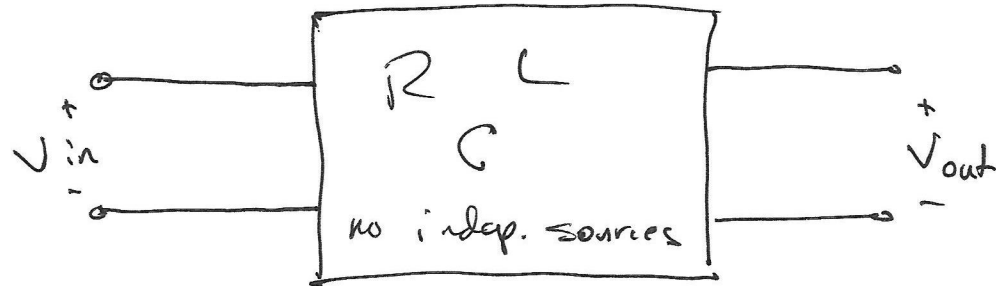

Define a transfer function

$$|H(\omega)| \triangleq \left| \frac{V_{out}}{V_{in}} \right|$$

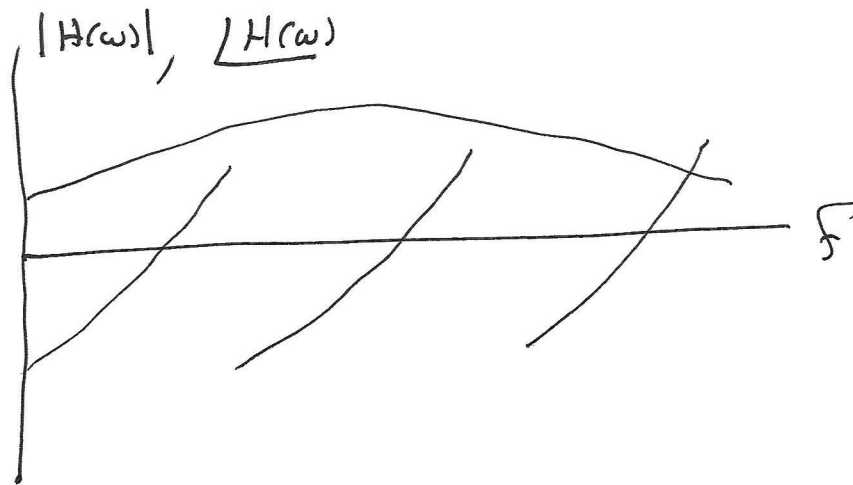

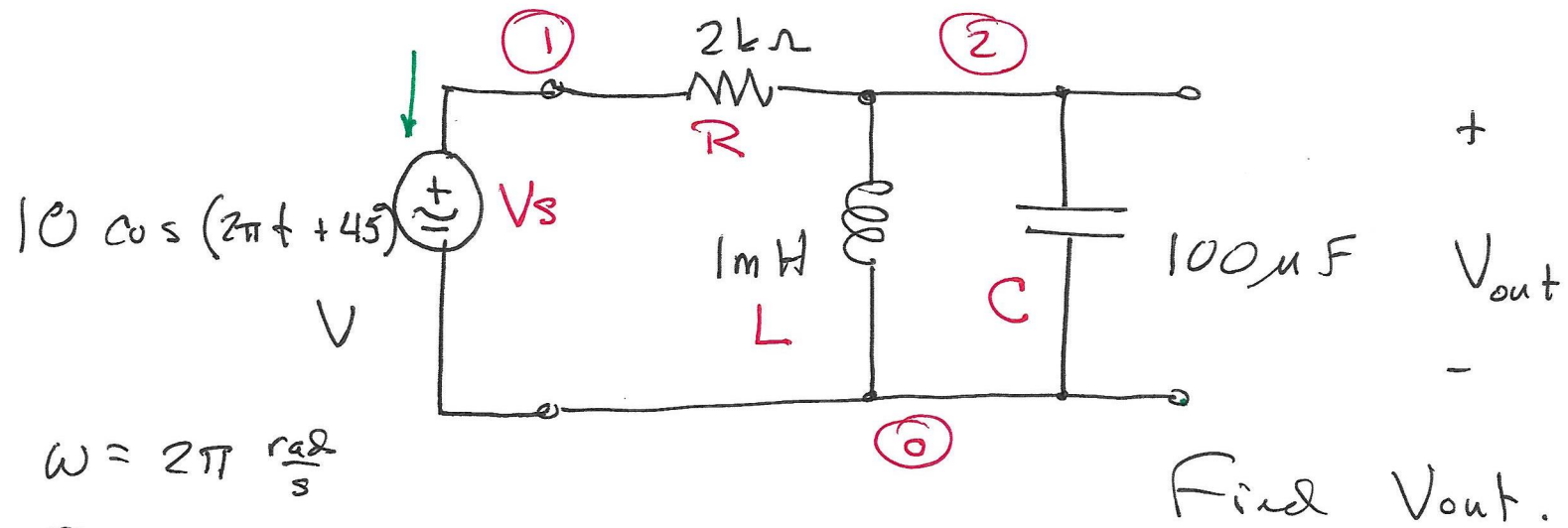

$$\omega = 2\pi \frac{\text{rad}}{\text{s}}$$

$$\theta = 45^\circ \text{ w.r.t. cosine}$$



# Title Line

Vs	1	0	AC
R	1	2	2k
L	2	0	1m
C	2	0	100u

magnitude  
 phase angle in degrees  
 not radians!

.AC LIN NP  
 .end

must be > 0  
 f<sub>end</sub> ≥ f<sub>start</sub>  
 frequency in Hz

number of points  
 total for a linear scale  
 number of points per decade on a DEC scale  
 " " " octave on an OCT scale

- LIN => linear
- DEC => decades
- OCT => octaves

1 1 1 1 1  
 10 points are 100  
 evenly spaced  
 logarithmic w.r.t. base 10  
 logarithmic w.r.t. base 2

$$\omega = 2\pi = 2\pi f \Rightarrow f = 1 \text{ Hz}$$

5

• AC LIN | | |


Output table will contain

voltage magnitude }  
" phase angle } for each node

current magnitude }  
" phase angle } for each indep. voltage source

Remember: All components are assumed  
to satisfy the P.S.C.

satisfies the P.S.C.

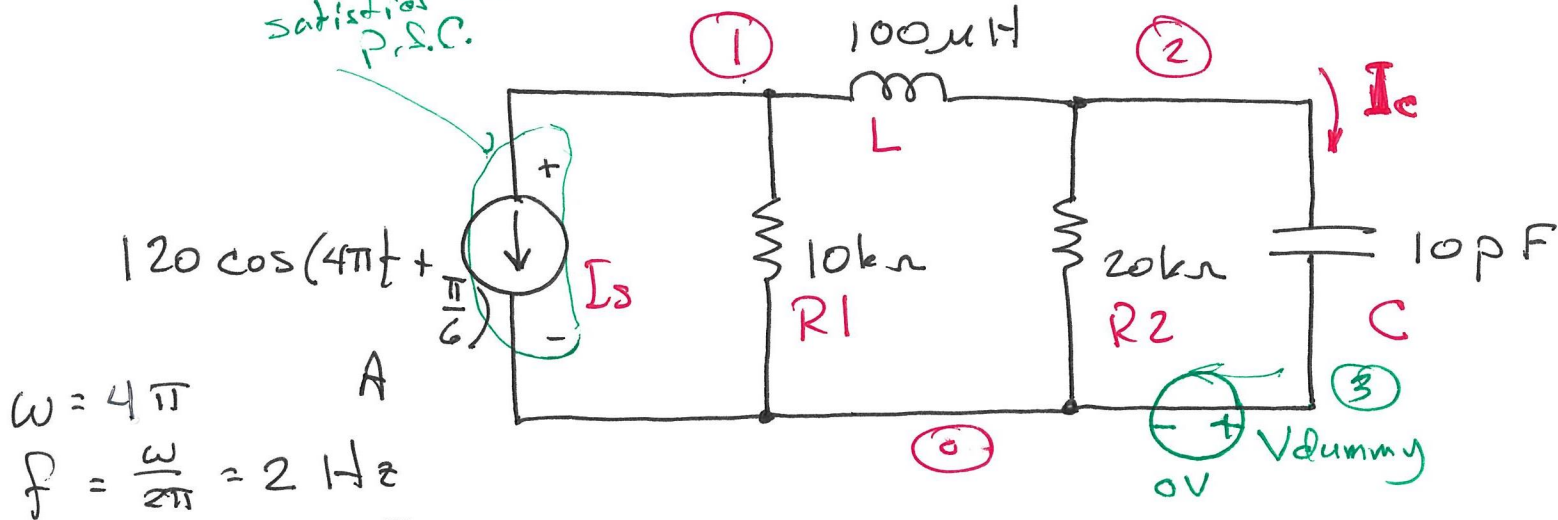

$\omega = 4\pi$   
 $f = \frac{\omega}{2\pi} = 2 \text{ Hz}$

Determine the current through the capacitor.  
 (magnitude and phase angle)

Title

Is	1	0	AC	120	30
R1	1	0	10k		
L	1	2	100u		
R2	2	0	20k		
C	2	3	10p		
Vdummy	3	0	DC	0	
.AC	LIN	1	2	2	
.end					

Phase angle is always degrees