

### Summing Amplifier

$$V_o = \frac{1}{10} (V_{in} + V_1 - V_2)$$

$$V_x = V_{in} - \frac{1}{2} V_2$$

$$V_y = V_1 - \frac{1}{2} V_2$$

$$I_y = \frac{V_y}{100k\Omega}$$

$$I_x = \frac{V_x}{100k\Omega}$$

$$I_z = I_x + I_y = \frac{V_x}{100k\Omega} + \frac{V_y}{100k\Omega}$$


$$= \frac{V_{in} - \frac{1}{2} V_2}{100k\Omega} + \frac{V_1 - \frac{1}{2} V_2}{100k\Omega}$$

$$= \frac{V_{in} + V_1 - V_2}{100k\Omega}$$

$$V_2 = 10k\Omega (I_z) = \frac{1}{10} (V_{in} + V_1 - V_2)$$



# Integrator

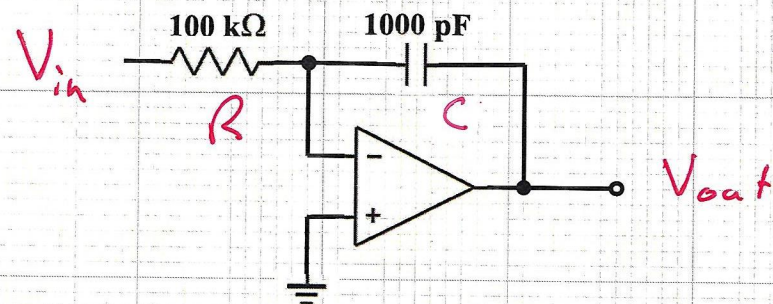

$$V_{out} = -\frac{1}{RC} \int V_{in} dt$$

$$V_{out} = -\frac{1}{RC} \cdot \frac{1}{j\omega} V_{in}$$


phasor  
notation

$$\text{let } s = j\omega$$

$$V_{out} = -\frac{1}{sRC} V_{in}$$

$$V_{in} = -sRC V_{out}$$


Integrator

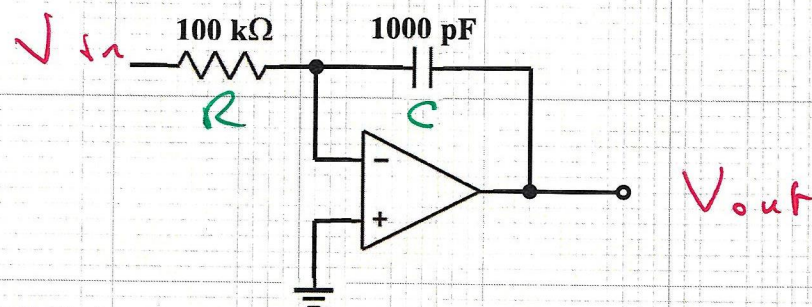

$$V_{in} = -sRC V_{out}$$
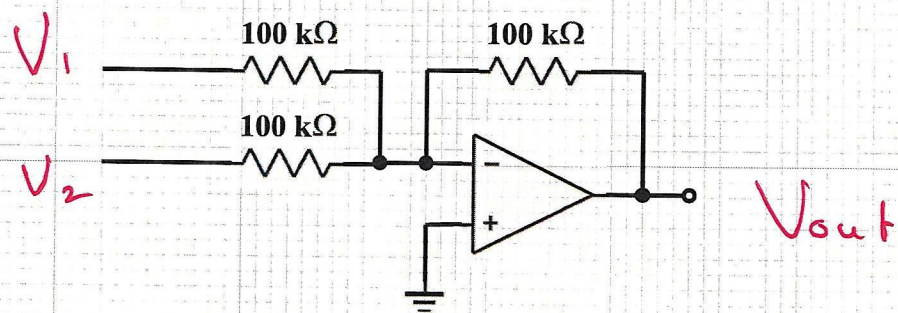
$$\text{or } V_{out} = -\frac{1}{sRC} V_{in}$$





$$V_{out} = -V_1 - V_2$$



$$V_{out,4} = -V_{out,3} - V_{out,1}$$

$$V_{out,2} = -sRC V_{out,3}$$

$$V_{out,1} = -sRC V_{out,2}$$

$$V_{out,1} = \frac{1}{10} (V_{in} + V_{out,3} - V_{out,2})$$

$$V_{out,1} = \frac{1}{10} \left\{ V_{in} - \frac{1}{sRC} V_{out,2} - \frac{1}{sRC} V_{out,1} \right\}$$

$\uparrow$   
 $-\frac{1}{sRC} V_{out,1}$

$$10 V_{out,1} = V_{in} + \frac{1}{s^2 R^2 C^2} V_{out,1} - \frac{1}{sRC} V_{out,1}$$

Multiply through by  $s^2 R^2 C^2$


$$10 s^2 R^2 C^2 V_{out,1} = s^2 R^2 C^2 V_{in} + V_{out,1} - sRC$$

$$s^2 R^2 C^2 V_{in} = (1 - sRC - 10 s^2 R^2 C^2) V_{out,1}$$





$$\frac{V_{out,1}}{V_{in}} = \frac{s^2 R^2 C^2}{1 - sRC - 10 s^2 R^2 C^2}$$


$$\lim_{\omega \rightarrow 0} \frac{V_{out,1}}{V_{in}} = \frac{0}{1} = 0$$

$$\lim_{\omega \rightarrow \infty} \left| \frac{V_{out,1}}{V_{in}} \right| = \frac{1}{10}$$

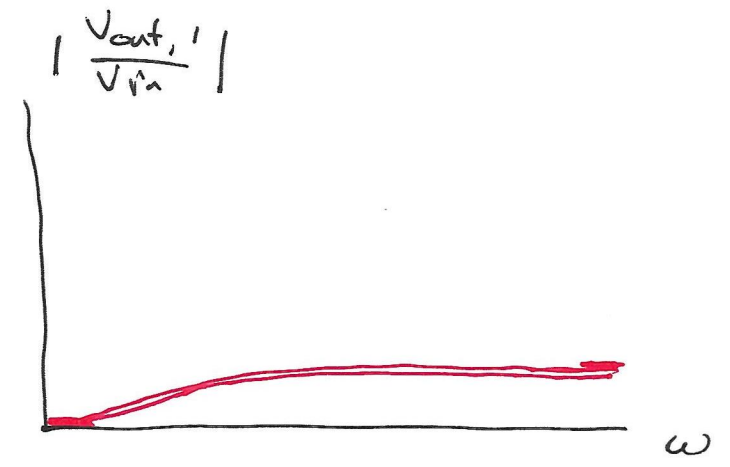



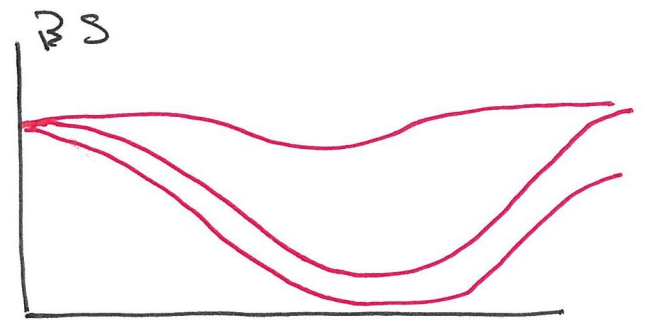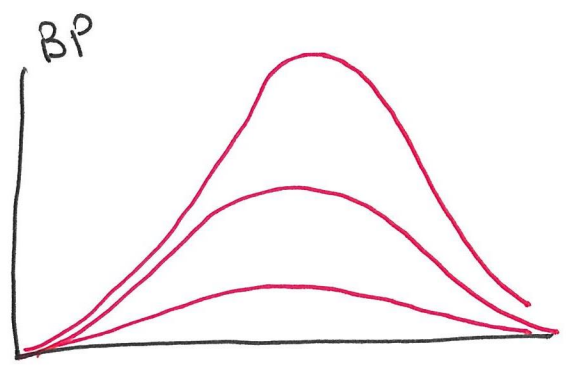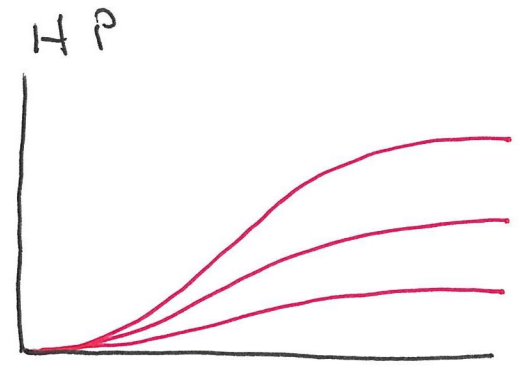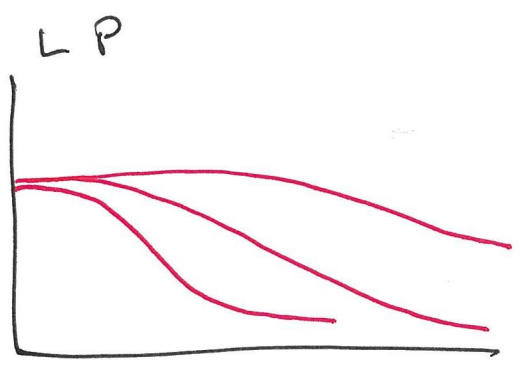

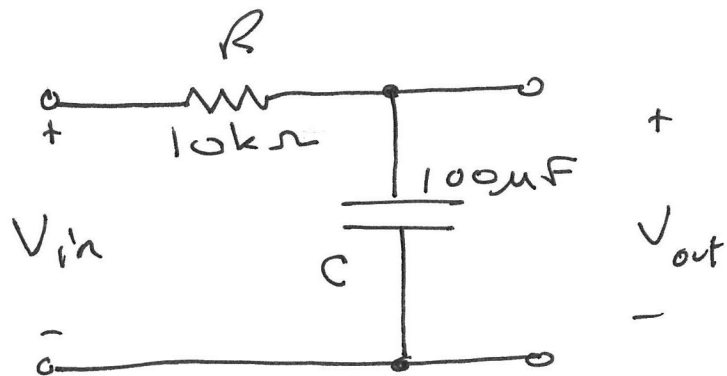


$$H(\omega) = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC}$$

$$\lim_{\omega \rightarrow 0} H(\omega) = 1$$

$$\lim_{\omega \rightarrow \infty} H(\omega) = 0$$

$$\frac{A}{\sqrt{2}}$$

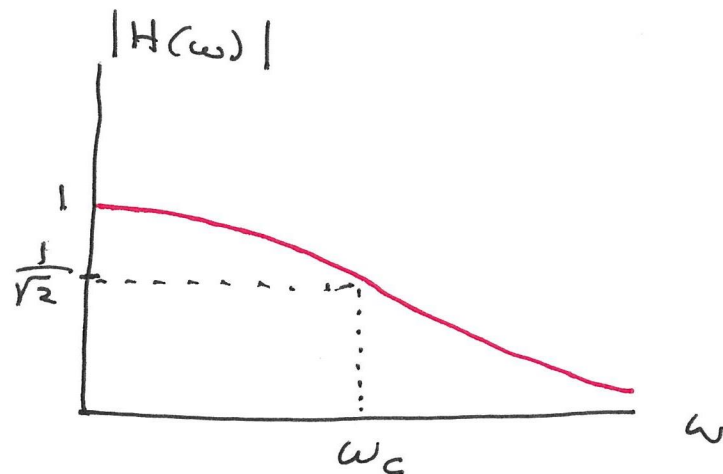



$$|H(\omega)| = \frac{1}{\sqrt{1^2 + (\omega RC)^2}}$$

At the cutoff frequency

$$|H(\omega_c)| = \frac{|H(\omega)|}{\sqrt{2}} = \frac{1}{\sqrt{2}}$$

$$|H(\omega_c)| = \frac{1}{\sqrt{1^2 + (\omega_c RC)^2}} = \frac{1}{\sqrt{2}}$$


$$\frac{1}{1^2 + (\omega_c RC)^2} = \frac{1}{2}$$

$$\text{or } 1 + (\omega_c RC)^2 = 2$$


$$(\omega_c RC)^2 = 1$$

$$\omega_c = \frac{1}{RC}$$


Given

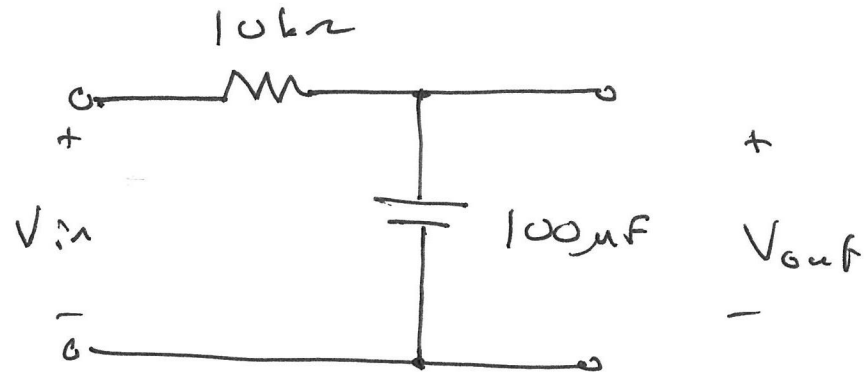

$$\omega_c = \frac{1}{RC} = 1$$

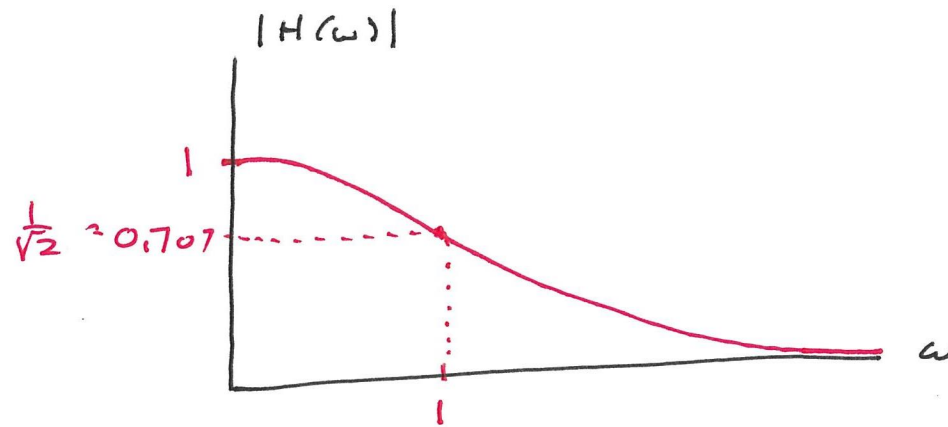




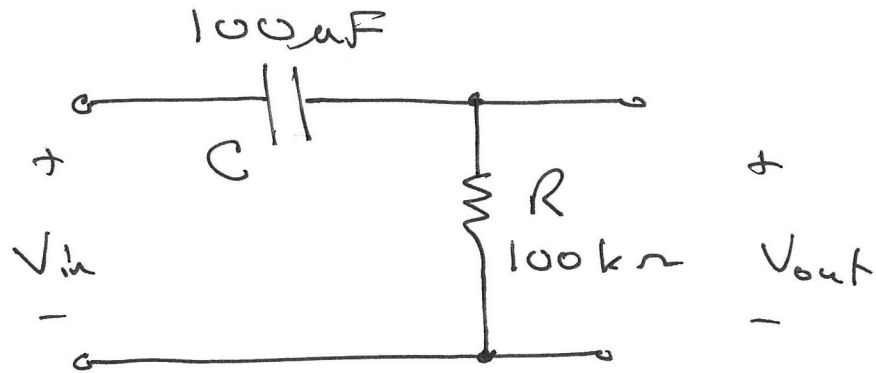

$$H(\omega) = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega RC}{1 + j\omega RC}$$

$$\lim_{\omega \rightarrow 0} H(\omega) = \frac{0}{1} = 0$$
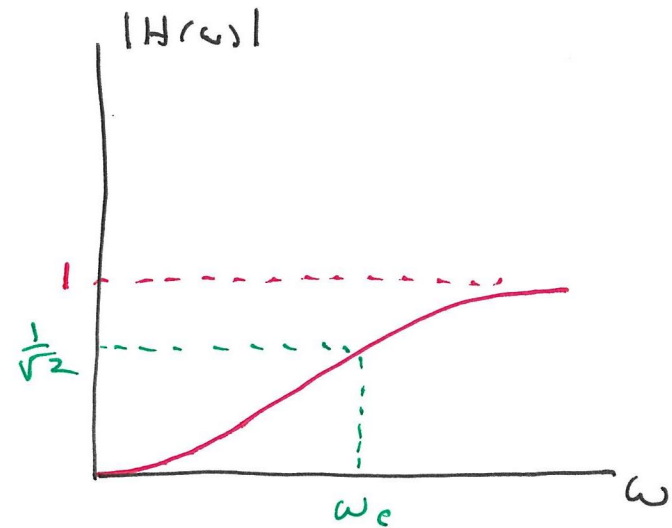
$$\lim_{\omega \rightarrow \infty} H(\omega) = 1$$



$$|H(\omega)| = \frac{\omega RC}{\sqrt{1^2 + (\omega RC)^2}}$$

At cutoff

$$|H(\omega_c)| = \frac{\omega_c RC}{\sqrt{1^2 + (\omega_c RC)^2}} = \frac{1}{\sqrt{2}}$$

$$\frac{(\omega_c RC)^2}{1^2 + (\omega_c RC)^2} = \frac{1}{2}$$


$$2(\omega_c RC)^2 = 1 + (\omega_c RC)^2$$

$$1 = (\omega_c RC)^2$$

$$\omega_c = \frac{1}{RC}$$



For BP

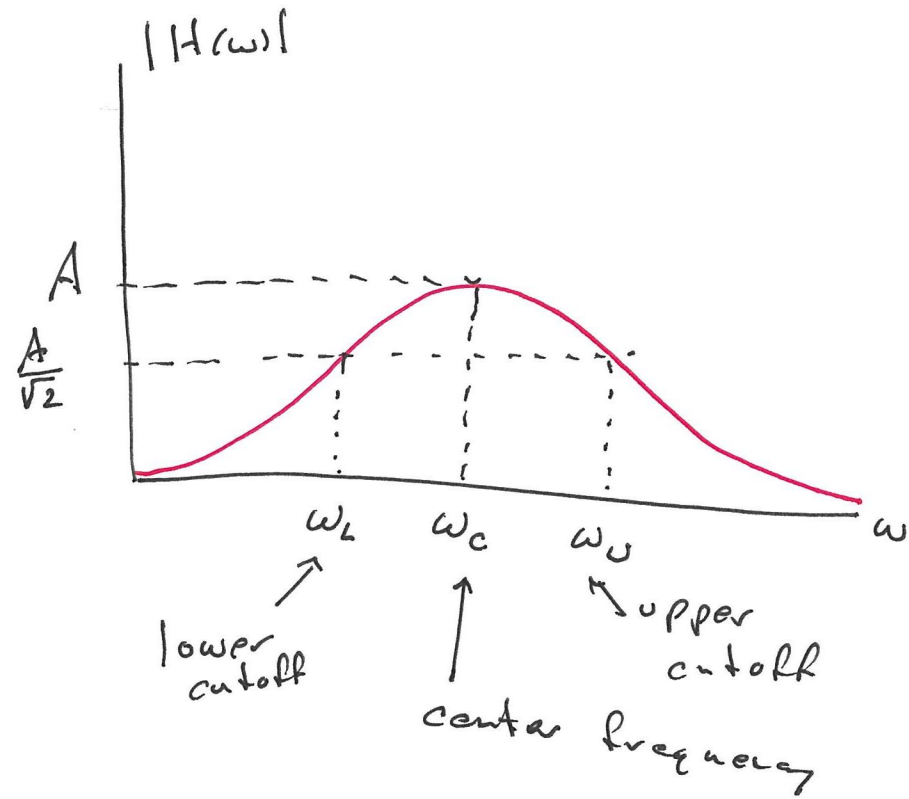

For BS

