

$$\dot{i}_C = C \dot{v}_C$$

$$v_R = R \dot{i}_C = RC \dot{v}_C$$

KVL:  $v_R + v_C = v$

$$RC \dot{v}_C + v_C = v$$

$$\dot{v}_C + \frac{1}{RC} v_C = \frac{V_s}{RC}$$

$$v_C(t) = K_1 e^{\alpha t} + K_2$$

$$\frac{1}{RC} K_2 = \frac{V_s}{RC}$$

$$K_2 = V_s$$

$$v_C(t) = K_1 e^{\alpha t} + V_s$$

$$\alpha K_1 e^{\alpha t} + 0 + \frac{1}{RC} K_1 e^{\alpha t} + \cancel{\frac{1}{RC} V_s} = \cancel{\frac{V_s}{RC}}$$

$$\alpha \cancel{K_1} e^{\alpha t} + \frac{1}{RC} \cancel{K_1} e^{\alpha t} = 0$$

$$\alpha + \frac{1}{RC} = 0$$

$$\Rightarrow \alpha = -\frac{1}{RC}$$

$$v_c(t) = K_1 e^{-\frac{1}{RC} t} + V_s$$

$$v_c(t_0) = 0$$

$$\text{Let } t_0 = 0$$

$$v_c(0) = 0$$


$$v_c(0) = K_1 e^{\cancel{0}} + V_s$$

$$= K_1 + V_s = 0 \Rightarrow K_1 = -V_s$$




$$\boxed{v_c(t) = -V_s e^{-\frac{1}{RC} t} + V_s \text{ for } t \geq 0}$$


The time at which  $e^{-\frac{t}{RC}} = e^{-1}$  is called  
the time constant

$$\tau = RC$$

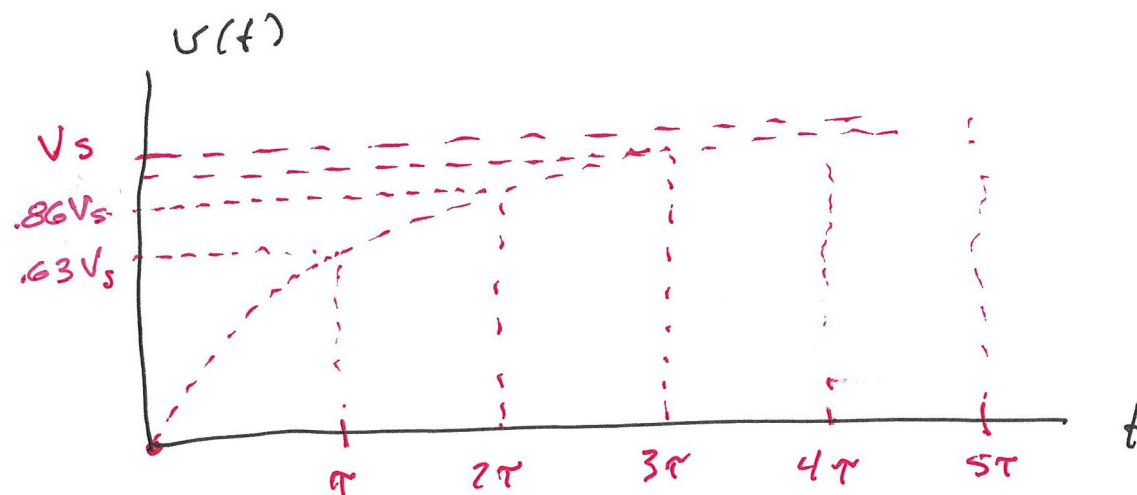

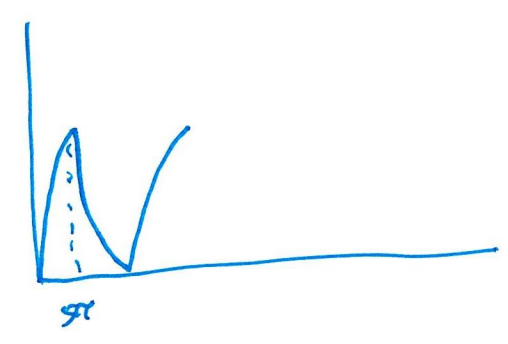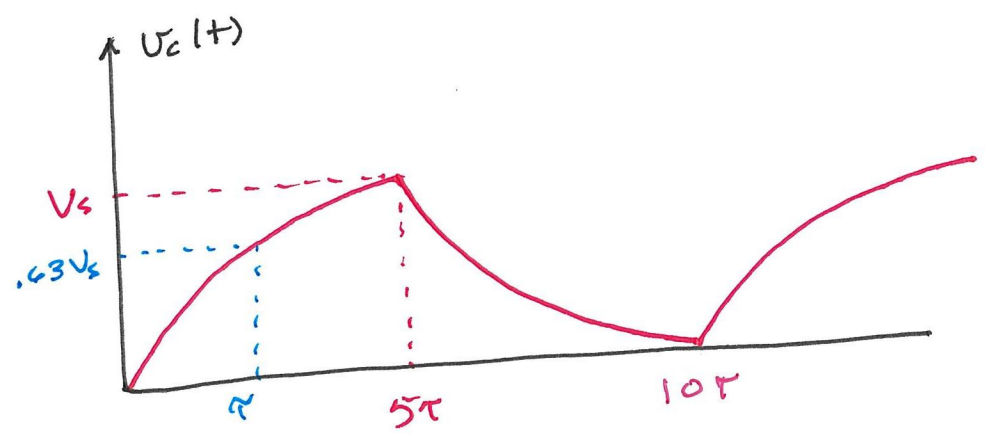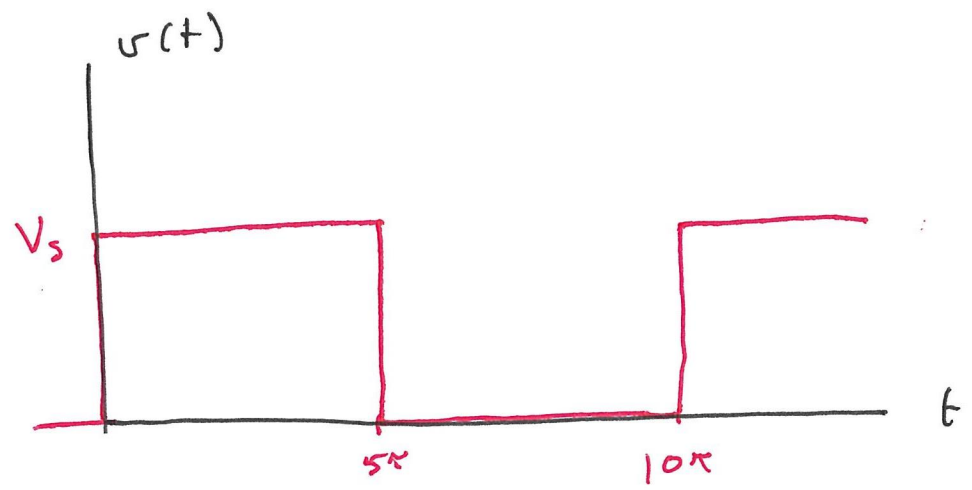Rule of Thumb:  
The signal has  
reached its final  
value when  
 $t = 5\tau$ .




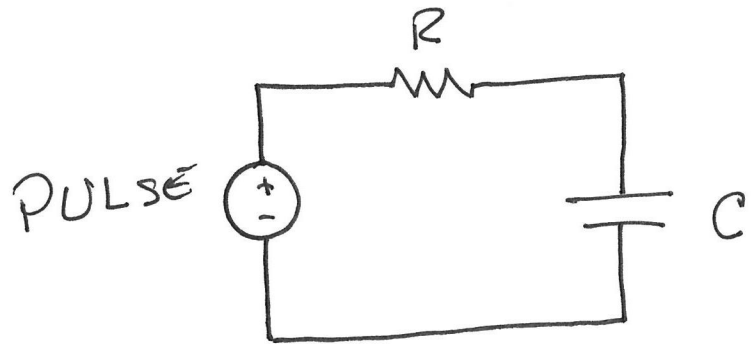

PULSE ( )

.TRAN 50m

# Pulse Waveform

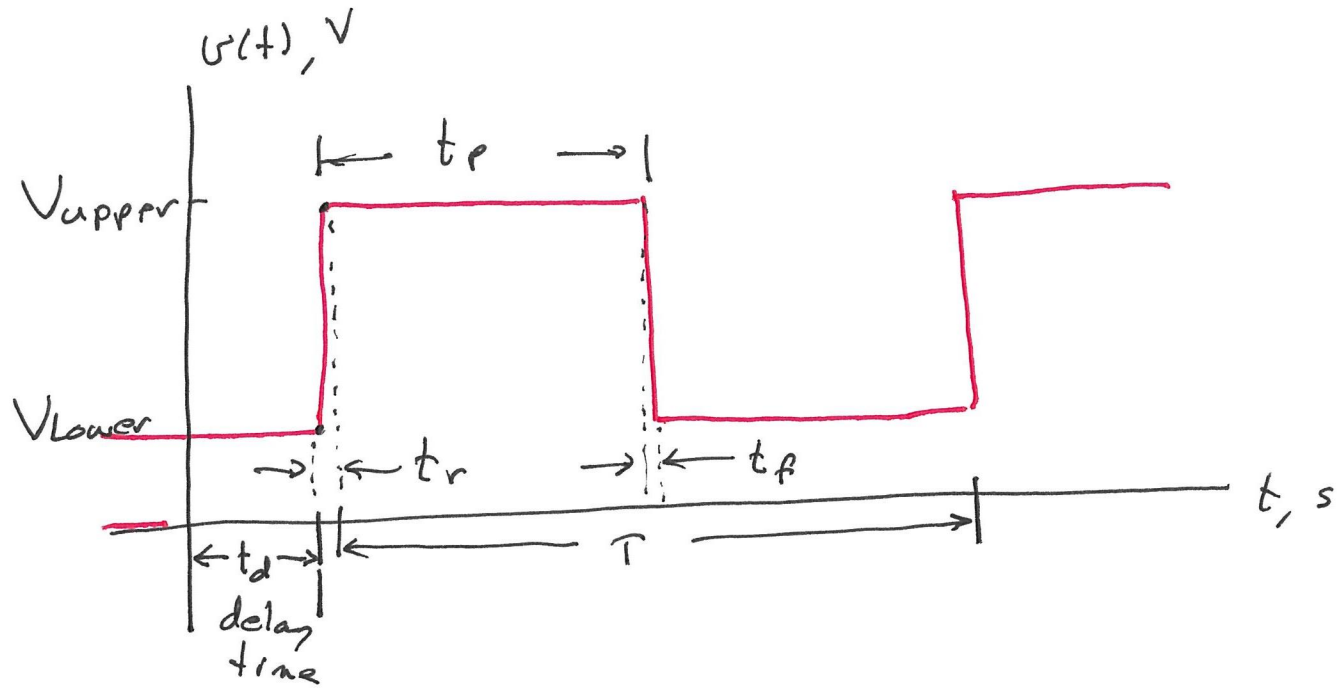

$V_{lower}$

$V_{upper}$

$t_d$  delay time

$t_r$  rise time


$t_f$  fall time

$t_p$  pulse width

$T$  period

For an RC circuit,  $\tau = RC$  seconds

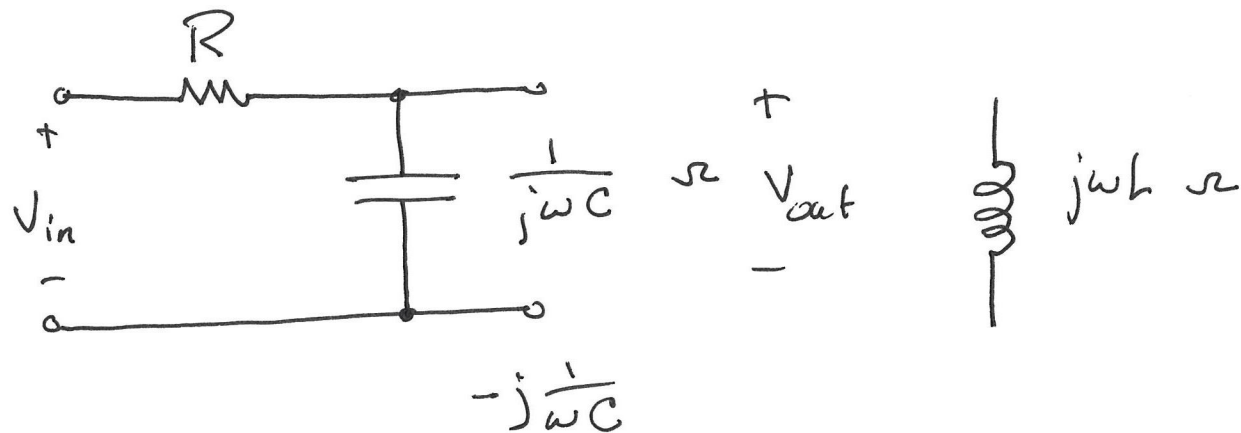For an RL circuit,  $\tau = L/R$  seconds



$$V_{out} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} V_{in} \cdot \frac{j\omega L}{j\omega C}$$

$$= \frac{1}{j\omega RC + 1} V_{in}$$



$$\frac{V_{out}}{V_{in}} = \frac{1}{j\omega RC + 1} \quad \text{is called the transfer function}$$


$$H(\omega) \stackrel{\Delta}{=} \frac{V_{out}}{V_{in}}$$

phasor rep. for  $V_{out}$   
 phasor rep. for  $V_{in}$

$$|H(\omega)| = \frac{|1|}{|j\omega RC + 1|} = \frac{1}{\sqrt{(1)^2 + (\omega RC)^2}}$$

$$\lim_{\omega \rightarrow 0} |H(\omega)| = \frac{1}{\sqrt{1^2}} = 1$$

$$\lim_{\omega \rightarrow \infty} |H(\omega)| = \frac{1}{\sqrt{(\omega RC)^2}} = \frac{1}{\omega RC} = 0$$

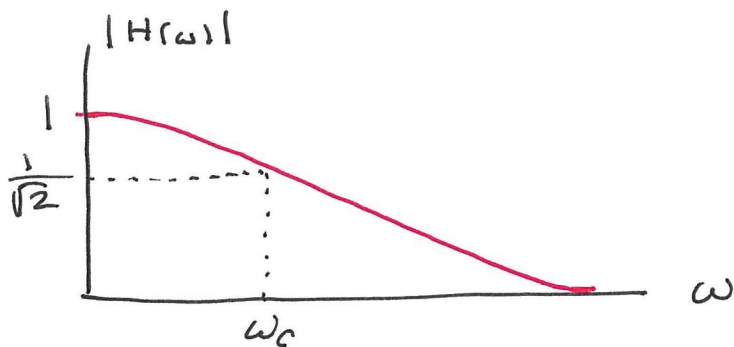


Low Pass  
filter

Phase angle of  $H(\omega)$

$$\angle H(\omega) = \angle 1 - \angle j\omega RC + 1$$

$$\angle 1 = 0^\circ$$

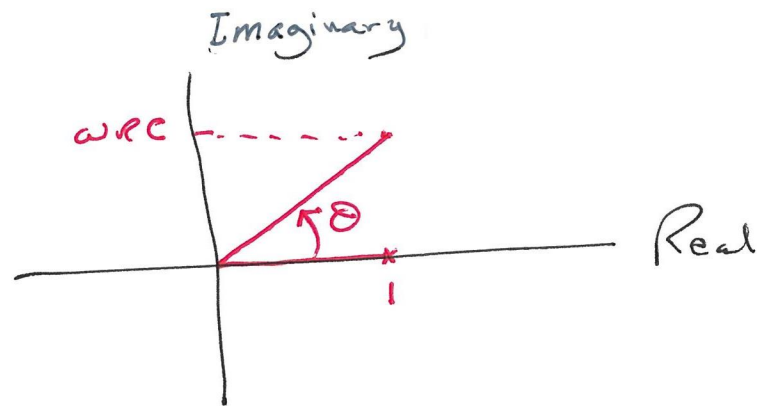

$$\angle j\omega RC + 1 = \tan^{-1} \frac{\omega RC}{1} = \tan^{-1} \omega RC$$

$$\angle H(\omega) = -\tan^{-1} \omega RC$$

$$\lim_{\omega \rightarrow 0} \angle H(\omega) = -\tan^{-1} 0 = 0$$

$$\lim_{\omega \rightarrow \infty} \angle H(\omega) = -\tan^{-1} \infty = -90^\circ$$

