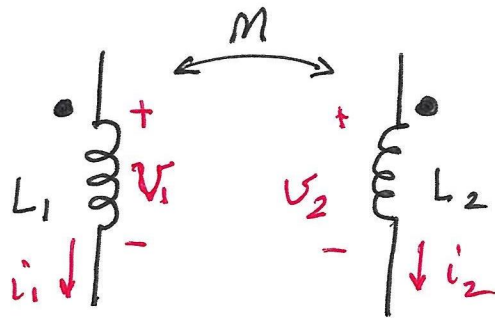


Mutual Inductance



L_1 and L_2 are called self inductance.

M is called mutual inductance

$$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$
$$V_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$




In AC notation:


$$V_1 = j\omega L_1 I_1 + j\omega M I_2$$

$$V_2 = j\omega M I_1 + j\omega L_2 I_2$$

due to mutual coupling

self-induced

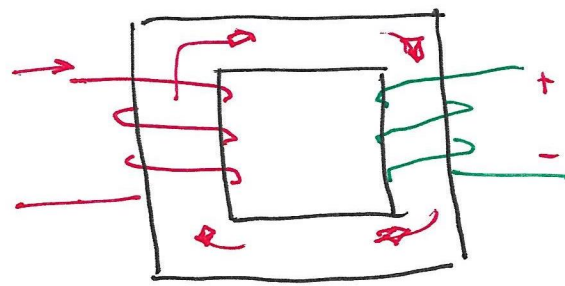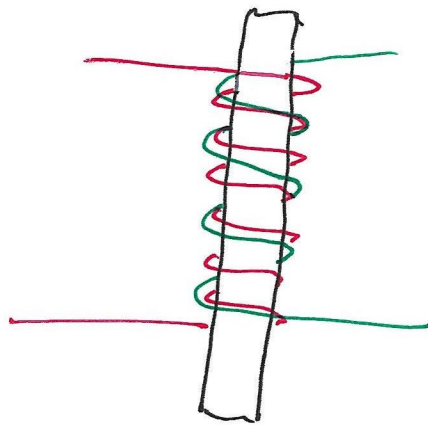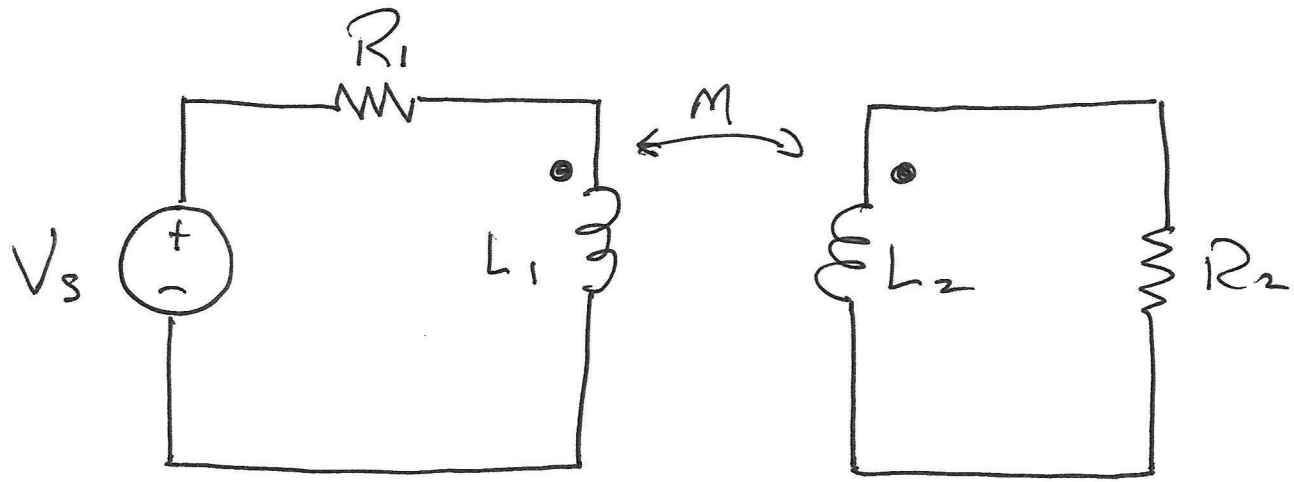

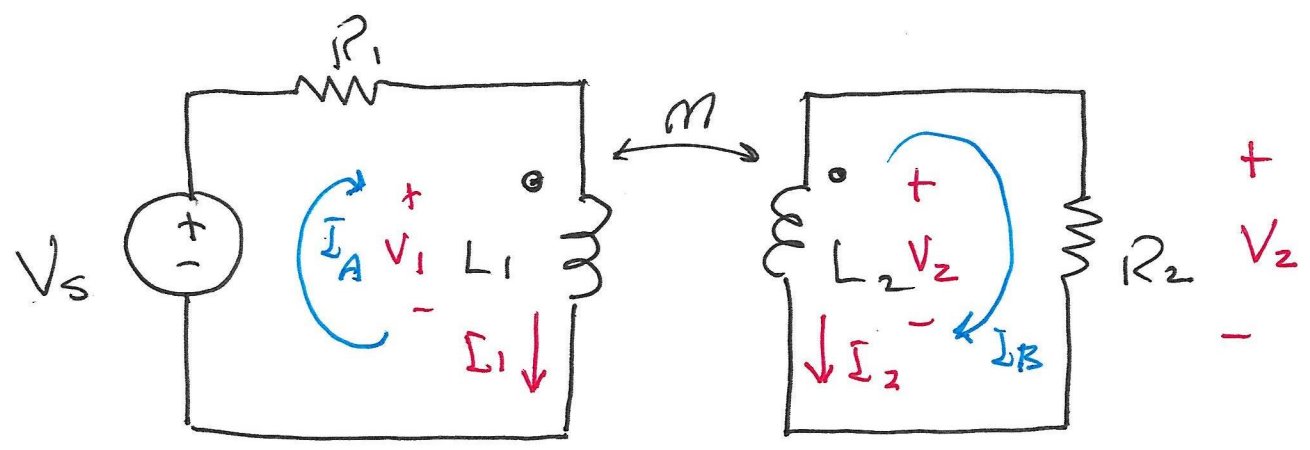

$$V_1 = j\omega L_1 \cancel{I_A} - j\omega M \cancel{I_B}$$

$$V_2 = j\omega M \cancel{I_A} - j\omega L_2 \cancel{I_B}$$

$$V_1 = j\omega L_1 I_A - j\omega M I_B$$

$$V_2 = j\omega M I_A - j\omega L_2 I_B$$

For loop A :

$$-V_s + R_1 I_A + V_1 = 0 \quad (1)$$

For loop B :

$$-V_2 + R_2 I_B = 0 \quad (2)$$

$$(1) \Rightarrow -V_s + R_1 I_A + j\omega L_1 I_A - j\omega M I_B = 0$$

$$(2) \Rightarrow -j\omega M I_A + j\omega L_2 I_B + R_2 I_B = 0$$



In matrix form :

$$\begin{bmatrix} R_1 + j\omega L_1 & -j\omega M \\ -j\omega M & R_2 + j\omega L_2 \end{bmatrix} \begin{bmatrix} I_A \\ I_B \end{bmatrix} = \begin{bmatrix} V_s \\ 0 \end{bmatrix}$$

Solve for I_B :

$$\begin{aligned} I_B &= \frac{\begin{vmatrix} R_1 + j\omega L_1 & V_s \\ -j\omega M & 0 \end{vmatrix}}{\begin{vmatrix} R_1 + j\omega L_1 & -j\omega M \\ -j\omega M & R_2 + j\omega L_2 \end{vmatrix}} = \frac{j\omega M V_s}{(R_1 + j\omega L_1)(R_2 + j\omega L_2) - (-j\omega M)(-j\omega M)} \\ &= \frac{j\omega M V_s}{R_1 R_2 + j\omega R_1 L_2 + j\omega L_1 R_2 - \omega^2 L_1 L_2 + \omega^2 M^2} \\ &= \frac{j\omega M V_s}{(R_1 R_2 - \omega^2 L_1 L_2 + \omega^2 M^2) + j\omega (R_1 L_2 + L_1 R_2)} \end{aligned}$$


Then $V_2 = R_2 I_B$

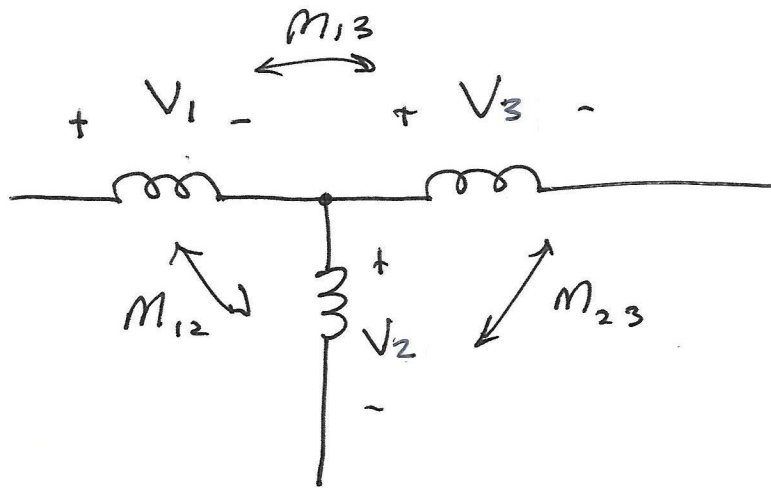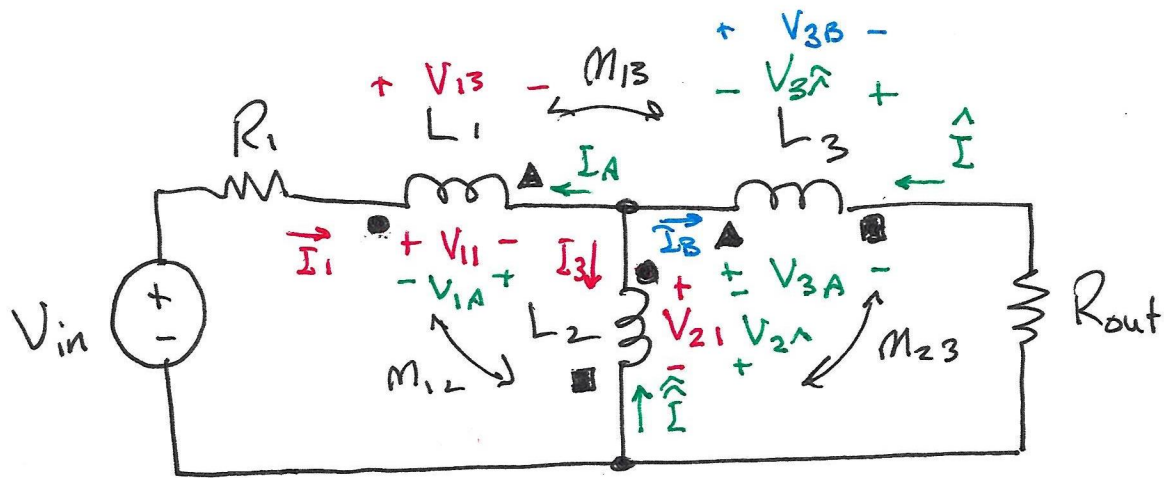

$$V_1 = V_{13} + V_{11} - V_{1A}$$

$$V_3 = V_{3B} - V_{3A} + V_{3A}$$


$$V_2 = V_{21} - V_{2A} + V_{23}$$

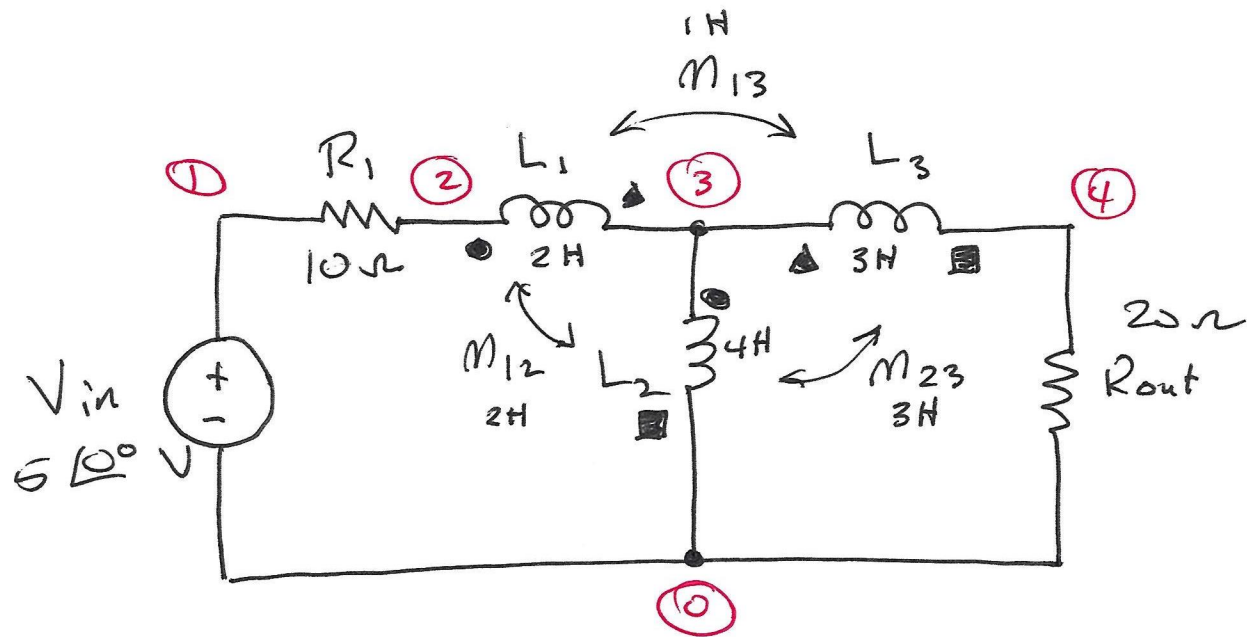

$$k_{12} = \frac{2}{\sqrt{4 \cdot 2}} = \frac{2}{\sqrt{8}} \approx 0.707$$

$$k_{13} = \frac{1}{\sqrt{2 \cdot 3}} = \frac{1}{\sqrt{6}}$$
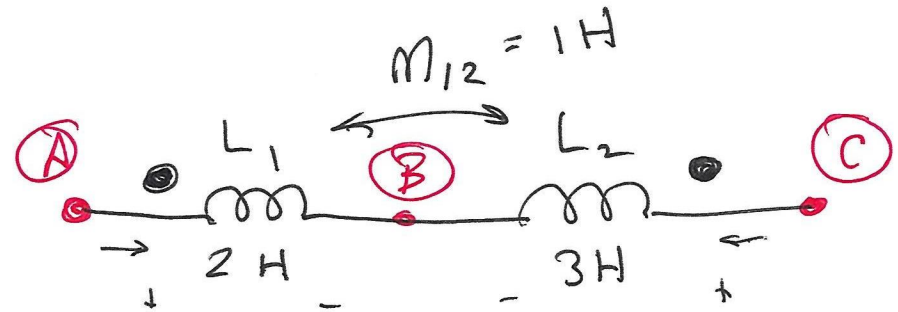
$$k_{23} = \frac{3}{\sqrt{4 \cdot 3}} = \frac{3}{2\sqrt{3}} \approx 0.87$$



L1	A	B	2
L2	C	B	3
k12	L1	L2	.4

Coupling coefficient

$$k = \frac{M_{12}}{\sqrt{L_1 L_2}}$$

Perfect coupling: $k = 1$
 Real circuits: $0 < k < 1$

$$k_{12} = \frac{1}{\sqrt{2 \cdot 3}} = \frac{1}{\sqrt{6}} \approx 0.4$$

Vin

R1

Rout

L1 2 3 2

L2 3 0 4


k12 L1 L2 .707

L3 3 4 3

k13 L1 L3 .4

k23 L2 L3 .87


.AC

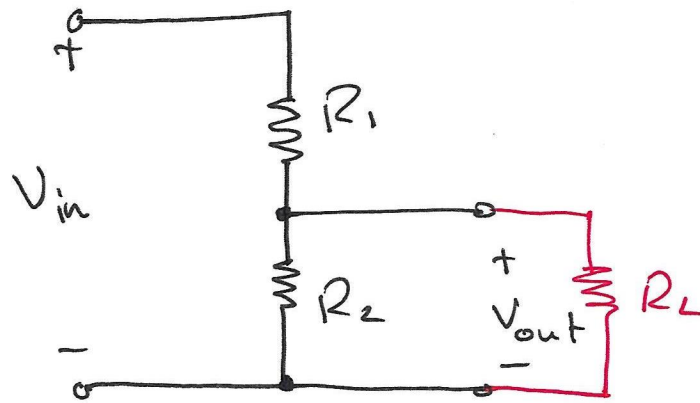

$$H = \frac{V_{out}}{V_{in}} = \frac{R_2}{R_1 + R_2}$$

$$H_{new} = \frac{V_{out}}{V_{in}} = \frac{R_2 \parallel R_L}{R_1 + R_2 \parallel R_L}$$


Two-port network description:

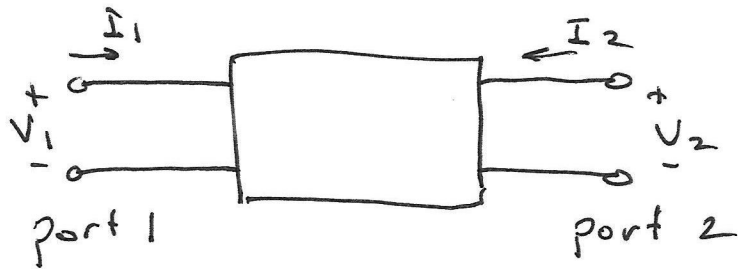

Impedance Parameters:

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

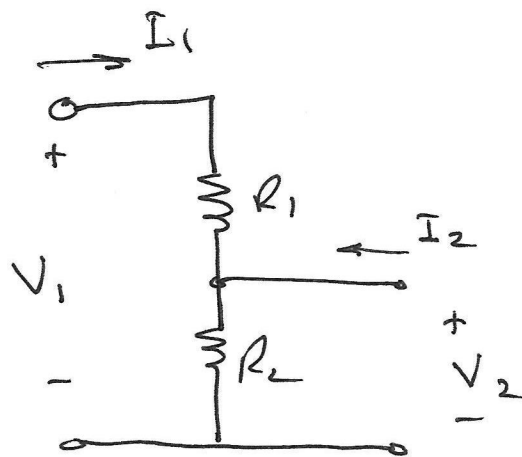


Determine Z_{11} , Z_{12} , Z_{21} , Z_{22}

where

$$V_1 = \textcircled{Z_{11}} I_1 + Z_{12} I_2$$

$$V_2 = \textcircled{Z_{21}} I_1 + Z_{22} I_2$$

If $I_2 = 0$:

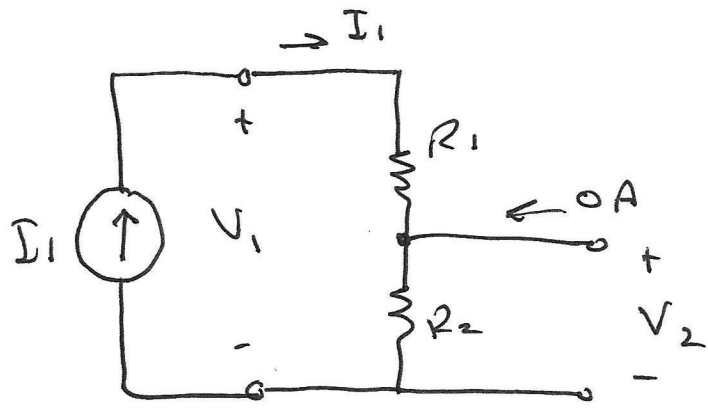

$$V_1 = Z_{11} I_1$$


$$= (R_1 + R_2) I_1$$

$$V_2 = R_2 I_1$$

$$Z_{11} = R_1 + R_2$$

$$Z_{21} = R_2$$

If $I_1 = 0$:

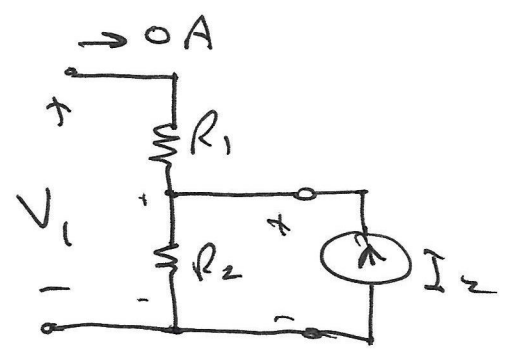

$$V_1 = Z_{12} I_2 =$$

$$V_2 = Z_{22} I_2 = R_2 I_2$$

↑
 Z_{22}