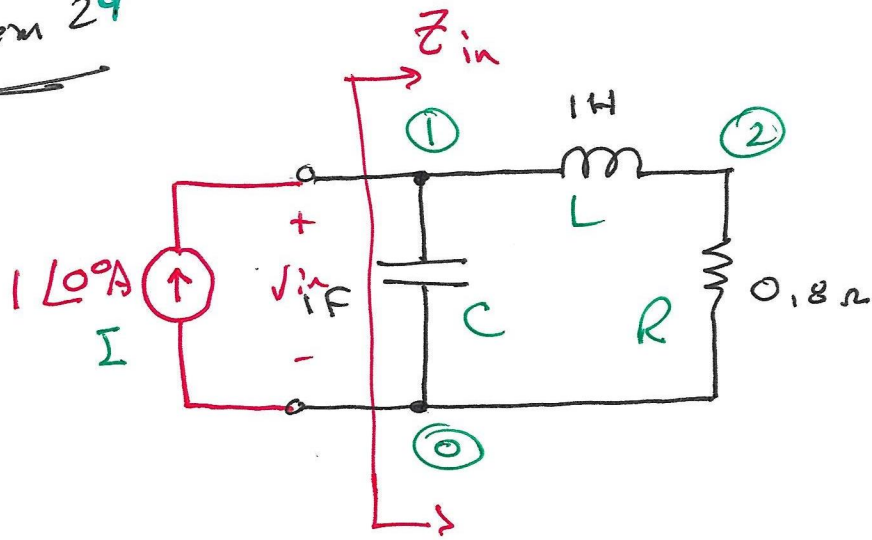


Problem 29



$$V_{in} = Z_{in} (1 \angle 0^\circ) = Z_{in}$$

Title

L 1 2 1

C 1 0 1

R 2 0 0.8


I 0 1 AC 1 0

.AC LIN 1000 1 100


.end

2nd choice:

.AC DFC 100 1 1G

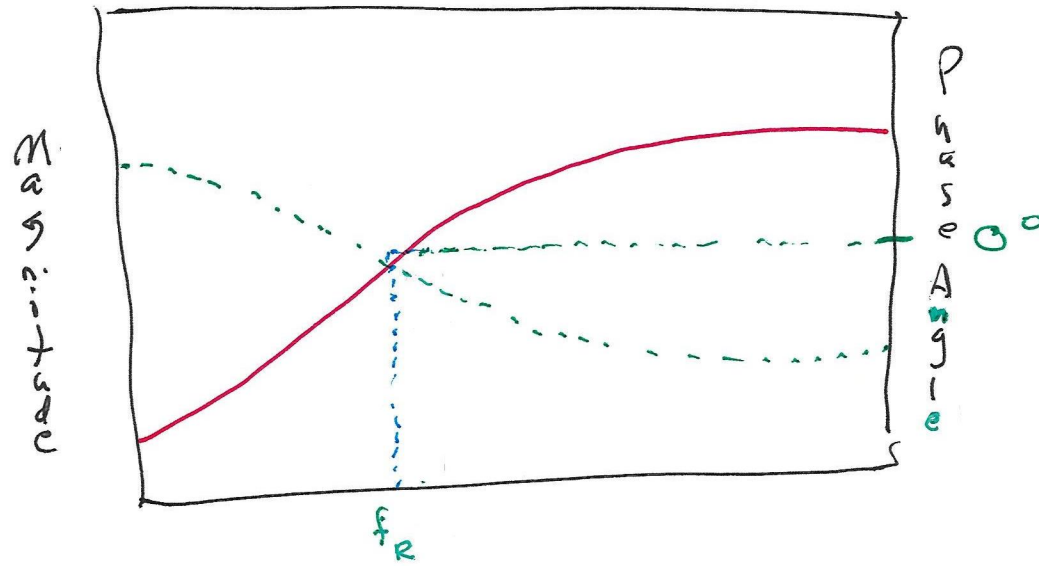

$$\omega_R = 2\pi f_R$$

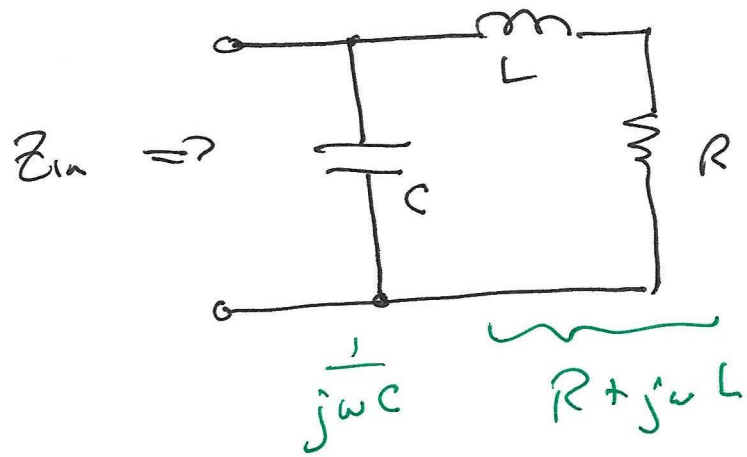

$$Z_{in} = \frac{\frac{1}{j\omega C} (R + j\omega L)}{\frac{1}{j\omega C} + R + j\omega L} = \frac{R + j\omega L}{1 + j\omega RC - \omega^2 LC}$$

$$= \frac{R + j\omega L}{(1 - \omega^2 LC) + j\omega RC} \cdot \frac{(1 - \omega^2 LC) - j\omega RC}{(1 - \omega^2 LC) - j\omega RC}$$

$$= \frac{R(1 - \omega^2 LC) + j\omega L(1 - \omega^2 LC) - j\omega R^2 C + \omega^2 RLC}{(1 - \omega^2 LC)^2 + (\omega RC)^2}$$

At resonance, the imaginary part of the numerator is zero.

$$\cancel{\omega} L (1 - \omega^2 L C) - \cancel{\omega} R^2 C = 0$$

$$L - \omega^2 L^2 C - R^2 C = 0$$

$$\omega^2 L^2 C = L - R^2 C$$

$$\omega^2 = \frac{L - R^2 C}{L^2 C}$$


$$\omega_R = \sqrt{\frac{L - R^2 C}{L^2 C}}$$

$$= \sqrt{\frac{1 - 0.64}{1}}$$

$$= \sqrt{.36}$$


$$= .6$$

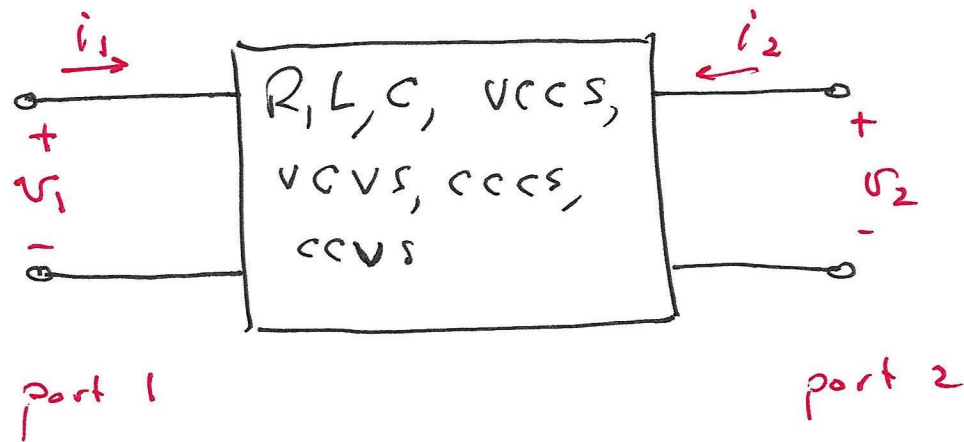Impedance Parameters for a Two-Port Network 5



$$v_1 = z_{11} i_1 + z_{12} i_2$$

$$v_2 = z_{21} i_1 + z_{22} i_2$$

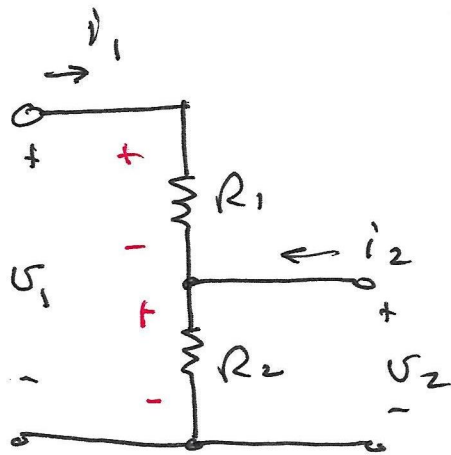

$$U_1 = Z_{11} i_1 + Z_{12} i_2$$

$$Z_{11} = \frac{U_1}{i_1} \Big|_{i_2=0}$$

$$= R_1 + R_2$$

$$U_2 = Z_{21} i_1 + Z_{22} i_2$$

$$Z_{21} = \frac{U_2}{i_1} \Big|_{i_2=0}$$

$$= R_2$$


$$v_1 = z_{11} i_1 + z_{12} i_2$$

$$z_{12} = \frac{v_1}{i_2} \Big|_{i_1=0} = R_2$$

$$v_2 = z_{21} i_1 + z_{22} i_2$$

$$z_{22} = \frac{v_2}{i_2} \Big|_{i_1=0} = R_2$$
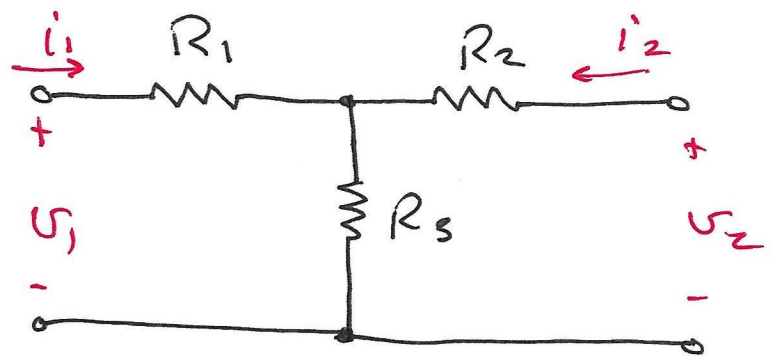
$$\begin{aligned}
 \therefore V_1 &= \overbrace{(R_1 + R_2)}^{Z_{11}} i_1 + \overbrace{R_2}^{Z_{12}} i_2 \\
 V_2 &= \underbrace{R_2}_{Z_{21}} i_1 + \underbrace{R_2}_{Z_{22}} i_2
 \end{aligned}$$



Find the impedance parameters
 $Z_{11}, Z_{12}, Z_{21}, Z_{22}$

$$Z_{11} = \left. \frac{V_1}{i_1} \right|_{i_2=0} = \frac{(R_1 + R_3) i_1}{i_1} \Big|_{i_2=0} = R_1 + R_3$$


$$Z_{12} = \left. \frac{V_1}{i_2} \right|_{i_1=0} = \frac{R_3 i_2}{i_2} \Big|_{i_1=0} = R_3$$

$$\therefore V_1 = (R_1 + R_3) i_1 + R_3 i_2$$

$$z_{21} = \frac{v_2}{i_1} \Big|_{i_2=0} = \frac{R_3 i_1}{i_1} \Big|_{i_2=0} = R_3$$

$$z_{22} = \frac{v_2}{i_2} \Big|_{i_1=0} = \frac{(R_2 + R_3) i_2}{i_2} \Big|_{i_1=0} = R_2 + R_3$$

$$v_2 = R_3 i_1 + (R_2 + R_3) i_2$$

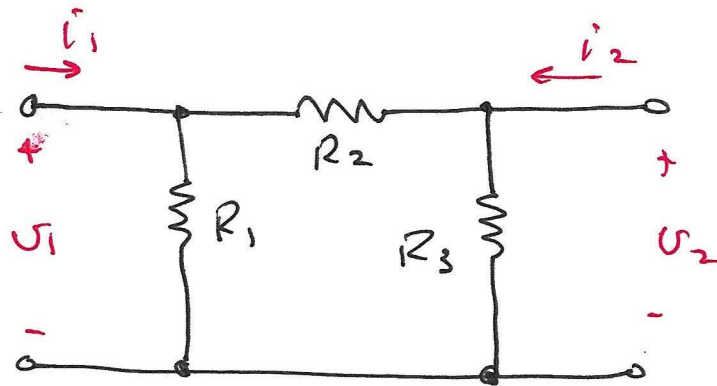

Determine the impedance parameters.

$$Z_{11} = \frac{V_1}{i_1} \Big|_{i_2=0} = \frac{[R_1 \parallel (R_2 + R_3)] i_1}{i_1} \Big|_{i_2=0} = \frac{R_1 (R_2 + R_3)}{R_1 + R_2 + R_3}$$

$$Z_{12} = \frac{V_1}{i_2} \Big|_{i_1=0} = \frac{R_3 R_1}{R_1 + R_2 + R_3} \frac{i_2}{i_2} \Big|_{i_1=0} = \frac{R_1 R_3}{R_1 + R_2 + R_3}$$

$$Z_{21} = \frac{V_2}{i_1} \Big|_{i_2=0} = \frac{R_1 R_3}{R_1 + R_2 + R_3} \frac{i_1}{i_1} \Big|_{i_2=0} = \frac{R_1 R_3}{R_1 + R_2 + R_3}$$

$$Z_{22} = \frac{V_2}{i_2} \Big|_{i_1=0} = \frac{R_1 + R_2}{R_1 + R_2 + R_3} \frac{i_2 R_3}{i_2} = \frac{R_3 (R_1 + R_2)}{R_1 + R_2 + R_3}$$