
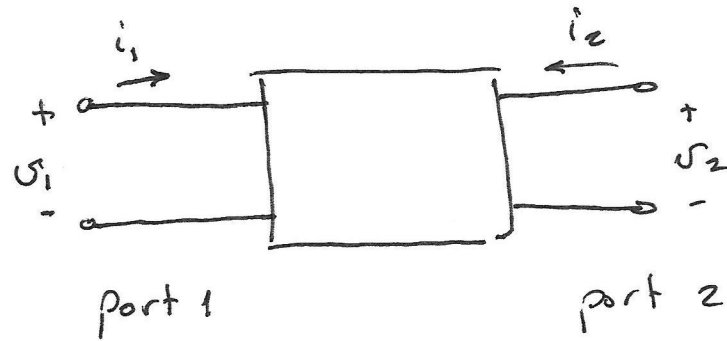


Impedance Parameters

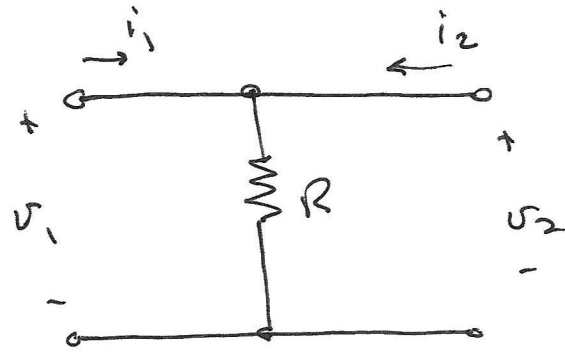

$$v_1 = z_{11} \hat{i}_1 + z_{12} \hat{i}_2$$

$$v_2 = z_{21} \hat{i}_1 + z_{22} \hat{i}_2$$




(1)
$$z_{11} = \frac{v_1}{i_1} \Big|_{i_2=0}$$

(2)
$$z_{12} = \frac{v_1}{i_2} \Big|_{i_1=0}$$

(3)
$$z_{21} = \frac{v_2}{i_1} \Big|_{i_2=0}$$

(4)
$$z_{22} = \frac{v_2}{i_2} \Big|_{i_1=0}$$

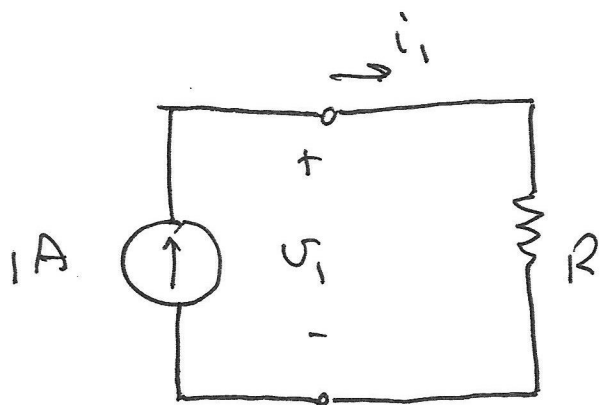To determine z_{11} and z_{21} , connect nothing to the r.h.s. (part 2)




$$(1) \quad z_{11} = \left. \frac{v_1}{i_1} \right|_{i_2=0} = v_1 \Big|_{i_2=0, i_1=1}$$

$$= R$$

$$(3) \quad z_{21} = \left. \frac{v_2}{i_1} \right|_{i_2=0} = v_2 \Big|_{i_2=0, i_1=1}$$

$$= R$$

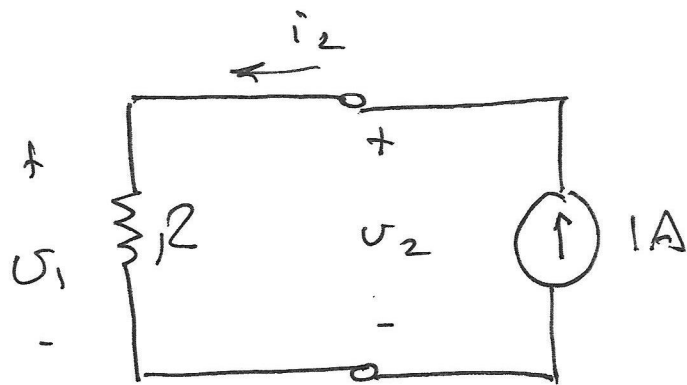


$$(2) \quad Z_{12} = \frac{U_1}{i_2} \Big|_{i_1=0} = U_1 \Big|_{i_1=0, i_2=1} = R$$

$$(4) \quad Z_{22} = \frac{U_2}{i_2} \Big|_{i_1=0} = U_2 \Big|_{i_1=0, i_2=1} = R$$

$$\therefore \quad U_1 = Ri_1 + Ri_2$$


$$U_2 = Ri_1 + Ri_2$$

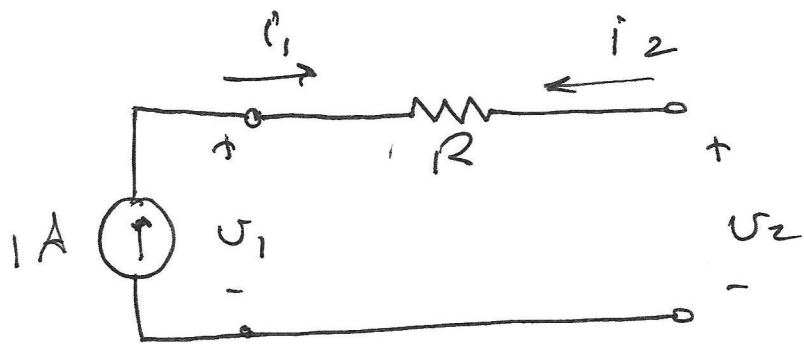

$$z_{in} = \frac{v_1}{i_1} \Big|_{i_2=0} = v_1 \Big|_{i_2=0, i_1=1} = ?$$

impossible

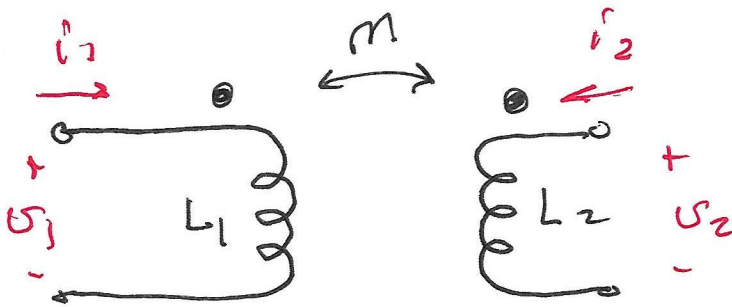This 2-port network does not have an impedance parameter description.




$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

$$V_1 = j\omega L_1 I_1 + j\omega M I_2$$
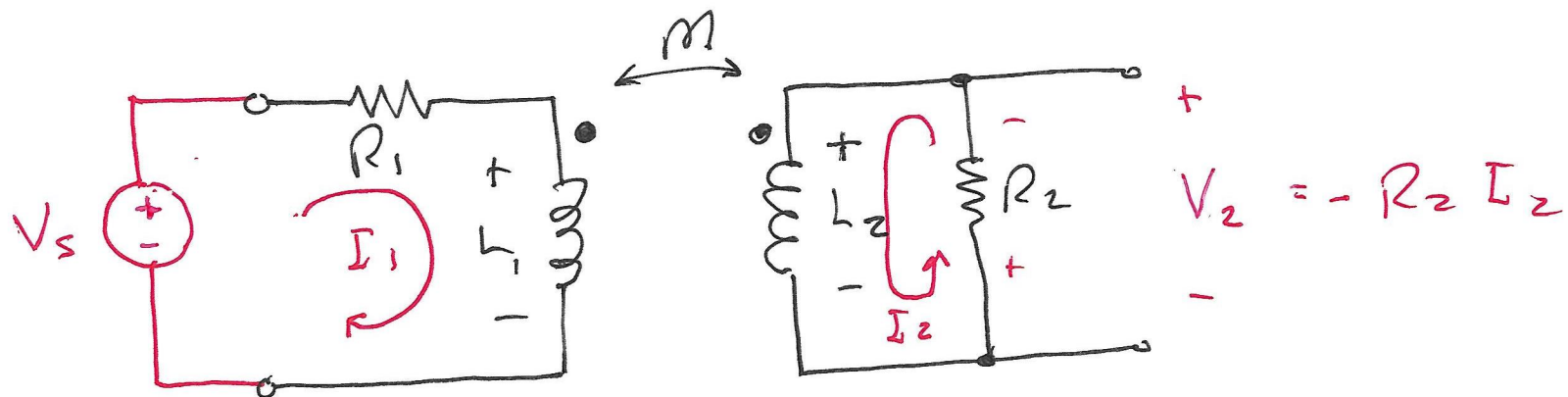
$$V_2 = j\omega M I_1 + j\omega L_2 I_2$$



$$-V_s + R_1 I_1 + j\omega L_1 I_1 + j\omega M I_2 = 0$$

$$R_2 I_2 + j\omega L_2 I_2 + j\omega M I_1 = 0$$


Solve for I_2 . Then $V_2 = -R_2 I_2$

$$\begin{bmatrix} R_1 + j\omega L_1 & j\omega M \\ j\omega M & R_2 + j\omega L_2 \end{bmatrix} \begin{bmatrix} \hat{I}_1 \\ \hat{I}_2 \end{bmatrix} = \begin{bmatrix} V_s \\ 0 \end{bmatrix}$$

Use Cramer's Rule:


$$\hat{I}_2 = \frac{\begin{vmatrix} R_1 + j\omega L_1 & V_s \\ j\omega M & 0 \end{vmatrix}}{\begin{vmatrix} R_1 + j\omega L_1 & j\omega M \\ j\omega M & R_2 + j\omega L_2 \end{vmatrix}} = \frac{0 - j\omega M V_s}{(R_1 + j\omega L_1)(R_2 + j\omega L_2) + \omega^2 M^2}$$
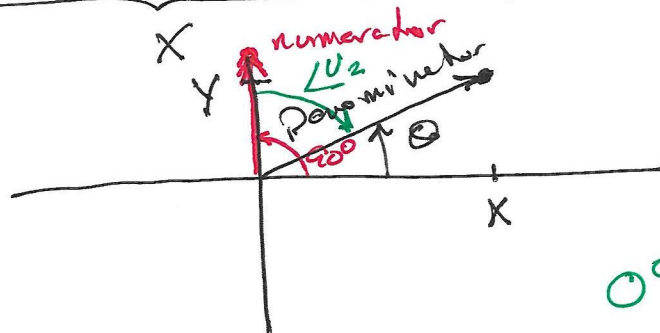
$$V_2 = \frac{j\omega M V_s R_2}{(R_1 R_2 + \omega^2 L_1 L_2 + \omega^2 M^2) + j\omega (L_1 R_2 + L_2 R_1)}$$



$$0 \leq \theta \leq 90^\circ$$
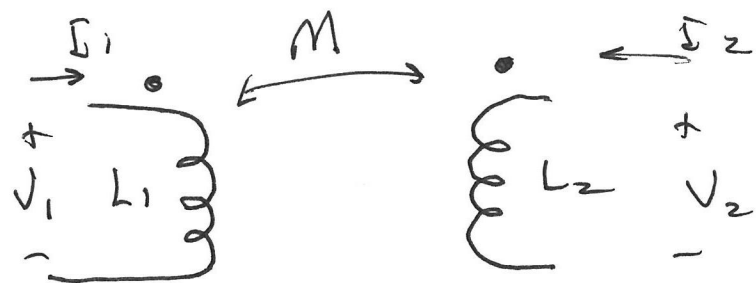
$$0^\circ \leq V_2 \text{ angle} \leq 90^\circ$$



$$V_1 = j\omega L_1 I_1 + j\omega M I_2$$

$$V_2 = j\omega M I_1 + j\omega L_2 I_2$$

