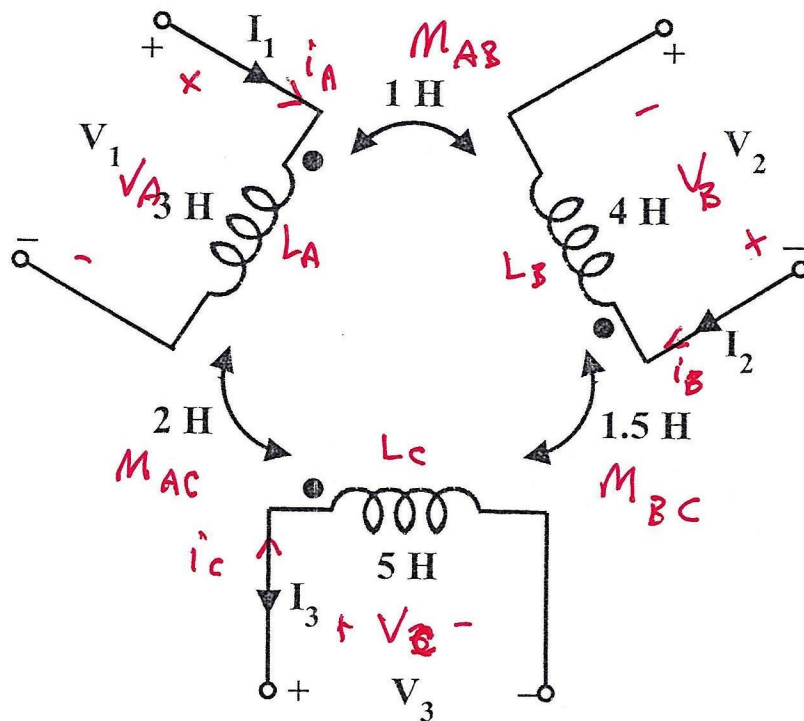


EE 3340  
**Homework Problem #038**

If  $I_1 = 2\angle 0^\circ$  A,  $I_2 = 1\angle 90^\circ$  A,  $I_3 = 1\angle -90^\circ$  A and  $\omega = 2$  rad/s for all three, determine  $V_1$ ,  $V_2$  and  $V_3$  in polar form. Show your work.



$$V_1 = \cancel{V_A} = j2 \cdot 3 \overset{I_1}{\cancel{I_A}} + j2 \cdot 1 \overset{I_2}{\cancel{I_B}} - j2 \cdot 2 \overset{I_3}{\cancel{I_C}} =$$


$$-V_2 = \cancel{V_B} = j2 \cdot 4 \cdot \overset{I_2}{\cancel{I_B}} + j2 \cdot 1 \cdot \overset{I_1}{\cancel{I_A}} - j2 \cdot 1.5 \overset{I_3}{\cancel{I_C}}$$

$$V_3 = \cancel{V_C} = -j2 \cdot 5 \cdot \overset{I_3}{\cancel{I_C}} + j2 \cdot 2 \cdot \overset{I_1}{\cancel{I_A}} + j2 \cdot 1.5 \overset{I_2}{\cancel{I_B}}$$

EE 3340

Homework Problem #038

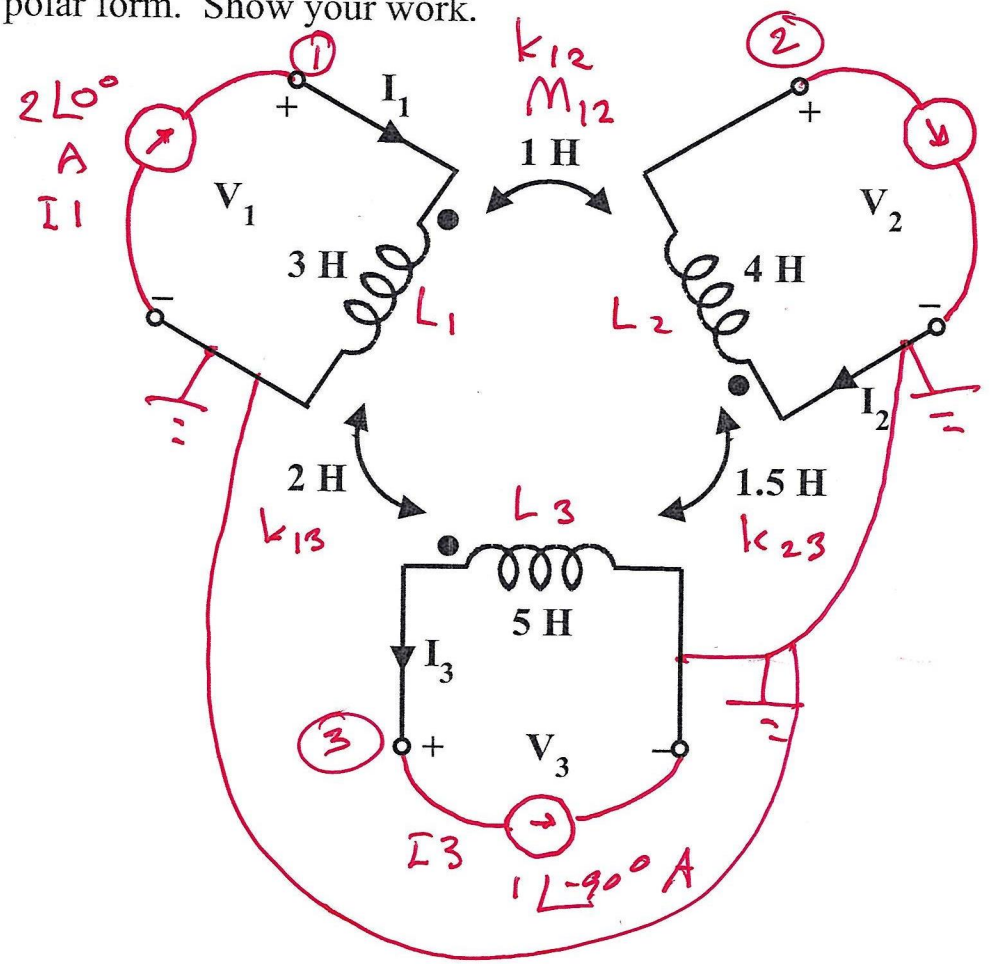If  $I_1 = 2\angle 0^\circ$  A,  $I_2 = 1\angle 90^\circ$  A,  $I_3 = 1\angle -90^\circ$  A and  $\omega = 2$  rad/s for all three, determine  $V_1$ ,  $V_2$  and  $V_3$  in polar form. Show your work.



$$k_{12} = \frac{M_{12}}{\sqrt{L_1 L_2}}$$

$$k_{23} = \frac{M_{23}}{\sqrt{L_2 L_3}}$$

$$k_{13} = \frac{M_{13}}{\sqrt{L_1 L_3}}$$


L1 1 0 3  
 L2 0 2 4  
 L3 3 0 5

{2\*3}

k12 L1 L2 {1/sqrt(3\*4)}  
 k23 L2 L3 {1.5/sqrt(4\*5)}  
 k13 L1 L3 {2/sqrt(3\*5)}

I1 0 1 AC 2 0  
 I2 2 0 AC 1 90  
 I3 3 0 AC 1 -90  
 .AC LIN 1 {2/(2\*pi)} {2/(2\*pi)}

line currents

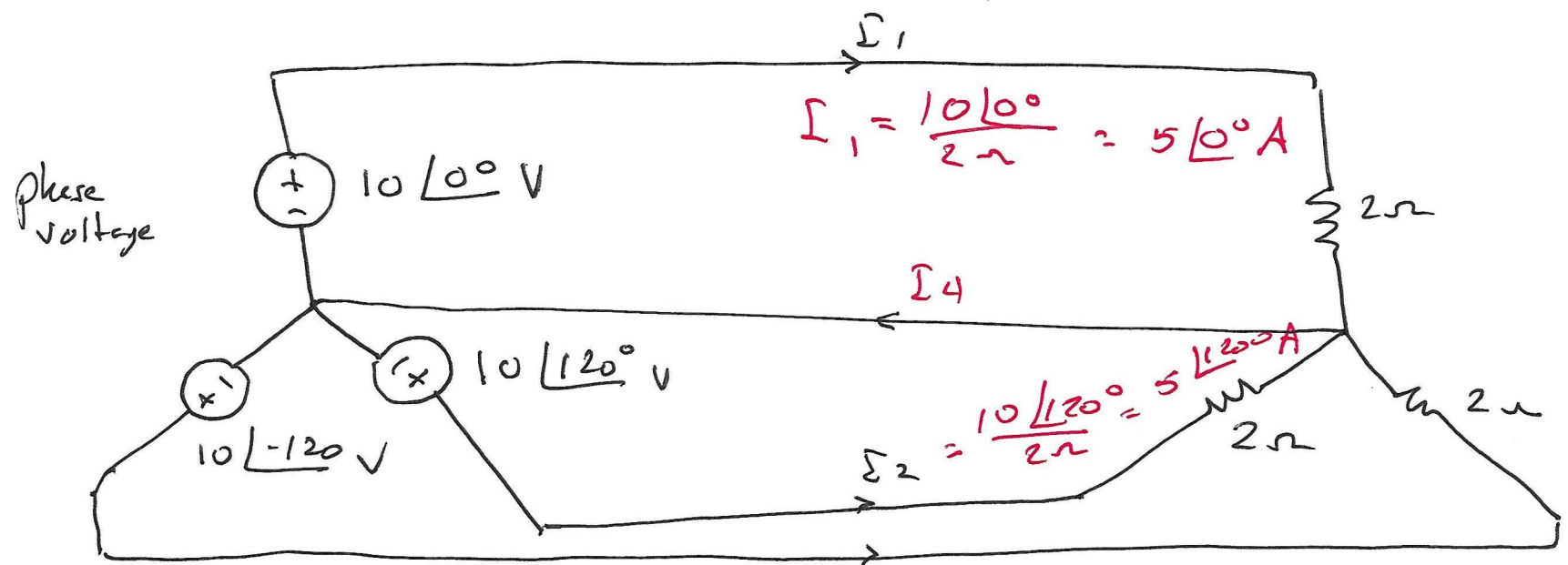

wye-connected source

$$I_3 = \frac{10 \angle -120^\circ}{2 \Omega} = 5 \angle -120^\circ \text{ A load}$$


wye-connected load

all same magnitude and evenly-spaced angles, the system is "balanced"


equal impedances  $\Rightarrow$  balanced load

$$\begin{aligned}
 I_4 &= I_1 + I_2 + I_3 \\
 &= 5 \angle 0^\circ + 5 \angle 120^\circ + 5 \angle -120^\circ \\
 &=
 \end{aligned}$$

3 phase

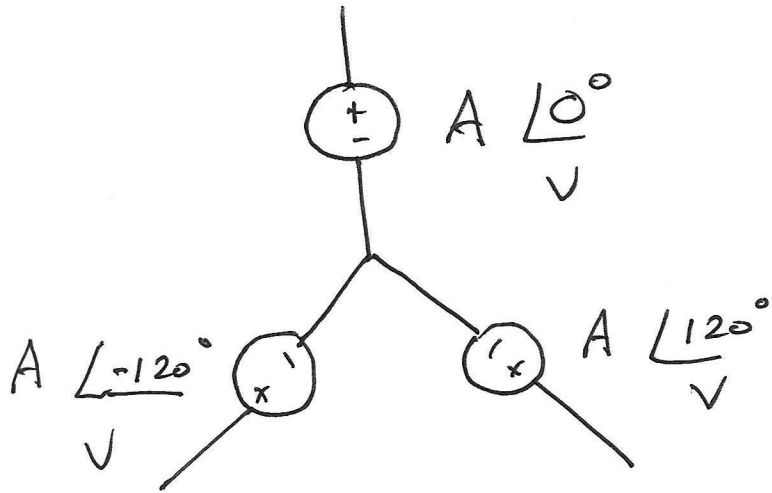


star  
wye

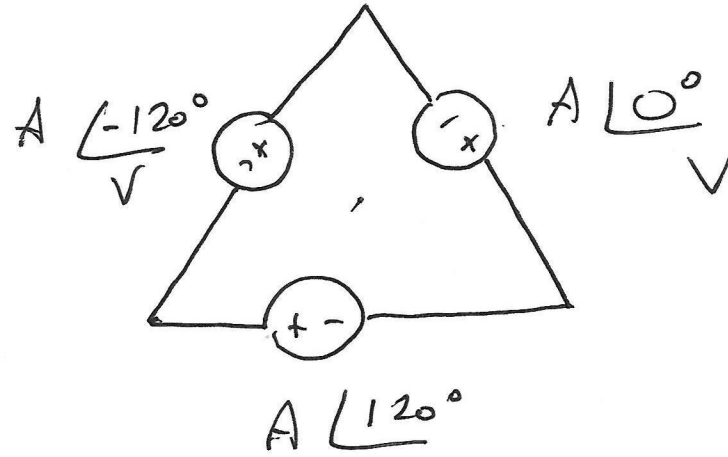

delta

Source



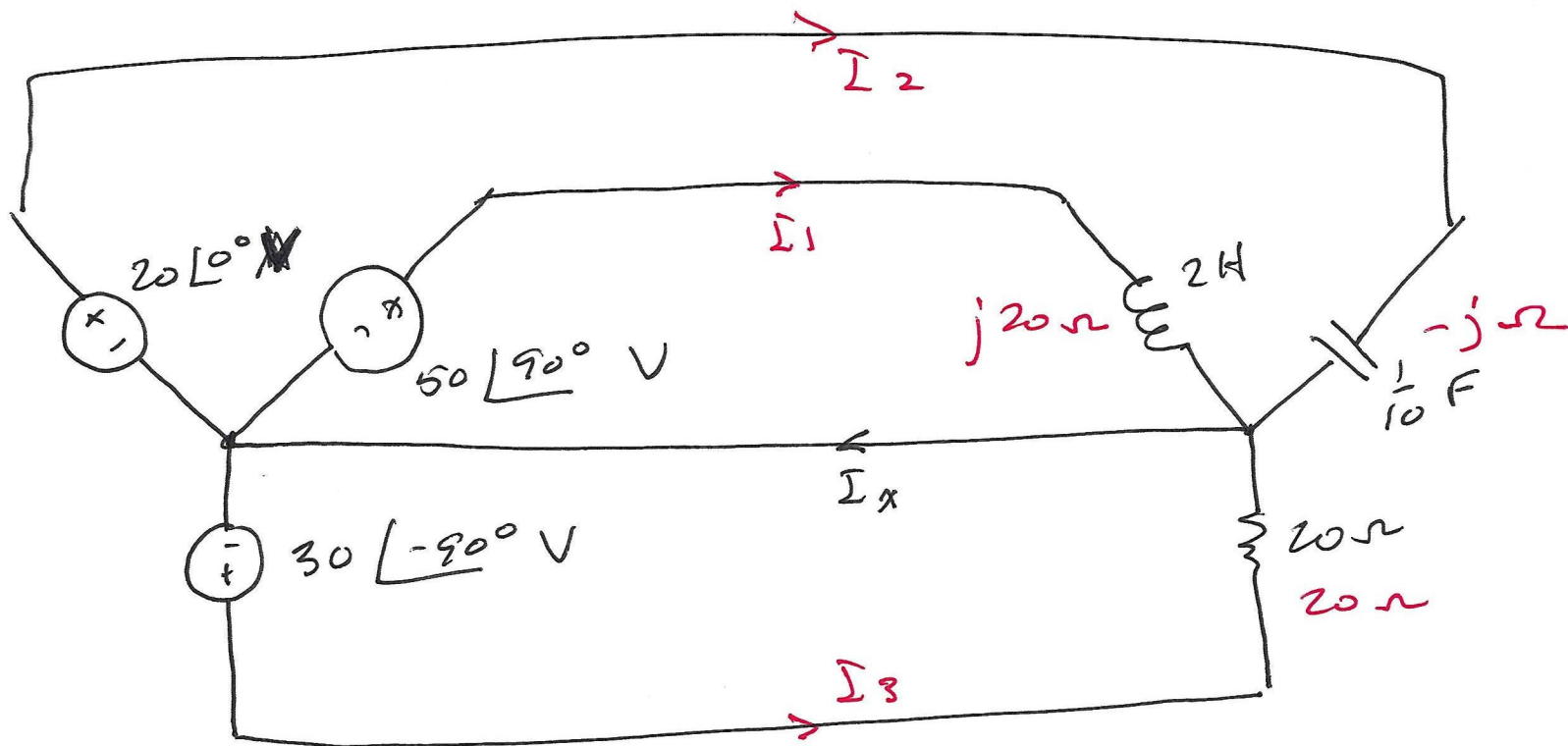

$$\omega = 10 \frac{\text{rad}}{\text{s}}$$

$$I_x = ?$$

$$I_1 = \frac{50 \angle 90^\circ}{j20} = 2.5 \angle 0^\circ \text{ A}$$

$$I_2 = \frac{20 \angle 0^\circ}{-j} = 20 \angle 90^\circ \text{ A}$$

$$I_3 = \frac{30 \angle -90^\circ}{20} = 1.5 \angle -90^\circ \text{ A}$$

$$\begin{aligned}\bar{I}_4 &= \bar{I}_1 + \bar{I}_2 + \bar{I}_3 \\ &= 2.5 \angle 0^\circ + 2 \angle 90^\circ + 1.5 \angle -90^\circ \\ &= 2.5 + j2 - j1.5 \\ &= 2.5 + j0.5 \quad A\end{aligned}$$