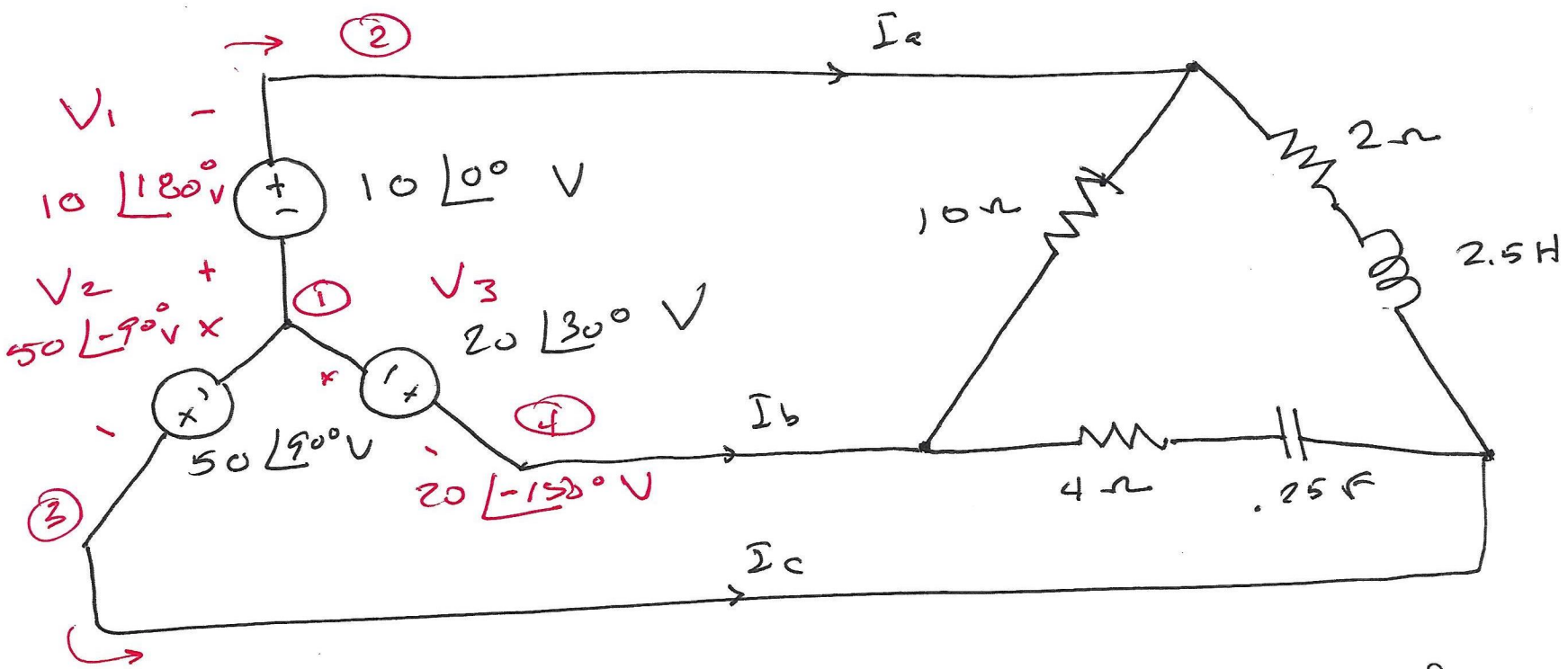


Choose, for example, $\omega = 2 \text{ rad/s}$

Then $j2L = j5 \Rightarrow L = 2.5 \text{ H}$


$-j\frac{1}{2C} = -j2 \Rightarrow C = \frac{1}{4} \text{ F}$




$\omega = 2 \text{ rad/s}$

$f = \frac{\omega}{2\pi} = \frac{1}{\pi} \text{ Hz}$

V_1	1	2	AC	10	180
V_2	1	3	AC	50	-90
V_3	1	4	AC	20	-150
\vdots					
.AC	LIN	1	{1/pi}	{1/pi}	

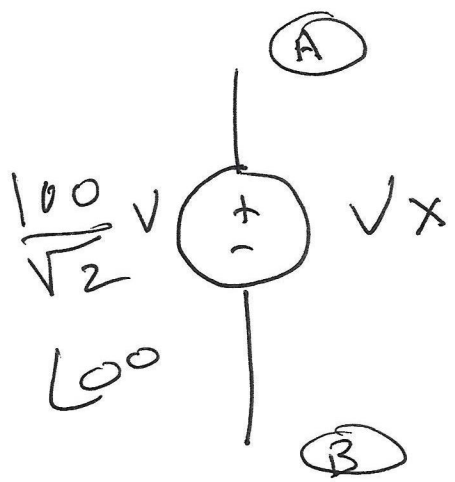

V_x A B AC $\{100/\sqrt{2}\}$

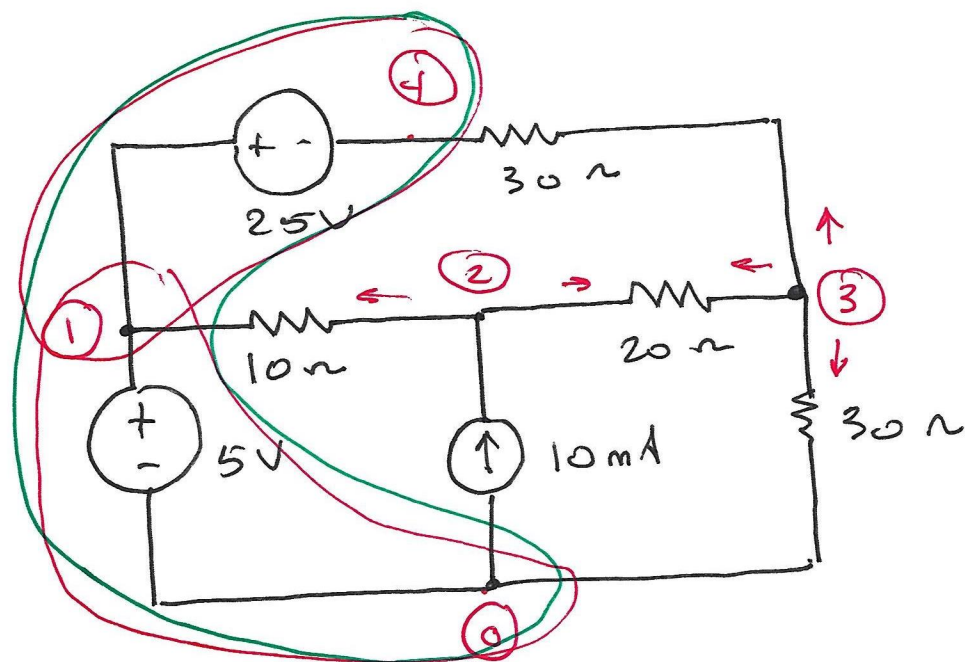

Standard Nodal Analysis

Define supernodes:

$$V_1 = 5$$

$$-V_4 + V_1 = 25$$


Write 2 KCL eqns.

node 2 $\frac{V_2 - V_1}{10} + \frac{V_2 - V_3}{20} - 10 \times 10^{-3} = 0$

node 3 $\frac{V_3 - V_2}{20} + \frac{V_3}{30} + \frac{V_3 - V_4}{30} = 0$

Total of 4 eqns.
4 unknowns.

MNA (Modified Nodal Analysis)

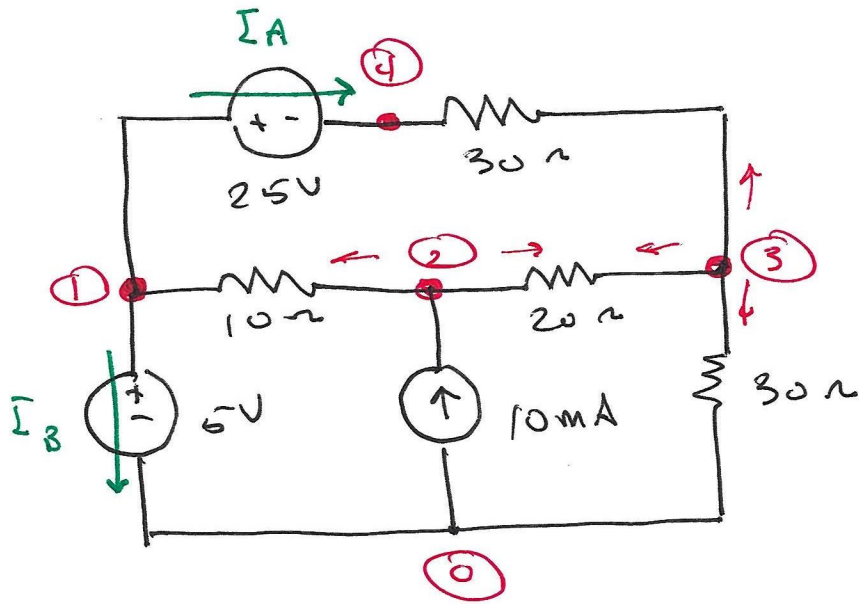

Write constraint equations:

$$V_1 - V_4 = 25$$

$$V_1 = 5$$

KCL for node 1: $\Sigma I_A + \frac{V_1 - V_2}{10} + \Sigma I_B = 0$

KCL for node 2: $\frac{V_2 - V_1}{10} + \frac{V_2 - V_3}{20} - 10 \text{ mA} = 0$


KCL for node 3: $\frac{V_3 - V_2}{20} + \frac{V_3 - V_4}{30} + \frac{V_3}{30} = 0$

KCL for node 4: $-\Sigma I_A + \frac{V_4 - V_3}{30} = 0$

Total of 6 eqns.
6 unknowns.

EE 3340
Homework Problem #043

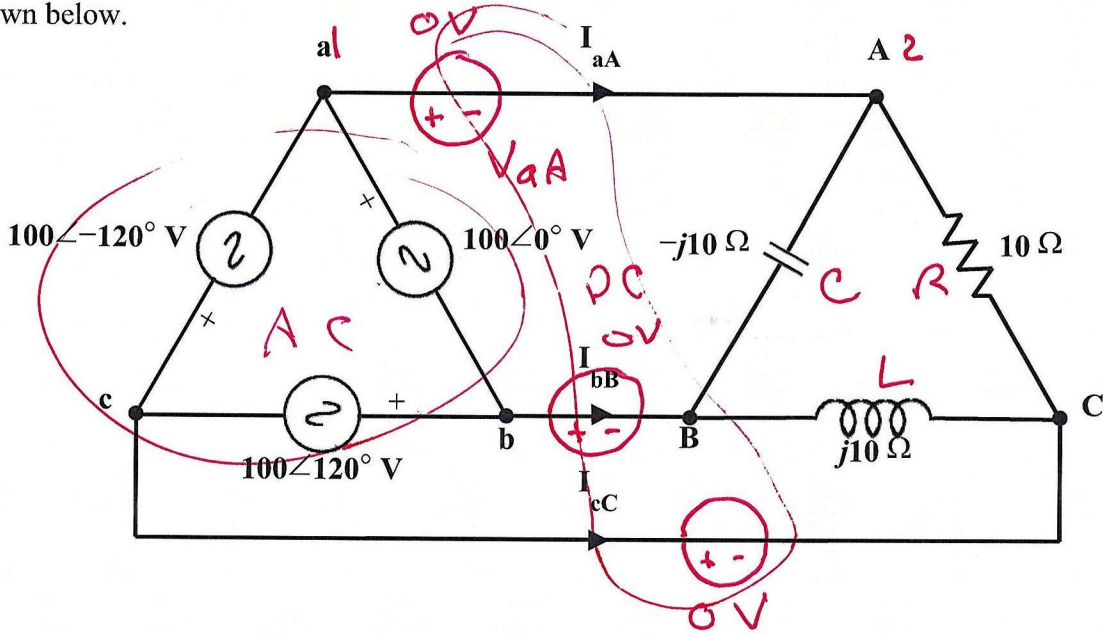Find the line currents, I_{aA} , I_{bB} and I_{cC} (in polar form) in the unbalanced three-phase circuit shown below.



V_{aA} a1 A2 DC 0

For practice, assume $\omega = 10 \text{ rad/s}$

$R = 10 \Omega$

$L = 1 \text{ H}$

$C = 10 \text{ m}$

$$\left\{ \begin{aligned} j\omega L &= j10 \\ j10L &= j10 \\ L &= 1 \text{ H} \end{aligned} \right.$$

$$\left\{ \begin{aligned} -j\frac{1}{\omega C} &= -j10 \\ \frac{1}{10C} &= 10 \\ C &= .01 \text{ F} \end{aligned} \right.$$