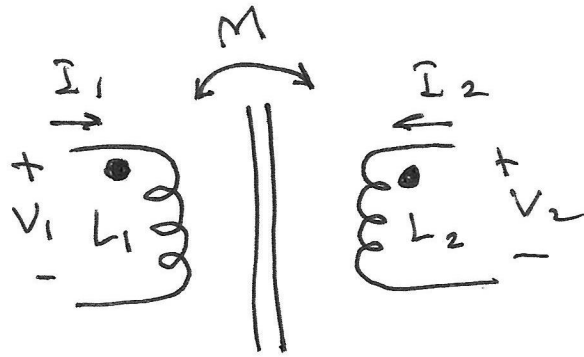


Mutual Inductance



Coefficient of coupling:

$$k = \sqrt{\frac{M}{L_1 L_2}}$$

If coupling is perfect:

$$k = 1$$

In the time domain:

$$v_1(t) = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$


$$v_2(t) = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

In the phasor (frequency) domain:


$$V_1 = j\omega L_1 I_1 + j\omega M I_2$$

$$V_2 = j\omega M I_1 + j\omega L_2 I_2$$

Real Transformer

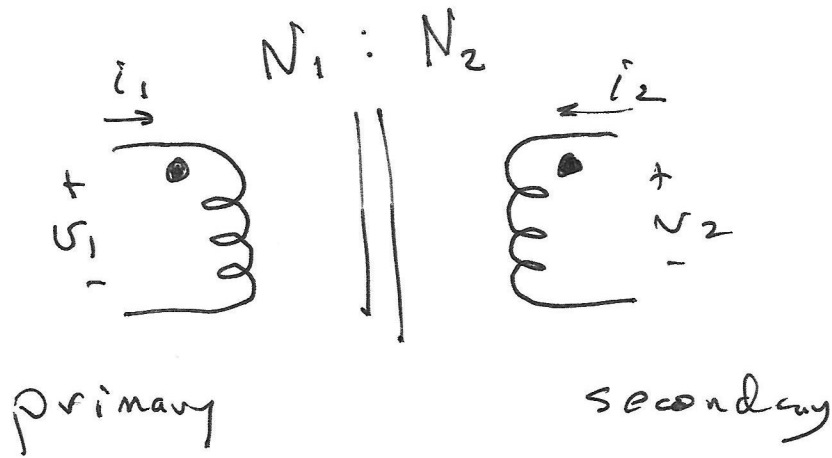

alternate notation

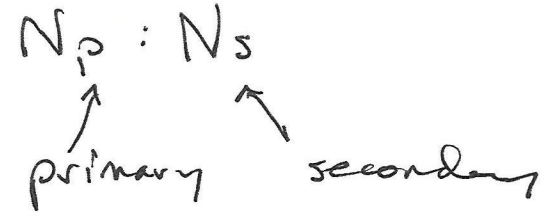

$$v_2 = \frac{N_2}{N_1} v_1$$


$$i_2 = - \frac{N_1}{N_2} i_1$$

Faraday's Law
Lenz's Law


Define $n = \frac{N_2}{N_1}$ ← turns in secondary
← turns in primary

$$U_2 = n U_1$$
$$i_2 = -\frac{1}{n} i_1 \Rightarrow i_1 = -n i_2$$

$$i_1 U_1 = i_2 U_2$$

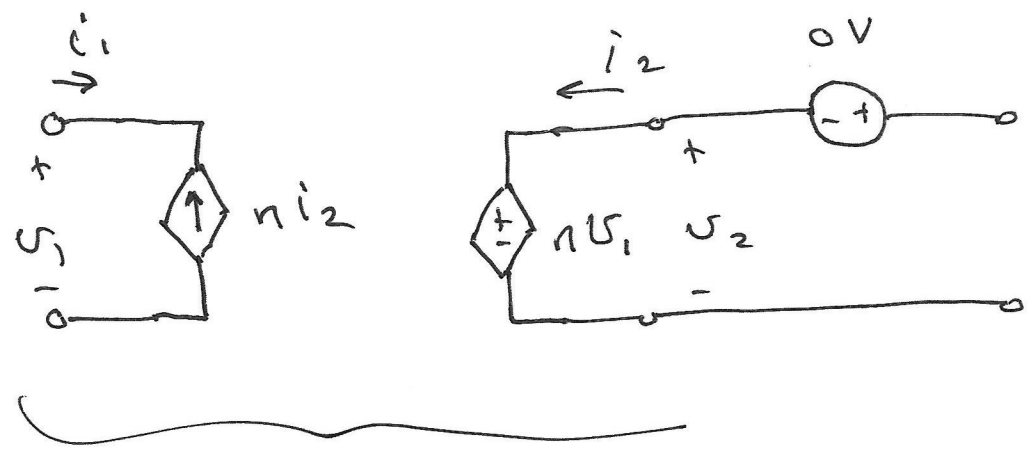

ideal transformer

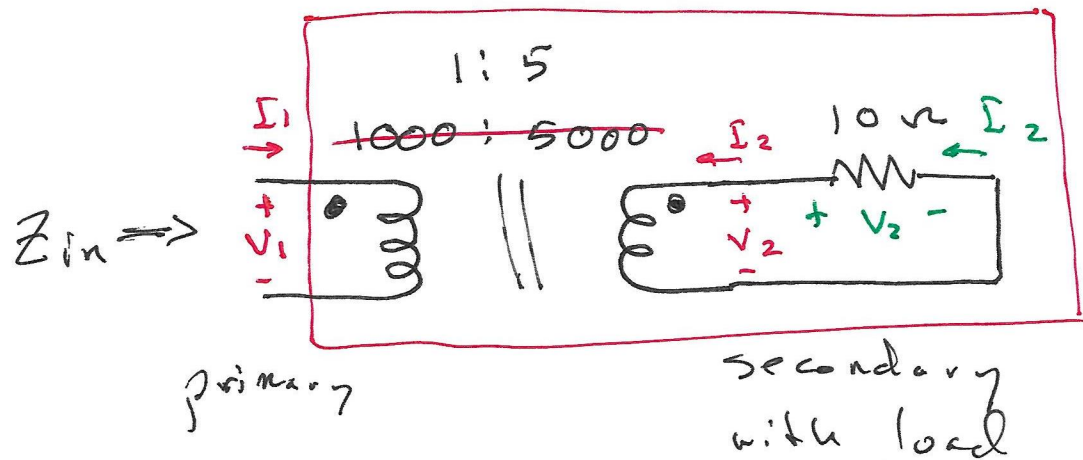

$$V_2 = -10 I_2$$

$$-\frac{V_2}{I_2} = 10$$

$$\frac{N_2}{N_1} = \frac{5}{1} \quad \text{or} \quad n = 5$$


$$V_2 = 5 V_1$$

$$I_2 = -\frac{1}{5} I_1$$

$$Z_{in} = \frac{V_1}{I_1} = \frac{\frac{1}{5} V_2}{-5 I_2} = -\frac{1}{25} \frac{V_2}{I_2}$$

$$-\frac{V_2}{I_2} = 10 \Omega$$
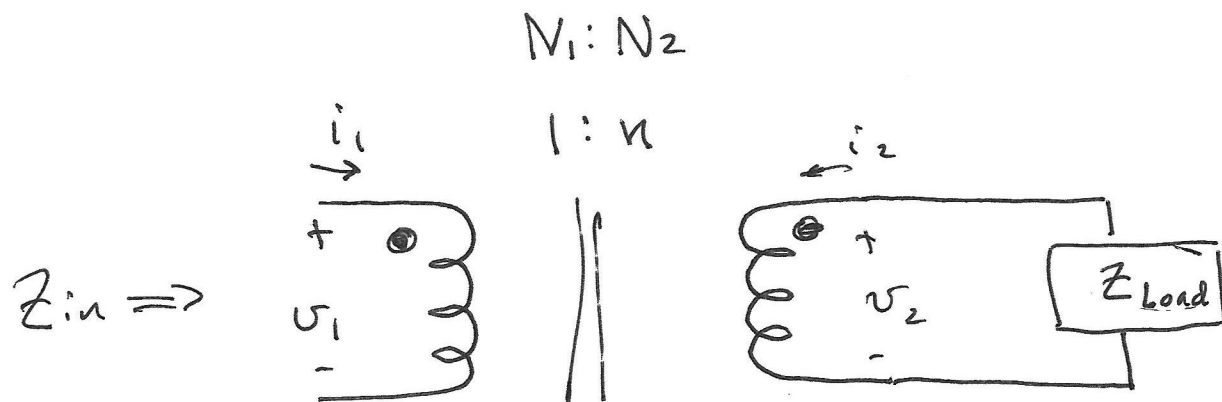
$$Z_{in} = -\frac{1}{25} (-10) = \frac{10}{25} = \frac{2}{5} \Omega$$



Determine Z_{in} in terms of n and Z_{load}

$$v_2 = n v_1$$

$$i_2 = -\frac{1}{n} i_1$$

$$v_2 = -Z_{load} i_2$$

$$v_2 = n v_1$$

$$i_2 = -\frac{1}{n} i_1$$

$$v_2 = -Z_{load} i_2$$

$$Z_{in} = \frac{v_1}{i_1}$$


$$Z_{in} = \frac{V_1}{I_1}$$

$$= \frac{\frac{1}{n} V_2}{-n I_2}$$

$$= -\frac{1}{n^2} \frac{V_2}{I_2}$$

$$= -\frac{1}{n^2} (-Z_{Load})$$

$$Z_{in} = \frac{1}{n^2} Z_{Load}$$

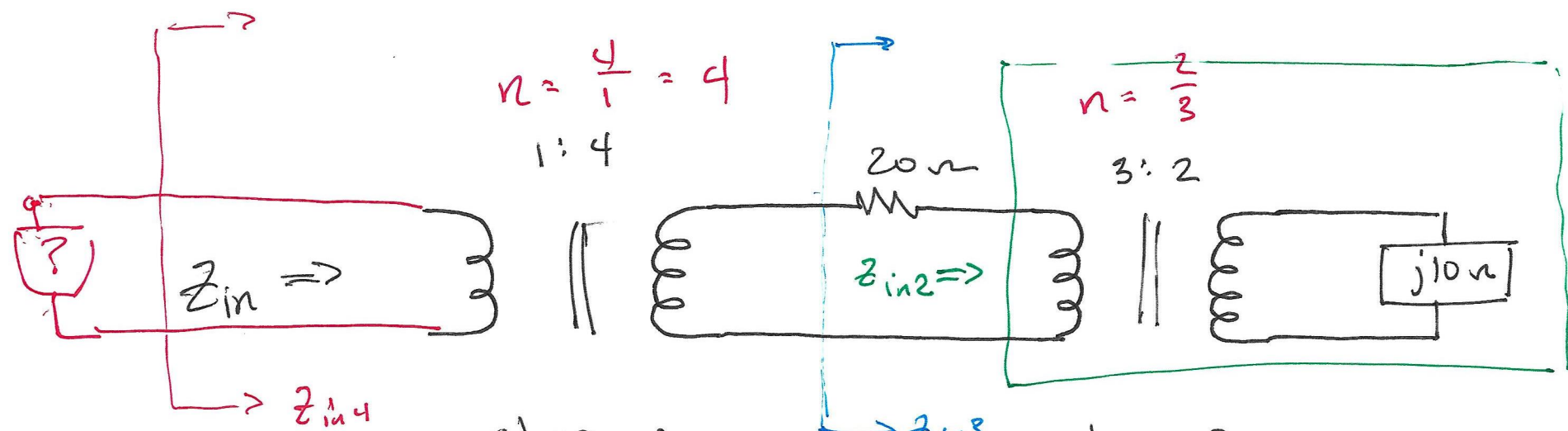

step-up transformer
(higher voltage on secondary)

step-down transformer
(lower voltage on secondary)

$$\begin{aligned}
 Z_{in2} &= \frac{1}{\left(\frac{2}{3}\right)^2} (j10) \\
 &= j\frac{90}{4} = j17.5 \Omega \\
 &= j\frac{45}{2} \Omega
 \end{aligned}$$

$$Z_{in3} = 20 + Z_{in2} = 20 + j\frac{45}{2} \Omega$$

$$\begin{aligned}
 Z_{in} &= \frac{1}{(4)^2} Z_{in3} \\
 &= \frac{1}{16} \left[20 + j \frac{45}{2} \right] \\
 &= \frac{5}{4} + j \frac{45}{32} \quad \Omega
 \end{aligned}$$

Assume ω is given.


Z_{in} has two components:


$\frac{5}{4}$ real \Rightarrow resistor of $\frac{5}{4} \Omega$

$\frac{45}{32} + j$ imaginary \Rightarrow inductor with

$$j\omega L = j \frac{45}{32}$$

$$L = \frac{45}{32\omega}$$

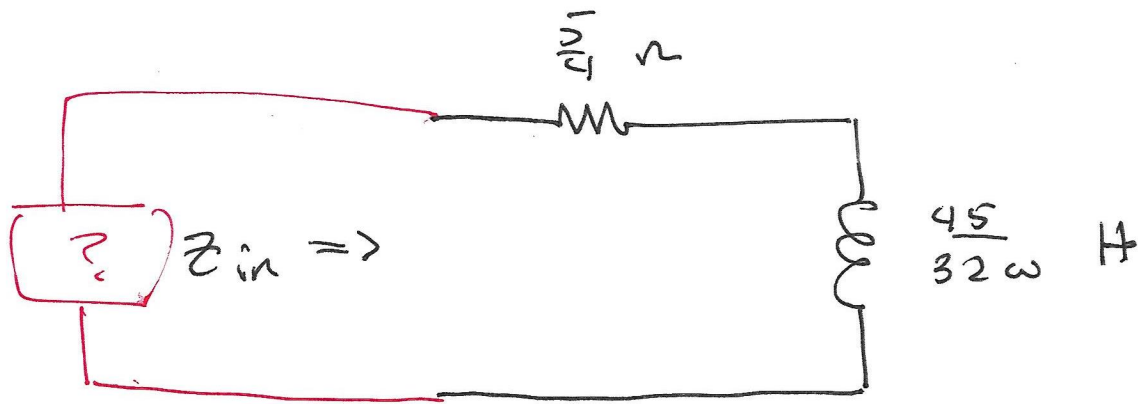

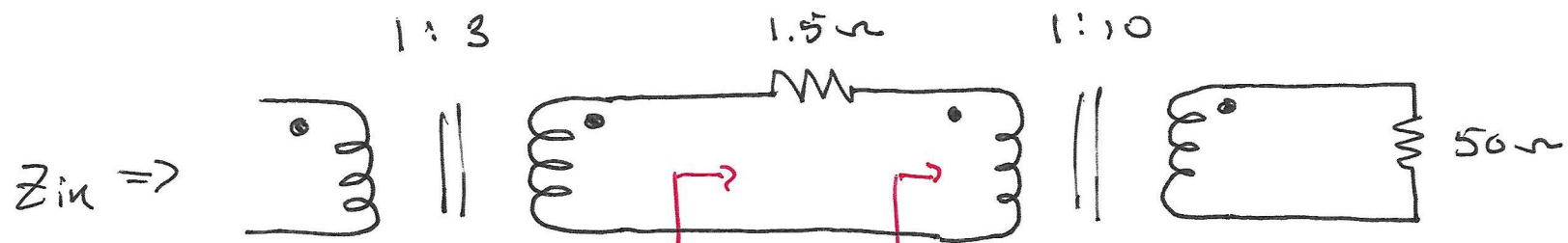

$$\frac{1}{(3)^2} (2)$$

$$= \frac{2}{9}$$

$$\approx .22 \Omega$$

$$Z_2 = 2 \Omega$$

$$Z_1 = .5 \Omega$$