

Name \_\_\_\_\_


*By writing or printing my name in the space above, I hereby affirm that I have neither given nor received assistance in preparing solutions for this exam.*

EE 3340  
**Final Exam**  
 Spring Semester 2022

**Show all work neatly and completely.**  
**Credit will not be given for work not shown.**

There are 7 problems provided here. Choose any 6 to submit for grading. Each of the 6 problems you submit will be worth a maximum of 25 points, making 150 points the maximum total possible score on the exam. There will be very little partial credit; take your time and **check your work**.

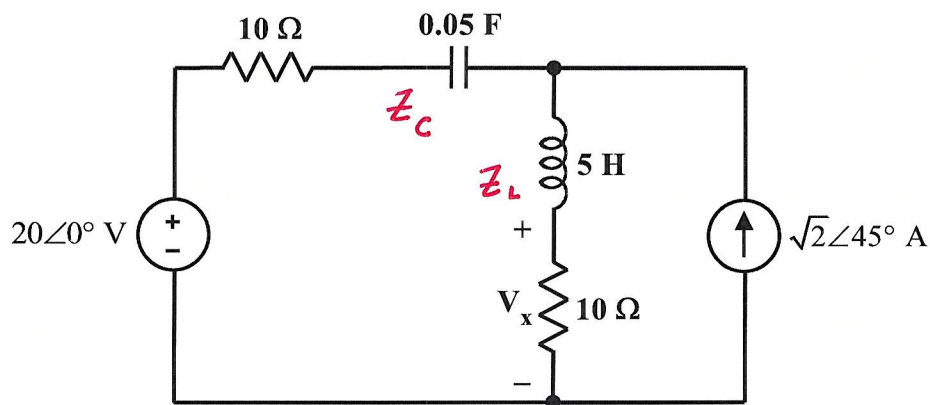1. Determine  $V_x$  in polar form if  $\omega = 2 \text{ rad/s}$ .



$$Z_C = \frac{1}{j(2)(0.05)} = -j10 \Omega, \quad Z_L = j(2)(5) = j10 \Omega$$

Use the superposition method.

Contribution from the voltage source:


$$V_{x1} = \frac{10}{10 + Z_C + Z_L + 10} \cdot 20 \angle 0^\circ = 10 \angle 0^\circ \text{ V}$$

Contribution from the current source:

$$\begin{aligned} V_{x2} &= 10 \cdot \frac{10 + Z_C}{10 + Z_C + Z_L + 10} \cdot \sqrt{2} \angle 45^\circ \\ &= \frac{1}{2} \cdot 10 \sqrt{2} \angle -45^\circ \cdot \sqrt{2} \angle 45^\circ = 10 \angle 0^\circ \text{ V} \end{aligned}$$

$$\therefore V_x = V_{x1} + V_{x2} = 20 \angle 0^\circ \text{ V}$$

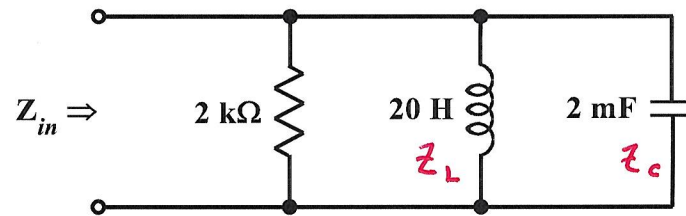2. Determine the input impedance,  $Z_{in}$ , in rectangular (Cartesian) form if  $\omega = 5$  rad/s.




$$z_L = j(5)(20) = j100\ \Omega$$

$$z_c = \frac{1}{j(5)(2 \times 10^{-3})} = -j100\ \Omega$$

$$z_{in} = \frac{1}{\frac{1}{2000} + \frac{1}{j100} + \frac{1}{-j100}}$$

$$= 2000 \angle 0^\circ\ \Omega$$

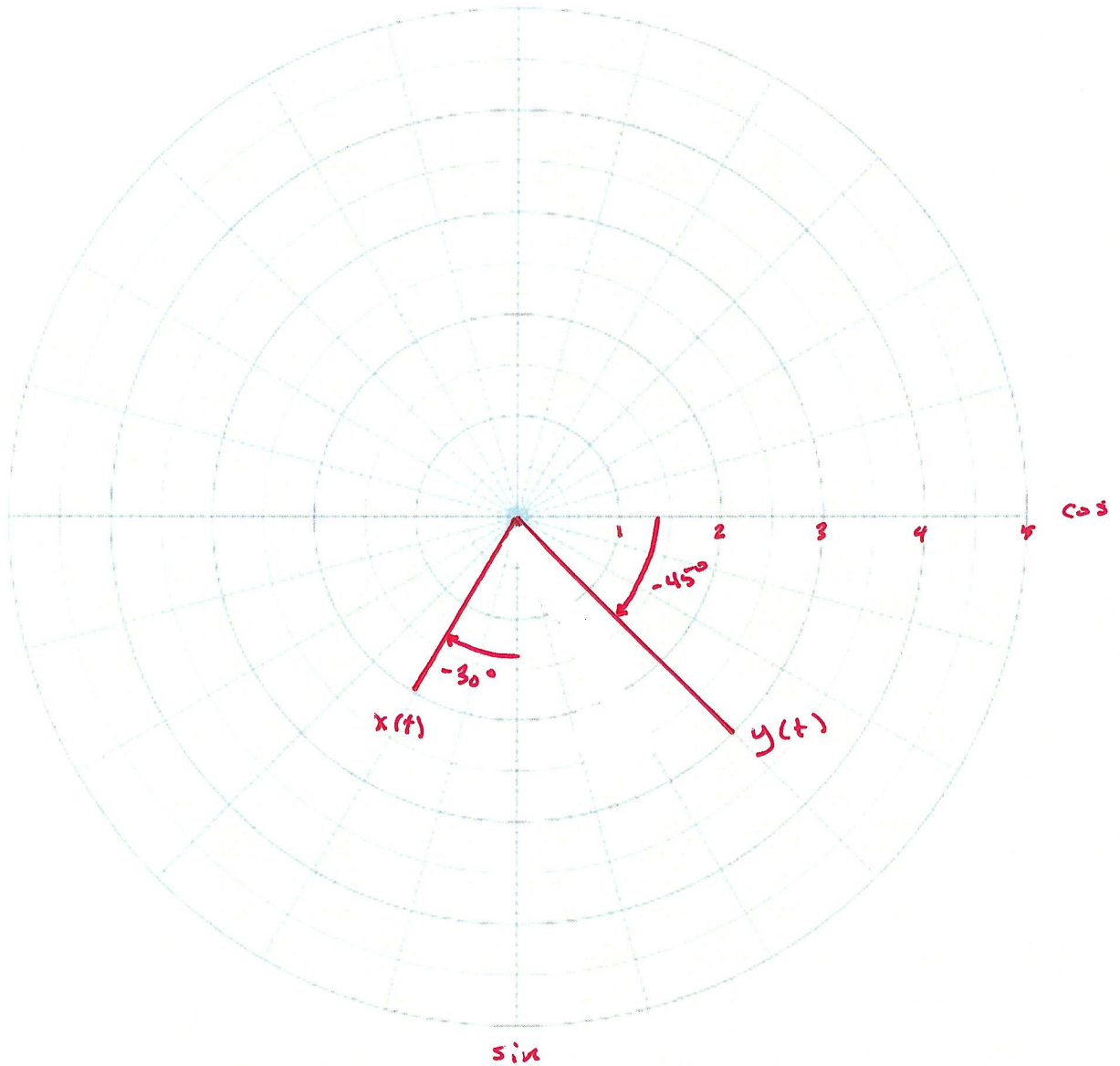
3. Given two signals,  $x(t) = 2\sin(\omega t - 30^\circ)$  and  $y(t) = 3\cos(\omega t - 45^\circ)$ :
- a. Accurately sketch a phasor diagram showing the proper length and orientation of each of these two signals.



- b. What is the phase angle of  $x(t)$  *with respect to*  $y(t)$ ?

$$-30^\circ - 90^\circ + 45^\circ = -75^\circ$$

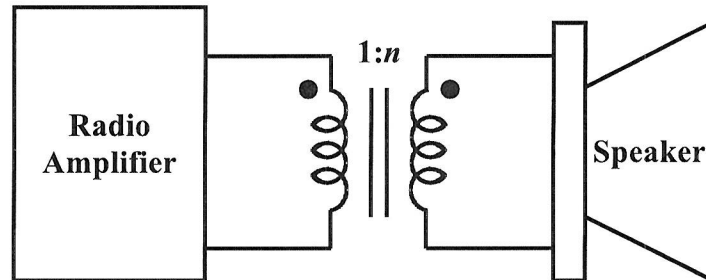
4. As a final step in the design process, the output stage of a radio amplifier must be matched to the impedance of its speaker by using an impedance-matching transformer as shown below. The selected speaker has input impedance equal to  $4\ \Omega$ , and the amplifier requires a load impedance of  $2500\ \Omega$  for optimum performance. Assume the transformer is ideal, and determine the necessary turns ratio to accomplish the desired match



$$\left(\frac{1}{n}\right)^2 (4\ \Omega) = 2500\ \Omega$$

$$\Rightarrow \frac{1}{n} = \sqrt{\frac{2500}{4}} = 25$$

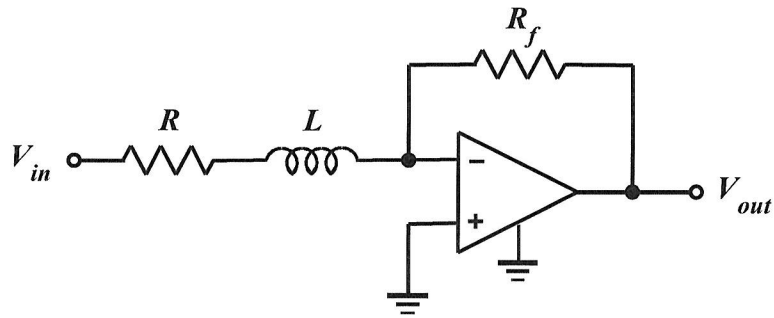
5. Determine the voltage transfer function of the filter circuit shown below and classify the filter as LP, HP, BP or BS. **Clearly** explain your reasoning.



$$\frac{V_{out}}{V_{in}} = - \frac{R_f}{R + j\omega L}$$


$$\omega \rightarrow 0 \Rightarrow \left| \frac{V_{out}}{V_{in}} \right| \rightarrow \frac{R_f}{R}$$

$$\omega \rightarrow \infty \Rightarrow \left| \frac{V_{out}}{V_{in}} \right| \rightarrow 0$$

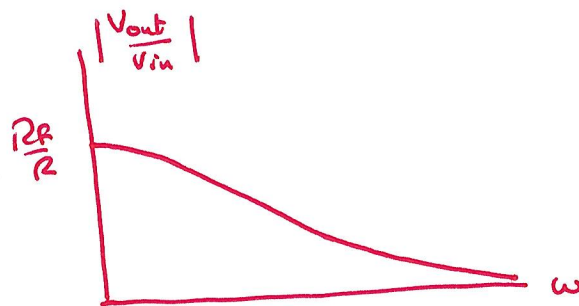

This is a LP filter.

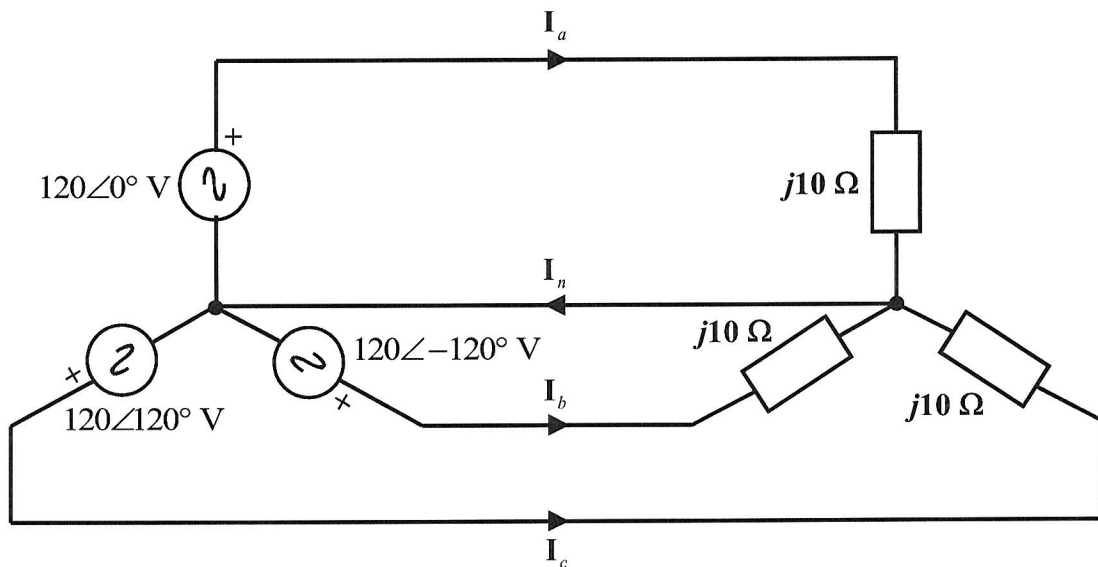6. A balanced three-phase distribution system is shown below. Determine the value of the neutral current,  $I_n$ , in rectangular (Cartesian) form.



Balanced  $\Rightarrow I_n = 0$

Proof:

$$I_a = \frac{120 \angle 0^\circ}{j10} = 12 \angle -90^\circ \text{ A} = -j12 \text{ A}$$

$$I_b = \frac{120 \angle -120^\circ}{j10} = 12 \angle -210^\circ \text{ A} = 12 \angle 150^\circ \text{ A}$$

$$= 12 \cos 150^\circ + j12 \sin 150^\circ$$

$$= -12 \cos 30^\circ + j12 \sin 30^\circ$$

$$I_c = \frac{120 \angle 120^\circ}{j10} = 12 \angle 30^\circ = 12 \cos 30^\circ + j12 \sin 30^\circ$$

$$I_n = I_a + I_b + I_c$$


$$= -j12 - 12 \cos 30^\circ + j12 \sin 30^\circ + 12 \cos 30^\circ + j12 \sin 30^\circ$$

$$= -j12 + j24 \sin 30^\circ$$

$$= -j12 + j12$$

$$= 0 \text{ A}$$

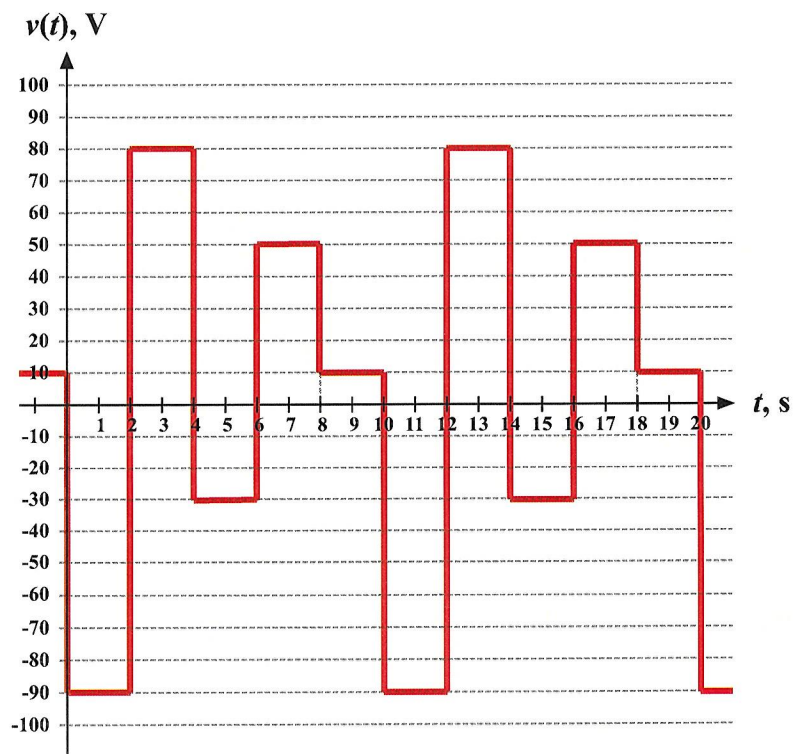7. The waveform shown below is periodic with  $T = 10$  s. Determine the *average and effective* values of  $v(t)$ .



$$V_{ave} = \frac{-90 + 80 - 30 + 50 + 10}{5} = 4 \text{ V}$$

$$V_{rms} = \sqrt{\frac{(-90)^2 + (80)^2 + (-30)^2 + (50)^2 + (10)^2}{5}}$$

$$= 60 \text{ V}$$