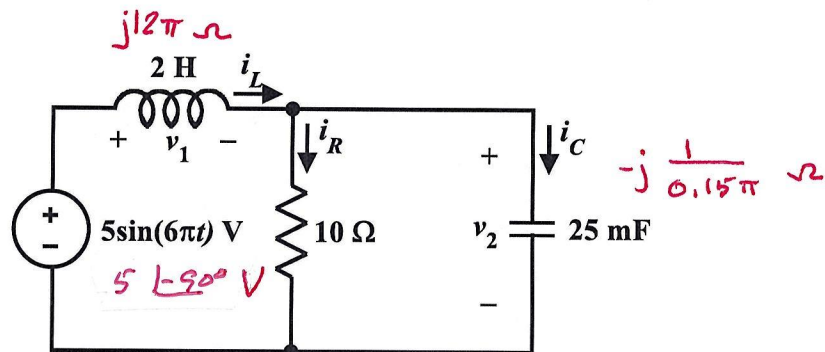


Homework Problem #009

For the circuit shown below, use the phasor analysis method to determine the AC steady-state part of $v_1(t)$, $v_2(t)$, $i_L(t)$, $i_R(t)$ and $i_C(t)$. Express your answers in polar form with the phase angles in degrees.



Using mesh analysis:

$$j12\pi \bar{I}_L + 10(\bar{I}_L - \bar{I}_C) = 5 \angle -90^\circ \quad \text{or} \quad -j5$$

$$10(\bar{I}_C - \bar{I}_L) - j \frac{1}{0.15\pi} \bar{I}_C = 0$$

In matrix form:

$$\begin{bmatrix} j12\pi + 10 & -10 \\ -10 & 10 - j \frac{1}{0.15\pi} \end{bmatrix} \begin{bmatrix} \bar{I}_L \\ \bar{I}_C \end{bmatrix} = \begin{bmatrix} -j5 \\ 0 \end{bmatrix}$$

Solving yields:

$$\bar{I}_L = -0.1402 - j0.0017 \approx 0.1402 \angle -179.3^\circ \text{ A}$$

$$\bar{I}_C = -0.1338 - j0.0301 \approx 0.1371 \angle -167.3^\circ \text{ A}$$

Then

$$V_1 = j12\pi \bar{I}_L \approx 5.28 \angle -89.3^\circ \text{ V}$$

$$V_2 = -j \frac{1}{0.15\pi} \bar{I}_C \approx 0.291 \angle 102.7^\circ \text{ V}$$

$$\begin{aligned} \bar{I}_R &= \bar{I}_L - \bar{I}_C = -0.0064 + j0.0284 \\ &\approx 0.0291 \angle 102.7^\circ \text{ A} \end{aligned}$$