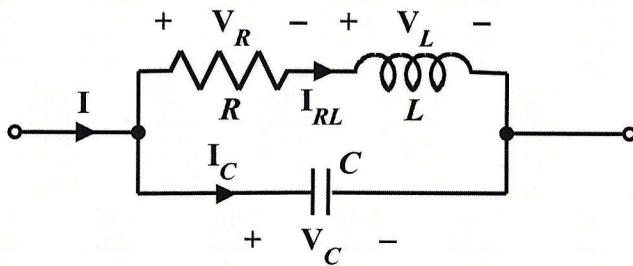


EE 3340  
Homework Problem #019

The circuit shown below is sometimes called a "tuning circuit."



If  $R = 20\Omega$ ,  $L = 5\text{mH}$ , and  $C = 0.5\mu\text{F}$ :

- a. Determine the frequency,  $\omega$ , at which its equivalent impedance,  $Z_{eq} = \frac{V_c}{I}$ , is purely resistive.

$$Z_{eq} = \frac{1}{j\omega C} \parallel (R + j\omega L) = \frac{\frac{1}{j\omega C}(R + j\omega L)}{\frac{1}{j\omega C} + R + j\omega L} = \frac{\frac{L}{C} - j\frac{R}{\omega C}}{R + j(\omega L - \frac{1}{\omega C})} \cdot \frac{R - j(\omega L - \frac{1}{\omega C})}{R - j(\omega L - \frac{1}{\omega C})}$$

$$= \frac{\frac{RL}{C} - \frac{R}{\omega C}(\omega L - \frac{1}{\omega C}) - j\frac{R^2}{\omega C} - j\frac{L}{C}(\omega L - \frac{1}{\omega C})}{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

$$\text{Im}\{Z_{eq}\} = 0 \Rightarrow \frac{R^2}{\omega C} + \frac{L}{C}(\omega L - \frac{1}{\omega C}) = 0 \Rightarrow \left(\frac{L}{C} - R^2\right) \frac{1}{\omega} = L^2 \omega$$

$$\text{or } \omega^2 = \frac{1}{L^2} \left(\frac{L}{C} - R^2\right) = \frac{1}{LC} - \frac{R^2}{L^2} \Rightarrow \omega = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$\therefore$  With the given component values,  $\omega = 19.6 \text{ k rad/s}$

- b. For the frequency determined in part a, determine that equivalent resistance.

$$\text{Re}\{Z_{eq}\} = \frac{\frac{RL}{C} - \frac{R}{\omega C}(\omega L - \frac{1}{\omega C})}{R^2 + (\omega L - \frac{1}{\omega C})^2} = 500 \Omega$$