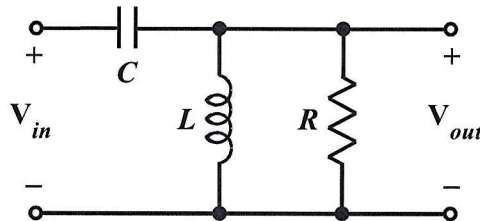


Homework Problem #022

The component values in the passive filter circuit shown below are: $C = 10\mu\text{F}$, $L = 1\text{H}$, and $R = 10\text{k}\Omega$.



- a. Derive an expression for the voltage transfer function, V_{out}/V_{in} . Also, determine expressions for the magnitude and the phase angle of that transfer function.

$$\frac{V_{out}}{V_{in}} = \frac{\frac{(j\omega L)R}{j\omega L + R}}{\frac{1}{j\omega C} + \frac{(j\omega L)R}{j\omega L + R}} = \frac{(j\omega L R)(j\omega C)}{(j\omega L + R) + (j\omega L)(j\omega C)R} = \frac{-\omega^2 L R C}{R(1 - \omega^2 L C) + j\omega L}$$

$$= \frac{-0.1 \omega^2}{10^4 (1 - 10^{-5} \omega^2) + j\omega}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{0.1 \omega^2}{\sqrt{10^8 (1 - 10^{-5} \omega^2)^2 + \omega^2}}$$

$$\angle \frac{V_{out}}{V_{in}} = 180^\circ - \tan^{-1} \frac{\omega}{10^4 (1 - 10^{-5} \omega^2)}$$

- b. Classify the filter as LP, HP, BP or BS, and explain your reasoning.

$$\lim_{\omega \rightarrow 0} \left| \frac{V_{out}}{V_{in}} \right| = \frac{0}{10^4} = 0$$

$$\lim_{\omega \rightarrow \infty} \left| \frac{V_{out}}{V_{in}} \right| = \lim_{\omega \rightarrow \infty} \frac{0.1 \omega^2}{0.1 \omega^2} = 1$$

This is a High Pass (HP) filter characteristic.