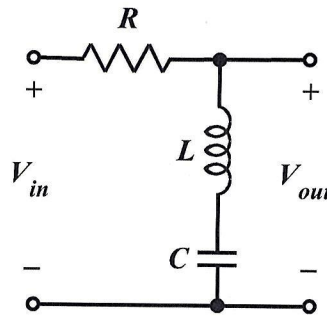


## Homework Problem #023

A passive *RLC* filter circuit is given below.



- a. Determine an expression for the voltage transfer function,  $V_{out}/V_{in}$ . Also, determine expressions for the magnitude and the phase angle of that transfer function.

$$\frac{1}{R}(V_{in} - V_{out}) = \frac{V_{out}}{j\omega L + \frac{1}{j\omega C}} \Rightarrow \frac{1}{R}V_{in} = \left(\frac{1}{R} + \frac{1}{j\omega L + \frac{1}{j\omega C}}\right)V_{out}$$

$$\frac{V_{out}}{V_{in}} = \frac{\frac{1}{R}}{\frac{1}{R} + \frac{1}{j\omega L + \frac{1}{j\omega C}}} = \frac{1}{1 + \frac{j\omega RC}{1 - \omega^2 LC}} = \frac{1 - \omega^2 LC}{(1 - \omega^2 LC) + j\omega RC}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{|1 - \omega^2 LC|}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}}$$

$$\angle \frac{V_{out}}{V_{in}} = -\tan^{-1} \left( \frac{\omega RC}{1 - \omega^2 LC} \right)$$

- a. Classify the filter as LP, HP, BP or BS, and explain your reasoning.

$$\lim_{\omega \rightarrow 0} \left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{1} = 1$$

$$\lim_{\omega \rightarrow \infty} \left| \frac{V_{out}}{V_{in}} \right| = \frac{\omega^2 LC}{\omega^2 LC} = 1$$

$$\text{If } \omega = \frac{1}{\sqrt{LC}}, \text{ then } \left| \frac{V_{out}}{V_{in}} \right| = 0$$

This is a Band Stop  
(BS) filter  
characteristic