

EE 3340

Homework Problem #028

Use LTspice to verify that this circuit has a resonance frequency of $\omega_R = \frac{1}{\sqrt{LC - R^2C^2}}$ rad/s.

