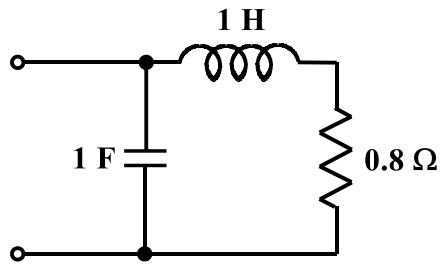


EE 3340  
**Homework Problem #029**



Use LTspice to determine:

(a) the resonance frequency for this circuit, and

(b) the input impedance at that frequency.