

Homework Problem #031

Determine the input impedance of the circuit shown below in rectangular form at $\omega = 2$ rad/s. Show your work.

