

EE 3340
Homework Problem #033

Use LTspice to verify that this circuit has a resonance frequency of $\sqrt{\frac{5}{21}}$ rad/s.

