

EE 3340
Homework Problem #035

Symbolically determine the voltage transfer function V_2/V_1 .

