

Homework Problem #039

The circuit shown below is operating in a **DC** steady-state condition. Determine the **DC** current I_x .

