

Homework Problem #042

Determine the line currents (I_{aA} , I_{bB} and I_{cC}) in the three-phase balanced Y-Y circuit shown.

