
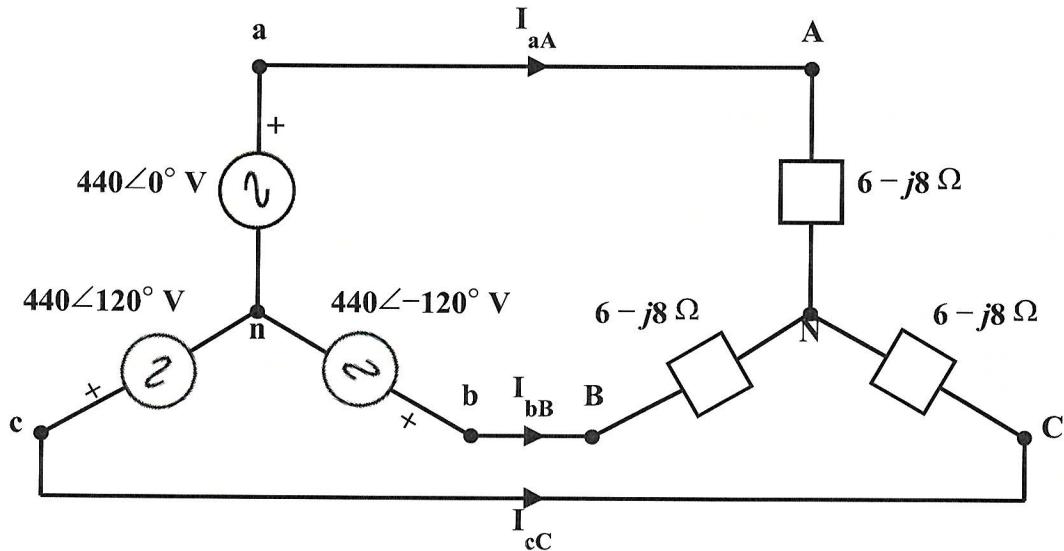


EE 3340
Homework Problem #042

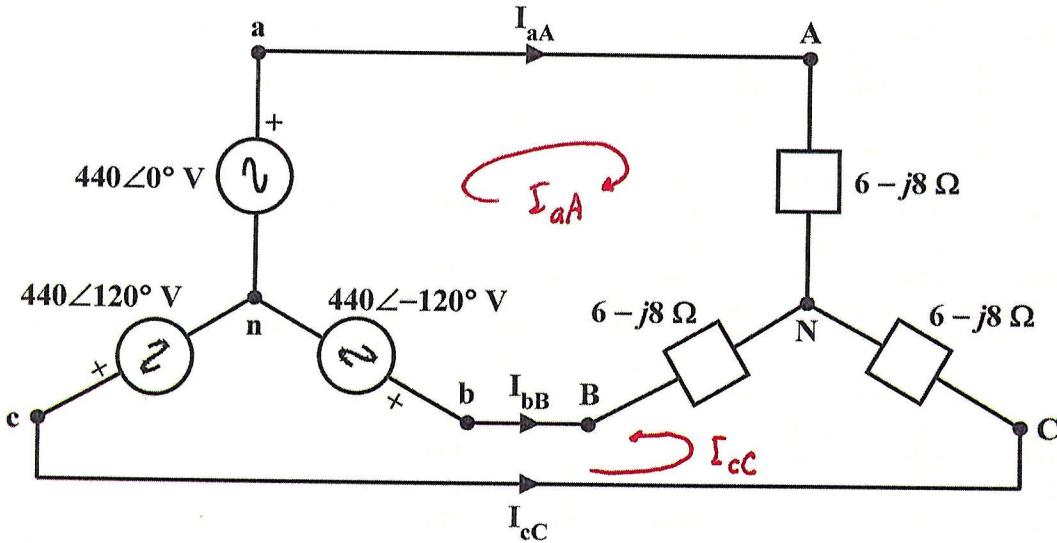Determine the line currents (I_{aA} , I_{bB} and I_{cC}) in the three-phase balanced Y-Y circuit shown.



See the attached pages for 3 methods
of solution.



$$-440\angle 0^\circ + (6-j8) \Sigma_{AA} + (6-j8)(\Sigma_{AA} + \Sigma_{CC}) + 440\angle -120^\circ = 0$$

$$440\angle 120^\circ - 440\angle -120^\circ - (6-j8)(\Sigma_{AA} + \Sigma_{CC}) - (6-j8)\Sigma_{CC} = 0$$

or

$$(12-j16) \Sigma_{AA} + (6-j8)\Sigma_{CC} = 440 - 440\angle -120^\circ$$

$$-(6-j8)\Sigma_{AA} - (12-j16)\Sigma_{CC} = 440\angle -120^\circ - 440\angle 120^\circ$$

or

$$(12-j16) \Sigma_{AA} + (6-j8)\Sigma_{CC} = 440\{1 - \cos(120^\circ) - j \sin(120^\circ)\}$$

$$-(6-j8)\Sigma_{AA} - (12-j16)\Sigma_{CC} = 440\{\cos(-120^\circ) + j \sin(-120^\circ) - \cos(120^\circ) - j \sin(120^\circ)\}$$

See MATLAB solution on the next page.

```

>> A=[12-j*16 6-j*8; -(6-j*8) -(12-j*16)]
A =
 12.0000 -16.0000i   6.0000 - 8.0000i
 -6.0000 + 8.0000i -12.0000 +16.0000i

>> c=440*[1-cosd(-120)-j*sind(-120); cosd(-120)+j*sind(-120)-
cosd(120)-j*sind(120)]

c =
 1.0e+02 *
 6.6000 + 3.8105i
 0.0000 - 7.6210i

>> meshCurrents=A\c

meshCurrents =
 26.4000 +35.2000i
 -43.6841 + 5.2631i

>> abs(meshCurrents(1))

ans =
 44

```

$I_{AA} = 44 \angle 53.13^\circ \text{ A}$

```

>> angle(meshCurrents(1))*180/pi

ans =
 53.1301

```

$I_{CC} = 44 \angle 173.13^\circ \text{ A}$

```

>> abs(meshCurrents(2))

ans =
 44.0000

```

$I_{BB} = 44 \angle -66.87^\circ \text{ A}$

```

>> angle(meshCurrents(2))*180/pi

ans =
 173.1301

```

```

>> IbB=-meshCurrents(1)-meshCurrents(2)

IbB =
 17.2841 -40.4631i

>> abs(IbB)

ans =
 44.0000

```

$I_{BB} = 44 \angle -66.87^\circ \text{ A}$


```

>> angle(IbB)*180/pi

ans =
 -66.8699

```

Alternately,

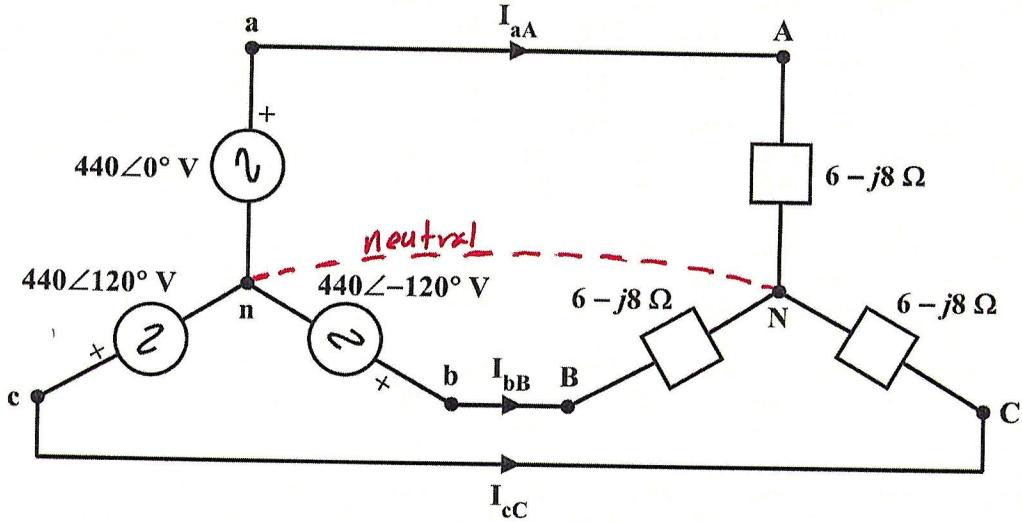


$$I_{aA} = \frac{440 \angle 0^\circ}{6-j8} = 44 \angle 53.13^\circ \text{ A}$$

$$I_{bB} = \frac{440 \angle -120^\circ}{6-j8} = 44 \angle -66.87^\circ \text{ A}$$

$$I_{cC} = \frac{440 \angle 120^\circ}{6-j8} = 44 \angle 173.13^\circ \text{ A}$$

Or

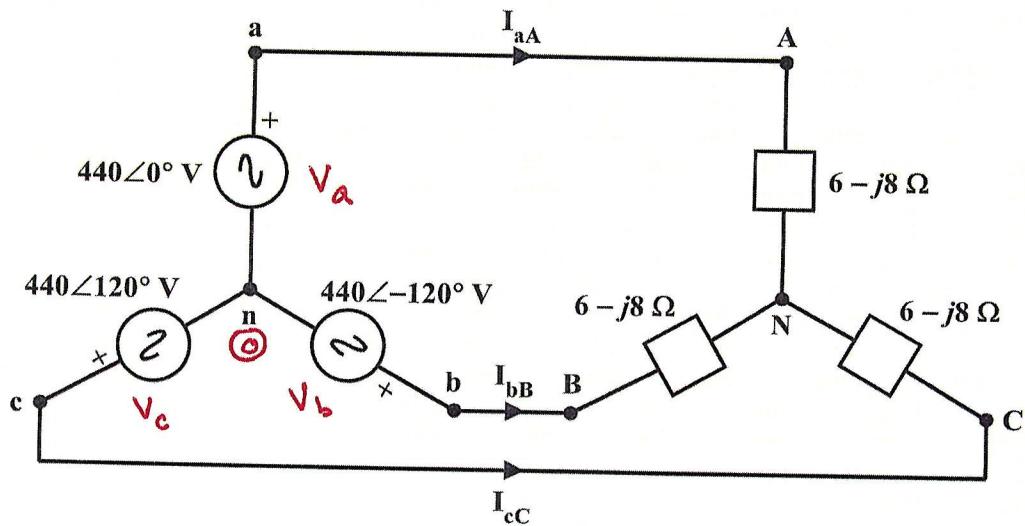

Use LTspice:

Assume $\omega = 1 \text{ rad/s}$. Then

$6-j8$ is a 6Ω resistor in series with a capacitor having value $\frac{1}{8} \text{ F}$.

V _a	a	0	AC	440	0
V _b	b	0	AC	440	-120
V _c	c	0	AC	440	120
R _A	A	1	6Ω		
C _A	1	N	$\{1/8\}$		
R _B	B	2	6Ω		
C _B	2	N	$\{1/8\}$		
R _C	C	3	6Ω		
C _C	3	N	$\{1/8\}$		
,AC	LIN	1	0.159154943	0.159154943	

LTspice XVII - [04.cir]

File Edit View Simulate Tools Window Help

* Q:\Websites\RES\EE 3340\homework problems\042.cir

```

Va a 0 AC 440 0
Vb b 0 AC 440 -120
Vc c 0 AC 440 120
RA A 1 6
CA 1 N {1/8}
RB B 2 6
CB 2 N {1/8}
RC C 3 6
CC 3 N {1/8}
.AC LIN 1 0.159154943 0.159154943
.end

```

* Q:\Websites\RES\EE 3340\homework problems\04.cir

--- AC Analysis ---

frequency:	0.159155 Hz
V(a):	mag: 440 phase: -3.70101e-015° voltage
V(b):	mag: 440 phase: -120° voltage
V(c):	mag: 440 phase: 120° voltage
V(l):	mag: 352 phase: -36.8699° voltage
V(n):	mag: 5.1238e-014 phase: 33.6901° voltage
V(2):	mag: 352 phase: -156.87° voltage
V(3):	mag: 352 phase: 83.1301° voltage
I(Cc):	mag: 44 phase: 173.13° device_current
I(Cb):	mag: 44 phase: -66.8699° device_current
I(Ca):	mag: 44 phase: 53.1301° device_current
I(Rc):	mag: 44 phase: 173.13° device_current
I(Rb):	mag: 44 phase: -66.8699° device_current
I(Ra):	mag: 44 phase: 53.1301° device_current
I(Vc):	mag: 44 phase: -6.8699° device_current
I(Vb):	mag: 44 phase: 113.13° device_current
I(Va):	mag: 44 phase: -126.87° device_current

I_{cC}



I_{bB}



I_{aA}



$$I_{aA} = I(R_a) = 44 \angle 53.13^\circ A$$

$$I_{bB} = I(R_b) = 44 \angle -66.87^\circ A$$

$$I_{cC} = I(R_c) = 44 \angle 173.13^\circ A$$