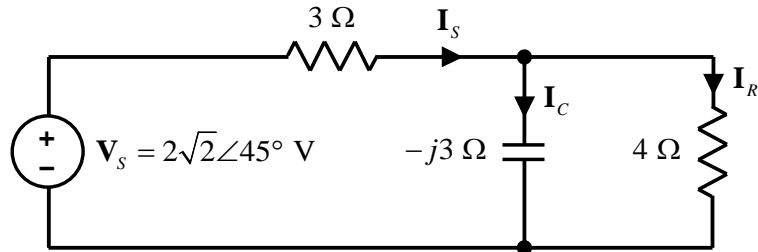


EE 3340
Homework Problem #044

For the circuit shown:



- (a) Apply current division to express \mathbf{I}_C and \mathbf{I}_R in terms of \mathbf{I}_S (*Not* in terms of \mathbf{V}_s).
- (b) Using \mathbf{I}_S as reference, accurately sketch a *relative* phasor diagram showing \mathbf{I}_C , \mathbf{I}_R , and \mathbf{I}_S and verify that the vector sum $\mathbf{I}_R + \mathbf{I}_C = \mathbf{I}_S$ is satisfied.
- (c) Now, fully analyze the circuit to determine \mathbf{I}_S and then accurately sketch the *absolute* phasor diagram with \mathbf{I}_C , \mathbf{I}_R , and \mathbf{I}_S drawn according to their true phase angles.